



# Transformers

(Part B)

## Practical Transformers

ECET 3500 – Survey of Electric Machines




## Ideal Transformer Model

Although the circuit model shown below can be used to define the operation of an **ideal transformer**, the “real world” operational characteristics of a transformer cannot be predicted by this model because it does not account for the internal losses and/or other non-ideal qualities of a practical transformer.

For this reason, we will develop a model for a practical transformer.

$$a = \frac{N_p}{N_s} \equiv \text{turns ratio}$$
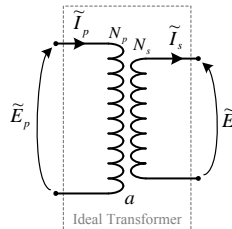
$$\frac{\tilde{E}_p}{\tilde{E}_s} = a \quad \frac{\tilde{I}_p}{\tilde{I}_s} = \frac{1}{a}$$





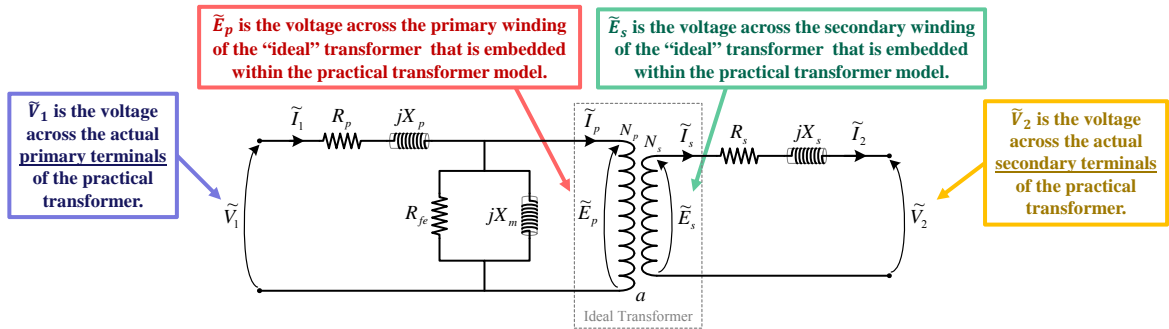
# Practical Transformer Model

A circuit model for a **practical transformer** can be developed by expanding the ideal transformer model to include additional circuit elements that account for the “losses” that occur when operating an actual transformer.


The following circuit model, which is typically referred to as either the **Cantilever Equivalent Circuit** or the **Steinmetz Equivalent Circuit**, is often used to predict the operation of a practical transformer.


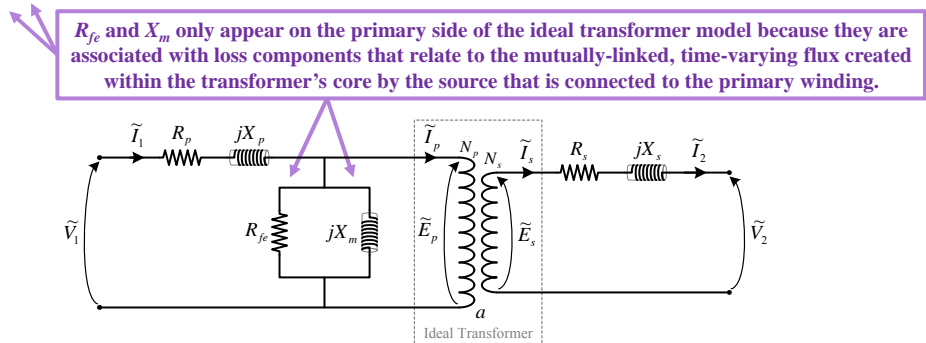
# Practical Transformer Model

Within the model for a **practical transformer**:

- $R_p$  and  $R_s$  account for the primary and secondary **winding resistances**
- $X_p$  and  $X_s$  account for the primary and secondary winding **leakage reactances**
- $R_{fe}$  accounts for the **Hysteresis/Eddy-Current losses** within the core
- $X_m$  accounts for the **magnetization current** drawn into the primary winding





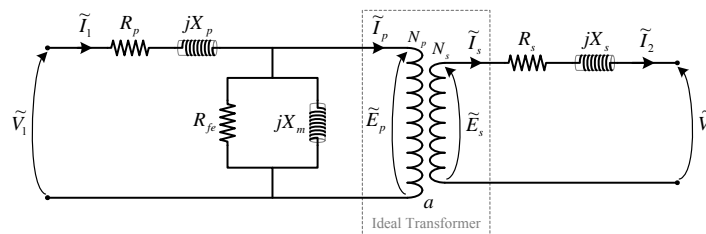
## Practical Transformer Model

Note – The circuit shown below is used to model the steady-state operation of transformers that have relatively low operating frequencies.  
(I.e. – **60Hz** or “power” transformers)


*A different model may be required for transformers that operate at higher frequencies in order to properly account for other “losses” that are typically neglected at 60Hz.*


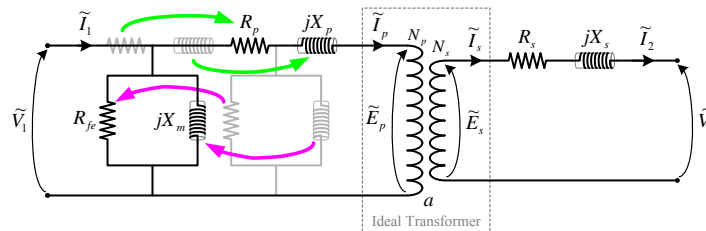
## Practical Transformer Model

In order to reduce the model’s complexity, the parallel elements  $R_{fe}$  and  $X_m$  can be moved to the “left-side” of the series elements  $R_p$  and  $X_p$ .

Note – This change should only introduce a small decrease in the overall accuracy of the model because  $R_{fe}$  and  $X_m$  are typically much larger in magnitude than  $R_p$  and  $X_p$ .






## Practical Transformer Model

Additionally, the series elements  $R_s$  and  $X_s$  can be referred (moved) to the primary-side of the ideal transformer provided that their values are each multiplied by  $a^2$ .

Note – as defined in the figure:  $R'_s = a^2 R_s$   
 $X'_s = a^2 X_s$

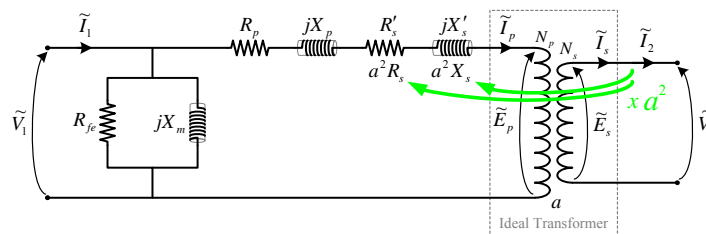The “prime” denotes that the impedance was referred to the primary-side of the ideal transformer.




## Practical Transformer Model

Then, the series resistive elements  $R_p$  and  $R'_s$  can then be combined into an equivalent resistive element  $R_{eq}$ , and the series reactive elements  $X_p$  and  $X'_s$  can be combined into an equivalent reactive element  $X_{eq}$ :

$$R_{eq} = R_p + R'_s$$

$$X_{eq} = X_p + X'_s$$

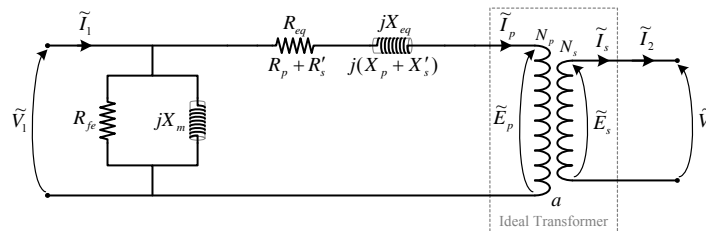where:  $R_{eq}$  and  $X_{eq}$  account for the overall resistance and leakage reactance of the transformer's windings.





## Example Problem


Given a **500VA, 60Hz, 240V–120V practical transformer** with the following equivalent circuit parameters:

$$R_{LV} = 0.20\Omega, X_{LV} = 0.40\Omega, R_{HV} = 0.80\Omega, X_{HV} = 1.20\Omega$$

$$R_{fe(LV)} = 480\Omega, X_{M(LV)} = 160\Omega \leftarrow \text{(both referred to the LV-winding)}$$

If the transformer is used to step-up the voltage from a **120 volt** source while supplying a load,  $Z_{Load} = (120 + j50)\Omega$ ...

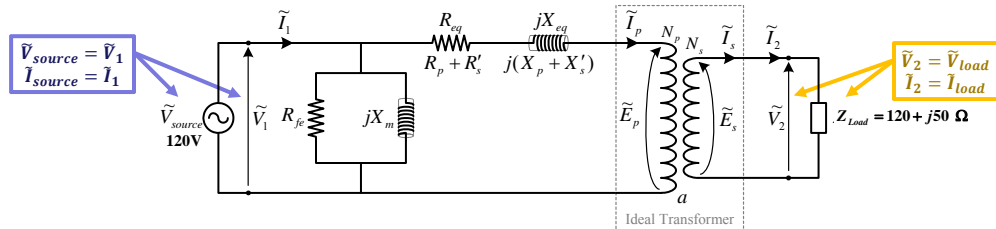Determine the **actual load voltage,  $\tilde{V}_2$** , and the overall **source current,  $\tilde{I}_1$** .



## Determining the Model Parameters

To begin the problem, the transformer's **operational turns-ratio** must be determined...


Since the transformer is being used to **step-up** the **120V** source voltage:

- the **120V winding is the primary winding**
- the **240V winding is the secondary winding**

← **LV winding**

← **HV winding**

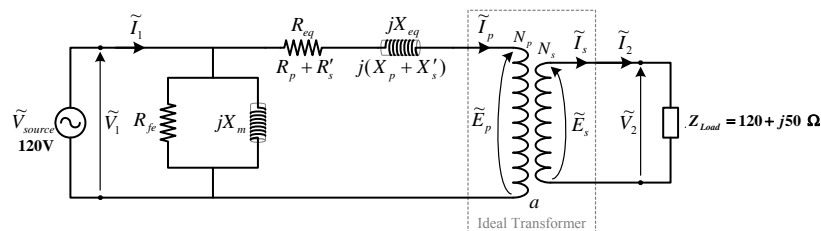Therefore, the **operational turns-ratio** is:  $a = \frac{120\text{ V}}{240\text{ V}} = \frac{1}{2}$





## Determining the Model Parameters

Additionally, since the **low-voltage winding** is the **primary winding**, the circuit parameters relating to the HV and LV sides may be redefined as:


$$R_p = R_{LV} = 0.20\Omega, \quad X_p = X_{LV} = 0.40\Omega,$$

$$R_s = R_{HV} = 0.80\Omega, \quad X_s = X_{HV} = 1.20\Omega,$$

from which  $R_{eq}$  and  $X_{eq}$  can be determined:

$$R_{eq} = R_p + a^2 R_s = 0.20 + \left(\frac{1}{2}\right)^2 (0.80) = 0.40\Omega$$
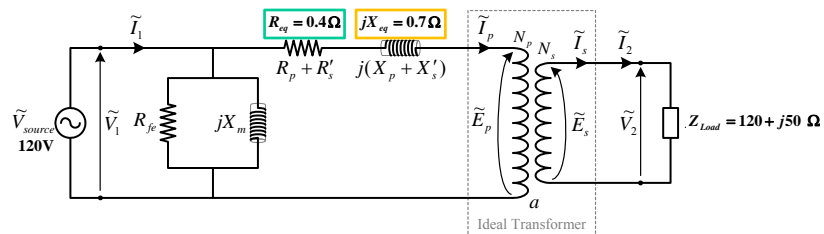
$$X_{eq} = X_p + a^2 X_s = 0.40 + \left(\frac{1}{2}\right)^2 (1.20) = 0.70\Omega$$




## Determining the Model Parameters

Note that, as defined in the problem statement,  $R_{fe}$  and  $X_m$  were both referred to the LV winding:

$$R_{fe(LV)} = 480\Omega \quad X_{M(LV)} = 160\Omega$$

Since the LV winding is the primary winding, both of those impedances can be directly imported into the model.

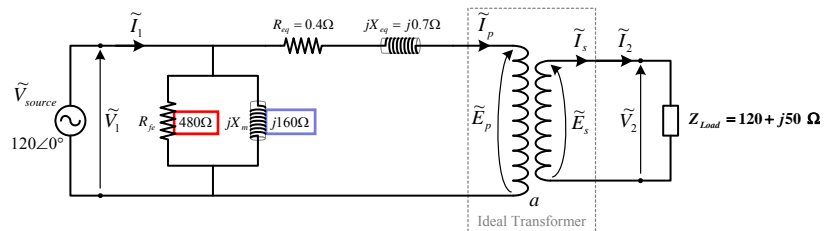Thus, the following figure shows the circuit model for the practical transformer with all of the parameters included:





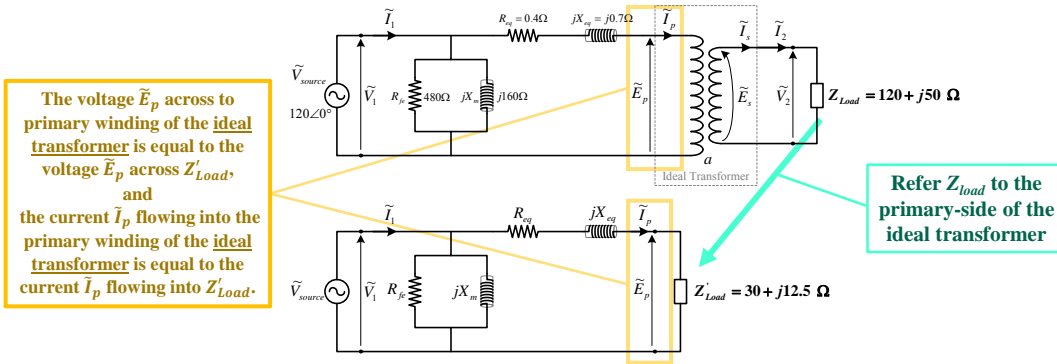
# Referring the Load to the Primary-Side

In order to simplify the overall circuit, the “**ideal transformer**” portion of the model can be removed by referring the load to the primary-side of the ideal transformer, such that:


$$Z'_{Load} = a^2 Z_{Load} = \left(\frac{1}{2}\right)^2 (120 + j50) = (30 + j12.5)\Omega$$


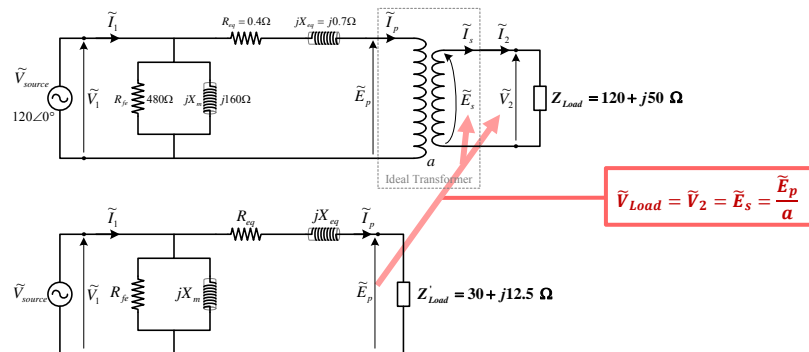
# Solving for the Load Voltage

Note that, although  $\tilde{E}_s$  is the voltage across the actual load  $Z_{Load}$  in the original circuit,  $\tilde{E}_p$  is the voltage across  $Z'_{Load}$  in the simplified circuit.

Thus, the **actual load voltage**,  $\tilde{E}_s$ , can be determined by first solving for  $\tilde{E}_p$  in the simplified circuit and then using the turns-ratio equation to get  $\tilde{E}_s$ .






## Solving for the Load Voltage

Since  $Z'_{Load}$  is in series with both  $R_{eq}$  and  $jX_{eq}$  in the simplified circuit, the voltage  $\tilde{E}_p$  can be determined using a voltage-divider equation:

$$\tilde{E}_p = \tilde{V}_1 \cdot \left( \frac{Z'_{Load}}{R_{eq} + jX_{eq} + Z'_{Load}} \right) = 120\angle 0^\circ \cdot \left( \frac{30 + j12.5}{0.4 + j0.7 + 30 + j12.5} \right) = 117.7\angle -0.85^\circ \text{ volts}$$

The **load voltage** can then be solved by utilizing the turns-ratio equation:
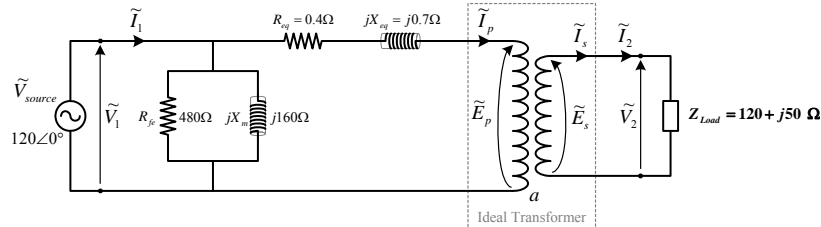
$$\tilde{V}_{load} = \tilde{V}_2 = \tilde{E}_s = \frac{\tilde{E}_p}{a} = \frac{117.7\angle -0.85^\circ}{\frac{1}{2}} = 235.4\angle -0.85^\circ \text{ volts}$$




## Solving for the Source Current

In order to solve for the **source current**  $\tilde{I}_1$ , the input impedance “looking” into the primary terminals of the practical transformer must be determined:

$$Z_{in} = R_{fe} \parallel X_m \parallel (R_{eq} + jX_{eq} + Z'_{load}) = \left( \frac{1}{480} + \frac{1}{j160} + \frac{1}{30.4 + j13.2} \right)^{-1} = 24.4 + j15.0 \Omega$$

after which the **source current**,  $\tilde{I}_1$ , can be determined by:
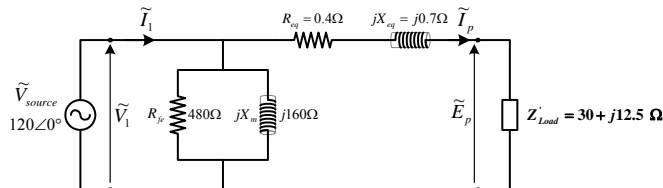
$$\tilde{I}_{source} = \tilde{I}_1 = \frac{\tilde{V}_1}{Z_{in}} = \frac{120\angle 0^\circ}{24.4 + j15.0} = 4.19\angle -31.6^\circ \text{ amps}$$








## Determining the Model Parameters

The model parameters for a specific transformer are often unknown because they aren't typically provided by the manufacturer.

But, the parameters can be determined by performing a simple pair of tests on the transformer:

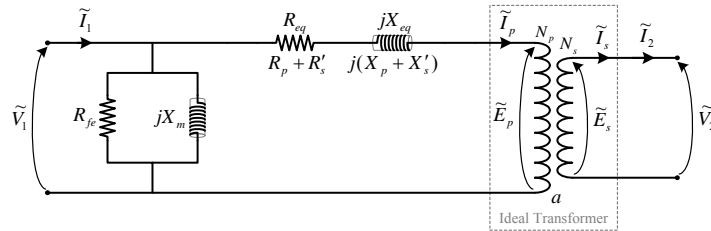
- The **Open-Circuit Test**, and
- The **Short-Circuit Test**.


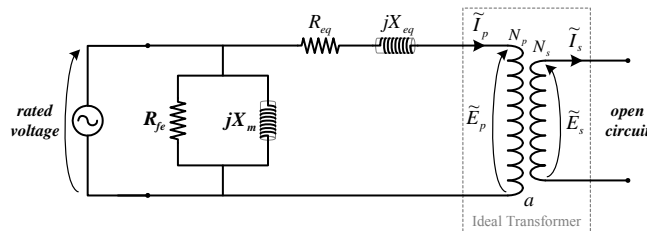
## The Open-Circuit Test

The **core-loss parameters**  $R_{fe}$  and  $X_m$  can be determined by performing an **Open-Circuit Test** on the transformer.

The **Open-Circuit Test** is typically performed by applying rated voltage to the primary winding of the transformer while leaving the secondary winding open-circuited.






## The Open-Circuit Test

If the secondary is open-circuited, then the current  $\tilde{I}_s$  must be zero:

$$\tilde{I}_s = 0$$

And, if the current  $\tilde{I}_s$  is zero, then the current  $\tilde{I}_p$  flowing into the primary winding of the ideal transformer must also be zero:

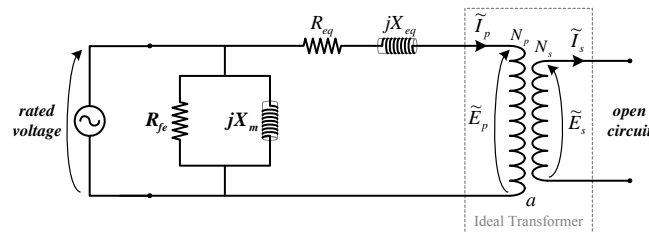
$$\tilde{I}_p = \frac{\tilde{I}_s}{a} = \frac{0}{a} = 0$$


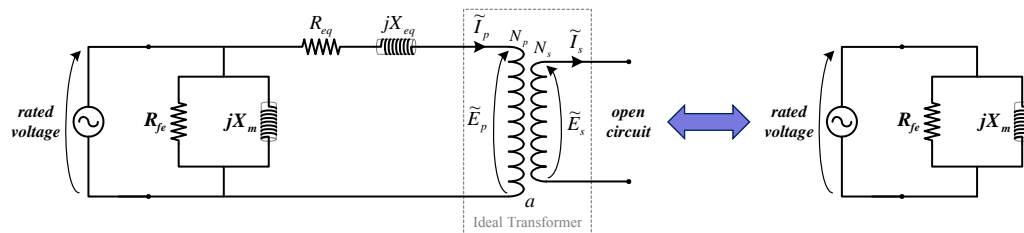
## The Open-Circuit Test

If the current  $\tilde{I}_p$  is zero, then no current will be flowing through the series elements  $R_{eq}$  and  $X_{eq}$ .

Thus, the only active portion of the circuit under **open-circuit conditions** is the parallel combination of branches containing the core-loss elements  $R_{fe}$  and  $X_m$ .






## The Open-Circuit Test

Apply rated voltage  $E_{oc}$  to the primary-winding of the transformer with the secondary-winding open-circuited.

Measure the current  $I_{oc}$  and the real power  $P_{oc}$  supplied by the source.

The values of the **core-loss elements** can be determined from:
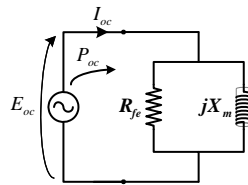
$$R_{fe} = \frac{E_{oc}^2}{P_{oc}} \quad X_m = \frac{E_{oc}^2}{\sqrt{(E_{oc} \cdot I_{oc})^2 - P_{oc}^2}}$$




## The Short-Circuit Test

The **winding-loss parameters**  $R_{eq}$  and  $X_{eq}$  can be determined by performing a **Short-Circuit Test** on the transformer.

The **Short-Circuit Test** is typically performed by supplying rated current to the primary winding of the transformer while the secondary winding is short-circuited.

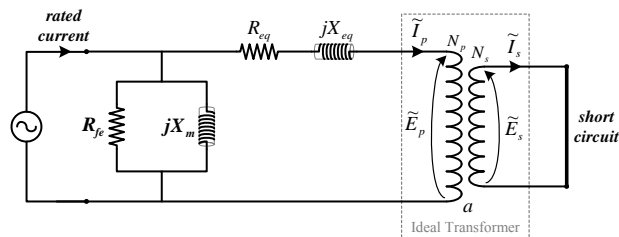**\*\*\* Warning – Only a small primary voltage is required in order to \*\*\*  
 \*\*\*\*\* reach rated current under short-circuit conditions \*\*\*\*\***






## The Short-Circuit Test

Under short-circuit conditions, the ideal transformer portion of the model can be replaced by an ideal wire since:

$$Z'_{Load} = a^2 Z_{Load} = a^2(0) = 0 \Omega$$

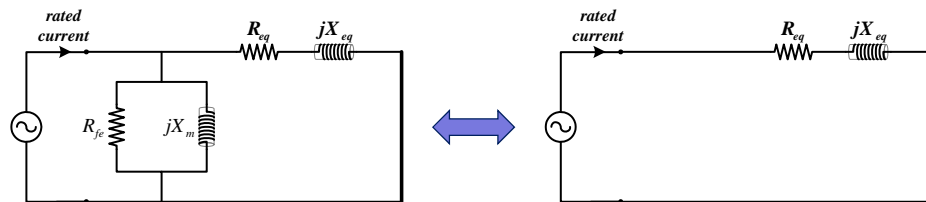And, since the impedance magnitudes of  $R_{fe}$  and  $X_m$  are typically much larger than those of  $R_{eq}$  and  $X_{eq}$ , the elements  $R_{fe}$  and  $X_m$  can be neglected without affecting the accuracy of the model.



## The Short-Circuit Test

Supply rated current  $I_{sc}$  to the primary-winding of the transformer with the secondary-winding short-circuited.

Measure the voltage  $E_{sc}$  and the real power  $P_{sc}$  supplied by the source.

The values of the **winding-loss elements** can be determined from:

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2} \quad X_{eq} = \frac{\sqrt{(E_{sc} \cdot I_{sc})^2 - P_{sc}^2}}{I_{sc}^2}$$

