Two loads are served out of Panel #1 by a pair of individual branch circuits, as shown below:



PART 1: Determine the magnitude of each load current.

$$Load#1 = \underline{56} \quad A \quad Load#2 = \underline{126} \quad A$$
$$I_{Line-Rated(Load#1)} = \frac{VA_{3\Phi}}{\sqrt{3} \cdot V_{Line-Rated}} = \frac{45,000}{\sqrt{3} \cdot 460} = 56.48A \Longrightarrow 56A$$
$$I_{Line-Rated(Load#2)} = \frac{W_{3\Phi}}{\sqrt{3} \cdot V_{Line-Rated}} = \frac{100,000}{\sqrt{3} \cdot 460 \cdot 1} = 125.51A \Longrightarrow 126A$$

Article 220.5(B) Calculations – Fractions of an Ampere – Calculations shall be permitted to be rounded to the nearest whole ampere, with decimal fractions smaller than 0.5 dropped.

<u>PART 2</u>: a) Determine the minimum-sized conductors and the smallest standard-sized circuit breaker for each branch circuit if <u>a separate conduit is used for each circuit</u> and <u>the ambient temp. is 30°C</u>:

Circuit #1: conductor size <u>4 AWG</u> CB#1 rating <u>70</u> A

Determine the minimum required conductor size:



Since the circuit will be rated ≤ 100 A, apply a <u>60°C temperature rating</u> to the conductors.

Based on Table 310.15(B)(16) – 4 AWG copper with a 60°C rating has an ampacity of 70A

Determine the minimum circuit breaker size:

 $CB_{rating} \ge 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = 1.25 \cdot 56 = 70A$

Thus, choose a **70A** circuit breaker.

Circuit #2: conductor size <u>1 AWG</u> CB#2 rating <u>150</u> A

Minimum required conductor size:

ampacity $\geq 126A$ Since the circuit will be rated $\geq 100A$, apply a conductor <u>75°C temp. rating</u>. Based on Table 310.15(B)(16) – **1 AWG** copper with a 75°C rating has an ampacity of **130A** Determine the minimum circuit breaker size:

 $CB_{rating} \ge 126A$ Choose a **150A** circuit breaker. **240.4(B)** <u>allows next higher CB above ampacity</u>.

PART 2: b) Assuming that (feeder) circuit #3 must serve both loads, determine the minimum-sized conductors and the smallest standard-sized circuit breaker that can be used for circuit #3:

Circuit #3: conductor size <u>3/0 AWG</u> CB#2 rating <u>200</u> A

Determine the minimum required conductor size:

REQUIRED AMPACITY BASED ON CONTINUOUS CURRENT ampacity $\geq 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = (126) + (1.25 \cdot 56) = 196A$

REQUIRED AMPACITY BASED ON ADJUSTMENT FACTORS

ampacity $\ge \frac{I_{actual}}{adjustment factors} = \frac{126 + 56}{(1) \cdot (1)} = 182A$

Since the circuit will be rated >100A, apply a <u>75°C temperature rating</u> to the conductors.

Based on Table 310.15(B)(16) – **3/0 AWG** copper with a 75°C rating has an ampacity of **200A**

Determine the minimum circuit breaker size:

 $CB_{rating} \ge 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = (126) + (1.25 \cdot 56) = 196A$

Thus, choose a **200A** circuit breaker.

<u>PART 3</u>: Repeat the steps specified in Part 2 (a) and (b), but with the following system changes:

- i) The conductors for circuits (#1 and #2) are in the same conduit (i.e. -6 conductors in raceway), and
- ii) The <u>ambient temperature is 38°C</u>:

conductor size <u>3 AWG</u> CB#1 rating <u>70</u> A Circuit #1: Based on Table 310.15(B)(3)(a): ampacity $\geq 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = 1.25 \cdot 56 = 70 \text{A}$ 4-6 cond. in raceway 0.80 Adj. Factor ampacity $\ge \frac{I_{actual}}{adjustment factors} = \frac{56}{(0.8) \cdot (0.82)} = 85A$ Based on Table 310.15(B)(2)(a): **3 AWG** copper with a 60°C rating has an ampacity of **85A** 38°C Ambient Temp. with 60°C Temp. Rating $CB_{rating} \ge 1.25 \cdot 56 = 70A$ Choose a **70A** circuit breaker. 0.82 Adj. Factor conductor size <u>3/0 AWG</u> CB#1 rating <u>150</u> A Circuit #2: ampacity $\geq 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = 1.126 = 126A$ ampacity $\ge \frac{I_{actual}}{adjustment factors} = \frac{126}{(0.8) \cdot (0.82)} = 192A$ Based on Table 310.15(B)(16) – **3/0 AWG** copper with a 75°C rating has an ampacity of **200A** $CB_{rating} \ge 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = 1.126 = 126A$ Choose a **150A** circuit breaker. conductor size <u>4/0 AWG</u> CB#1 rating <u>200</u> A Circuit #3: ampacity $\geq 100\% \cdot I_{non-continuous} + 125\% \cdot I_{continuous} = (126) + (1.25 \cdot 56) = 196$ A Only the Ambient Temp. factor ampacity $\ge \frac{I_{actual}}{adjustment factors} = \frac{126 + 56}{(0.8) \cdot (1)} = 228A$ applies to Circuit #3 since it doesn't share a conduit.

Based on Table 310.15(B)(16) -4/0 AWG copper with a 75°C rating has an ampacity of 230A ampacity $\ge (126) + (1.25 \cdot 56) = 196$ A Choose a 200A circuit breaker.