

Problem #2) Given the 3 Φ , 480V feeder from problem #1, if the circuit conductors are **200' long**,

a) Determine the **drop** that will occur in the line-voltage of the feeder while supplying rated load.

$$V_{\text{drop(Line)}} = \underline{\hspace{2cm}} \text{ V}$$

b) Does the voltage-drop calculated in part **(a)** fall under **acceptable standards** as recommended in the NEC? Justify/explain your answer:

Circle your answer \rightarrow Yes / No
(Explain in the space below)

c) If the 3 Φ , L-L-L short-circuit current available at the “service-end” of the feeder is **21,000A**, determine the **short circuit current** that will be available at “load-end” of the feeder using the point-to-point method of calculation.

$$I_{SCA(\text{Load-End})} = \underline{\hspace{2cm}} \text{ amps}$$

Problem #3) Given a 480V, 3 Φ , 60Hz branch circuit that consists of three individual, #6 AWG, THHN, aluminum conductors that are fed through an aluminum conduit,

- a) Determine the **AC resistance** and **reactance** of the conductors in Ω per 1000' (assuming an operational temperature rating of 60°C).

$$R_{AC} = \underline{\hspace{2cm}} \Omega/1000'$$

$$X_L = \underline{\hspace{2cm}} \Omega/1000'$$

- b) If the branch circuit is supplying a load that operates with a power factor of 0.72 lagging, determine the **effective impedance** of the conductors in Ω per 1000'.

$$Z_e = \underline{\hspace{2cm}} \Omega/1000'$$

Problem #4) Determine the **general lighting load** for a **three-story, 160ft x 420ft** (per floor) motel after any appropriate demand factors are applied.

$$\text{General Lighting Load} = \underline{\hspace{2cm}} \text{VA}$$

Problem #5) Given a **3Φ, 150kVA, 7200V– 208V, Δ-Y**, “step-down” transformer that provides service to an industrial building;

a) Determine the **rated phase-voltage** for the low-voltage side of the transformer.

$$V_{Phase(rated)LV} = \underline{\hspace{2cm}} \text{ V}$$

b) Determine the **rated line-current** for both the high-voltage and low-voltage sides of the transformer.

$$I_{Line(rated)HV} = \underline{\hspace{2cm}} \text{ A}$$

$$I_{Line(rated)LV} = \underline{\hspace{2cm}} \text{ A}$$


c) Assuming that an “infinite bus” supplies the transformer’s primary windings, determine the 3Φ, L-L-L **short-circuit current** available at the secondary terminals of the transformer.

$$I_{SCA(Sec)} = \underline{\hspace{2cm}} \text{ A}$$

Problem #6) A raceway contains **four** different 3Φ branch circuits that are all supplying balanced loads. If all four circuits are composed of **#8 AWG, THHN, copper conductors** and the ambient temperature is **42°C**, determine the effective **ampacity** for each of the circuit conductors.

$$Ampacity = \underline{\hspace{2cm}} \text{ A}$$

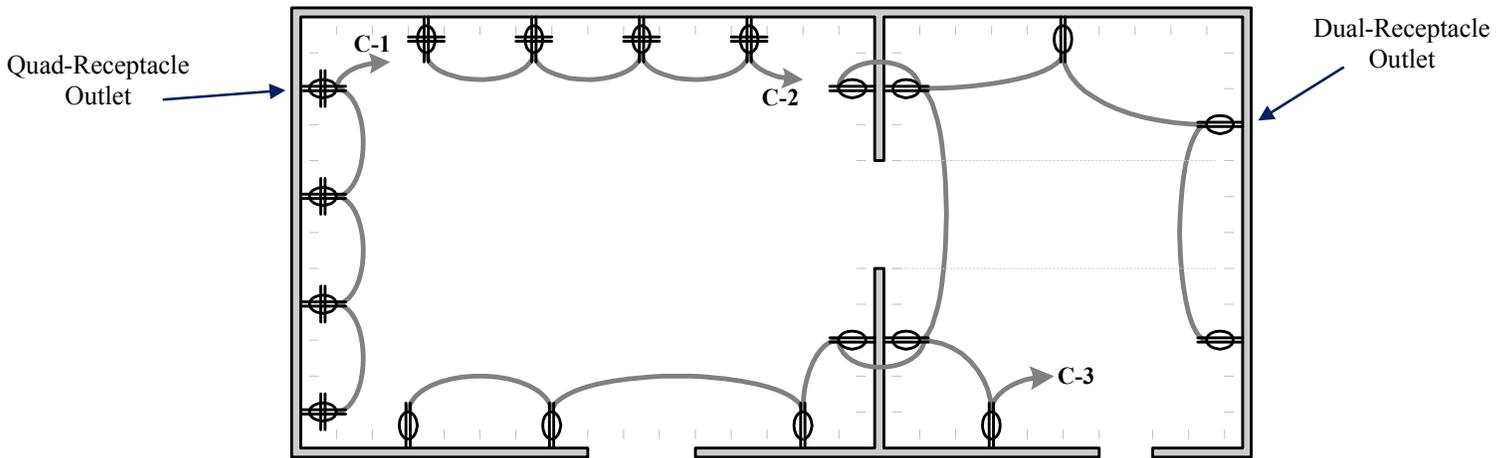Problem #7) The following figure shows three (120V, 1 Φ) general-purpose receptacle circuits located within a building. A separate conduit is utilized for each set of circuit conductors.



Assuming an ambient temperature of 30°C and based on NEC guidelines,

- a) Determine the **minimum load rating** that can be applied to circuit **C-1**, the **smallest-size copper conductors** that can be utilized for the circuit, and the **smallest, standard-sized circuit breaker** that can be used to protect the circuit.
- b) Determine the **minimum load rating** that can be applied to circuit **C-3**, the **smallest-size copper conductors** that can be utilized for the circuit, and the **smallest, standard-sized circuit breaker** that can be used to protect the circuit.

a) C-1 Load Rating = _____ VA

C-1 CB Rating = _____ A


C-1 Conductor Size = _____ AWG

b) C-3 Load Rating = _____ VA

C-3 CB Rating = _____ A

C-3 Conductor Size = _____ AWG

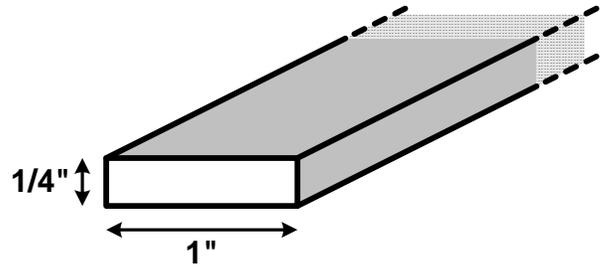Problem #8) Given the rectangular-shaped conductor shown below, determine the **cross-sectional area** of the conductor in **circular mils**.



Area = _____ **cmils**

Problem #9) Specify if the statements are **TRUE** or **FALSE** based on the NEC and/or standard design practice:

- _____ Given a standard **100A circuit breaker** that is protecting a circuit, the circuit breaker may eventually trip if 85A flows continuously in the circuit.
- _____ **Ampacity** may be defined as the maximum continuous current that a conductor may carry without causing the conductor's temperature to exceed its limiting temperature rating designated for the type of insulated conductor involved.
- _____ **Convenience receptacles** should be placed no more than 6 feet apart along any continuous wall within any habitable room of a dwelling unit.
- _____ An **increase in the lengths** of a circuit's conductors will result in an increase in the voltage-drop caused by the circuit, a decrease in the short-circuit current available at the load-end of the circuit, and no change in the ampacity of the circuit's conductors.
- _____ Given a branch circuit that utilizes aluminum conductors, the **ampacity** of the conductors can be increased by switching from aluminum to copper without changing conductor size.
- _____ Branch circuits rated **greater than 50A** can be used to supply heavy-duty lighting outlet loads.
- _____ The **overcurrent protection device** protecting a branch circuit should always be placed at the "load-end" of the circuit conductors.
- _____ According to the NEC, each 3-feet (or fraction thereof) of a **fixed multi-outlet assembly**, where appliances are unlikely to be used simultaneously, shall be considered as one outlet (with a rating) of not less than 180 volt-amperes.

Do Not Write Below This Line _____.


1) ____/8 2) ____/10 3) ____/8 4) ____/6 5) ____/8 6) ____/5 7) ____/10 8) ____/3 9) ____/12
 Total) _____/70

Indust. Dist. & NEC – Exam II pt. B **Print Name (Last Name First):** _____

Instructions: Part “B” of this exam is composed of two “take-home” problems that must be completed individually, under “closed-book” conditions, with no assistance from any person/resource except for the PowerPoint slides, the reference booklet, and the Exam IIA “note-sheet”.

Problem #10) Given the portion of a 3Φ distribution system shown in the following figure:

Note - Assume 30°C ambient temperature.

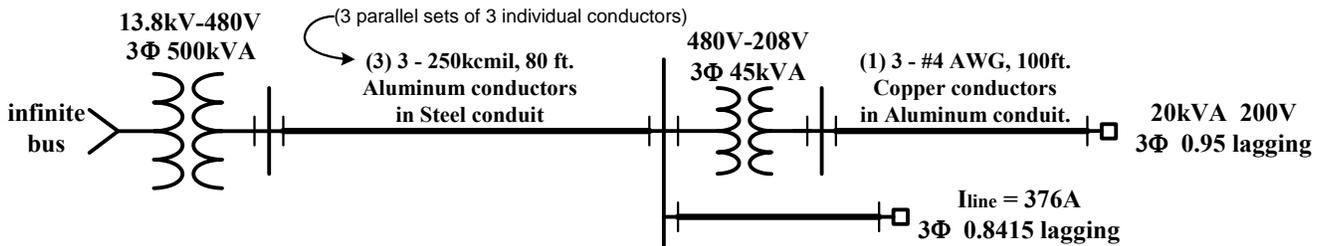

Using the point-to-point method of calculation:

- a) Determine the 3Φ, L-L-L **short circuit current** available at the secondary terminals of the 500kVA transformer.

$$I_{SCA(SecT1)} = \underline{\hspace{10em}} \text{ amps}$$


- b) Determine the 3Φ, L-L-L **short circuit current** available at “load-end” of the 80’ feeder circuit.

$$I_{SCA(Feeder)} = \underline{\hspace{10em}} \text{ amps}$$

- c) Determine the 3Φ, L-L-L **short circuit current** available at the secondary terminals of the 480-208V transformer.

$$I_{SCA(SecT2)} = \underline{\hspace{10em}} \text{ amps}$$

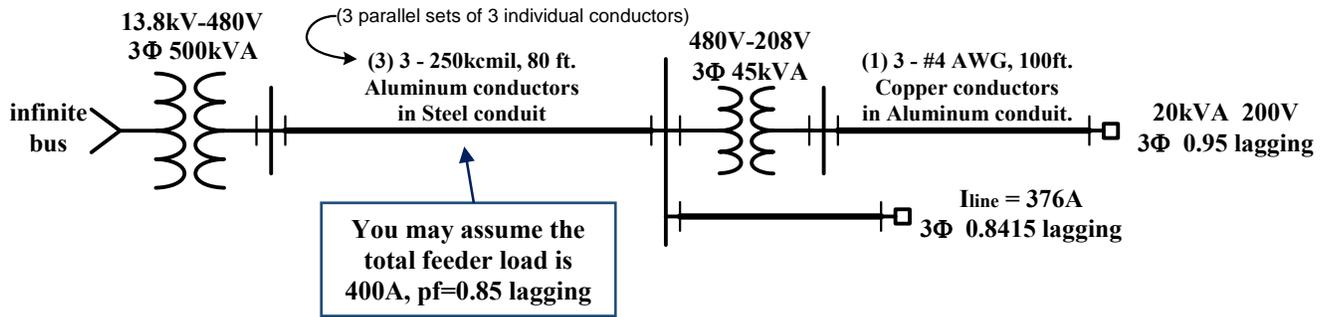Problem #11) Given the same system as in problem #10:



Neglecting any transformer losses, determine the **operational line-voltage** seen at the 20kVA load outlet assuming that rated voltage is present at the secondary terminals of the 500kVA transformer, that the load supplied by the #4 AWG, 100' branch circuit is drawing rated power, and that the total current supplied by the 80' long feeder circuit is 400A at a pf = 0.85 lagging.

$$V_{Line(Load)} = \underline{\hspace{10em}} \text{ volts}$$

Do Not Write Below This Line

Part A) _____/70 10) _____/14 11) _____/16

Total) _____/100