






## Presentation Format – Part A

This presentation on Ladder Logic Programming will begin by introducing the overall structure of a Ladder Diagram.

Included within the introduction is a brief discussion on the general types of Instructions that will appear within a Ladder Diagram, and the overall flow of the program as it is executed.

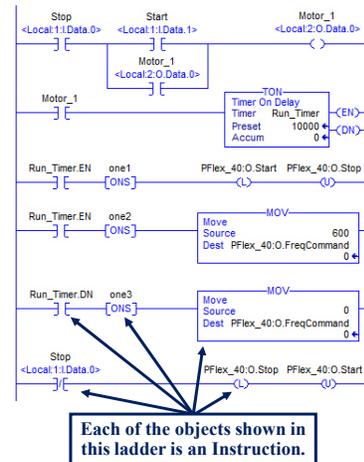Several commonly used Instructions will then be discussed in detail, including both the format of the instructions and their operation when utilized within a Ladder Logic Program.




## Presentation Format – Part B

The second part of this presentation will focus on the practical implementation of Ladder Logic Programming in order to control the operation of a PLC.

The method for linking the operation of the PLC's Input and Output Ports to the operation of the Instructions within a Ladder Diagram will first be presented, after which several

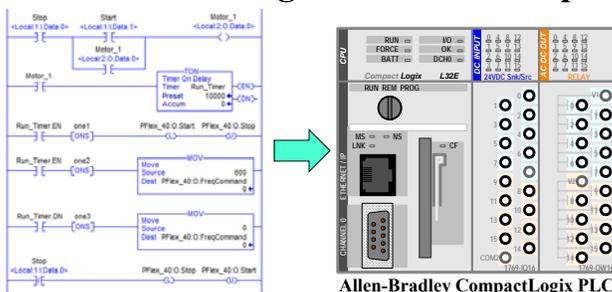basic control system tasks will be implemented with the use of Ladder Logic Programming.







# RSLogix/Studio 5000

**RSLogix 5000\*** is a platform developed by Rockwell Software for the programming of Allen-Bradley PLCs.

RSLogix 5000 (v.21) is shown in this presentation since we will utilize that software to program the PLCs in the lab.

Note that Ladder Logic is not exclusive to the RSLogix platform.

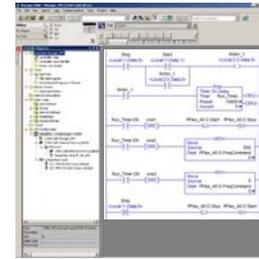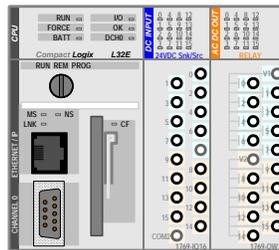It is a standardized programming language (IEC 61131-3) that has been adopted by all PLC manufacturers because of its structural similarity to relay-logic-based control circuits.



RSLogix 5000 Software Platform

\* – Studio 5000 is the new version of the RSLogix platform that was developed to support PLCs with multi-core processors. Although this presentation discusses RSLogix 5000, the contents also applies to the Studio 5000 platform.



(Part A)


## *Introduction to Ladder-Diagrams*


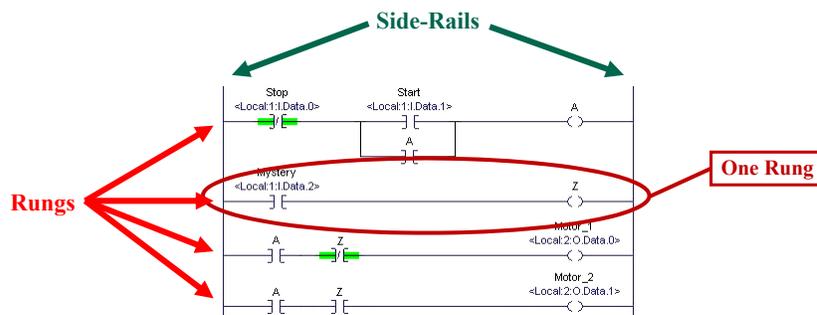
# Ladder Diagrams

Ladder Diagrams are graphical representations of a ladder logic program.

They are named such because of their ladder-like appearance, with two vertical Side-Rails and multiple horizontal Rungs.



## Ladder Diagrams – Rungs

The Rungs of the Ladder Diagram contain multiple Instructions that, when combined together, can provide the function of one or more lines of code in a text-based programming language.

For example, the function

let C=1 if (A=1 and B=0) else let C=0

can be implemented using either Ladder-Logic or C++ as:



Ladder Logic Rung

```

If ( A == 1 && B == 0 ) {
  C = 1
}
else {
  C = 0
}

```


C++ If-Else Statement


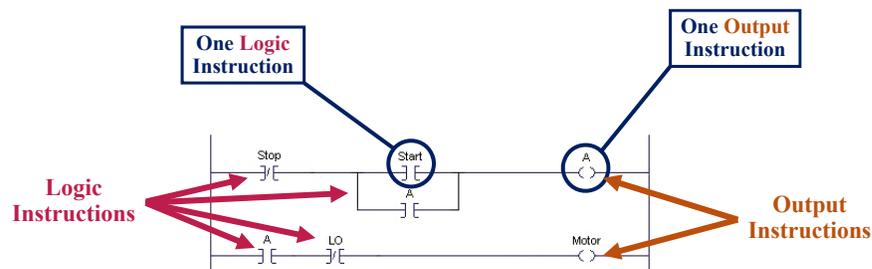
# Ladder Logic Instructions

Ladder Logic Instructions can be separated into two primary categories:

- **Output Instructions**
- **Logic (Input) Instructions**




# Output Instructions

Output Instructions perform a task.

The task performed may be simple or complex depending on the specific instruction, such as:

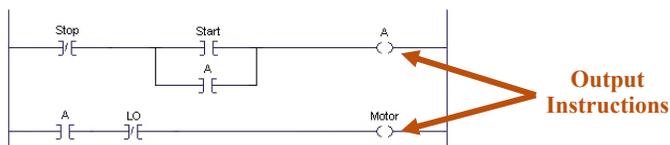- ✦ Changing the Value of a Number Stored in Memory
- ✦ Turning ON or OFF one of the PLC's Output Ports
- ✦ Operating as a Timer or a Counter
- ✦ Energizing or Changing the Output Frequency of a VFD





# Output Instructions

Output Instructions perform a task.

The task performed may be simple or complex depending on the specific instruction, such as:

- ✦ Changing the Value of a Number Stored in Memory
- ✦ Turning ON or OFF one of the PLC's Output Ports
- ✦ Operating as a Timer or a Counter
- ✦ Energizing or Changing the Output Frequency of a VFD



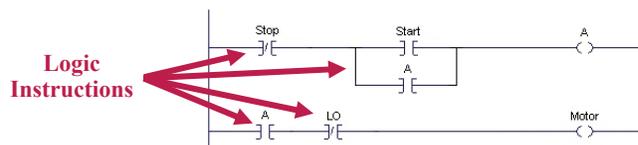
# Logic Instructions

Logic Instructions provide the functional logic that controls the operation of the Output Instructions.



In general, the “associated parameters” are one or more values stored in specific memory locations that are directly linked to a specific logic instruction.





## Rung Requirements

Each rung must have at least one **Output Instruction**.



Multiple **Output Instruction** may be placed in-series and/or in-parallel on the same rung.

Multiple **Logic Instructions** may be placed in-series and/or in-parallel on the same rung.

Each rung is not required to have any **Logic Instructions**.

\* – If multiple **Output Instructions** are placed on the same rung, **Logic Instructions** may be placed between those instructions provided that the right-most position on the rung is occupied by an **Output Instruction**. Note that rungs configured in this manner will not be covered in this presentation.



## Rung Condition


Rung Condition is a TRUE/FALSE logic state that is based on the state and placement of a rung's **Logic Instructions** and whether or not those instructions provide at least one path through **Logic Instructions** that are all **TRUE**, beginning from the left side-rail and progressing to the right.





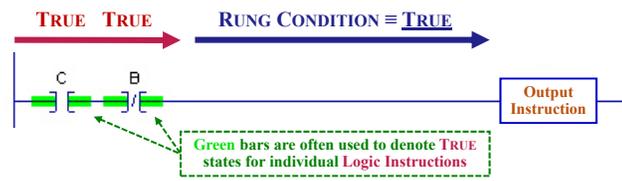
## TRUE Rung Condition

An **Output Instruction** experiences a **TRUE Rung Condition** when the rung's **Logic Instructions** provide a “**TRUE path**” from the left-hand side-rail of the ladder to the left side of the **Output Instruction**.


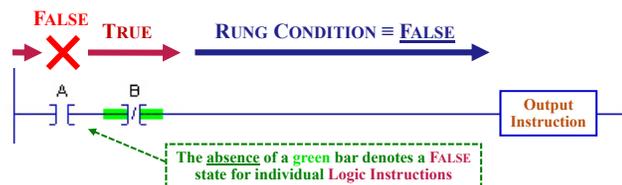
## FALSE Rung Condition


An **Output Instruction** experiences a **FALSE Rung Condition** when the rung's **Logic Instructions** prevent a “**TRUE path**” from the left-hand side-rail of the ladder to the left side of the **Output Instruction**.





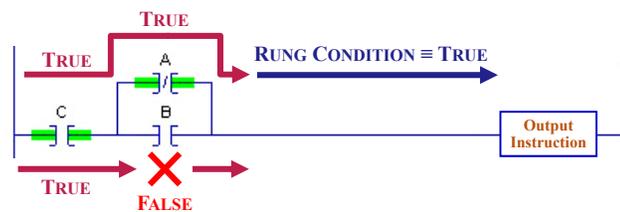
## Rung Condition

Note that the **Logic Instructions** placed on a rung may offer more than one potential path from the left-hand rail to an **Output Instruction**.


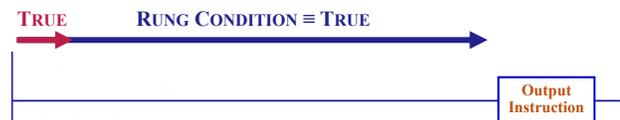
## Empty Rung Condition

When determining the **Rung Condition**, a rung is assumed to begin with a **TRUE** logic state at the left side-rail.





## Rung Condition Evaluation Order

**Rung Condition** is not affected by an **Output Instruction** when progressing from left-to-right across a specific rung.

Thus, if a rung contains multiple **Output Instructions**, then:

- the **Rung Condition** for the left-most **Output Instruction** is determined first and the operation that instruction is completed, after which
- the process repeats for each additional **Output Instruction** on the rung until the right side-rail is reached.



## Rung Condition Evaluation Order

Even if the operation of an **Output Instruction** would change the state of the previously-evaluated **Logic Instructions**, those **Logic Instructions** will not be re-evaluated and the previously-determined **Rung Condition** (to the left) will remain unchanged until the next time the rung is executed.

On the other hand, an **Output Instruction** may affect the state of any **Logic Instructions** that are placed to its right on a rung, in-turn possibly affecting the **Rung Condition** that is experienced by any additional **Output Instructions** that are also placed to its right\*.


\* – This is a complex situation that will not be covered in this presentation.


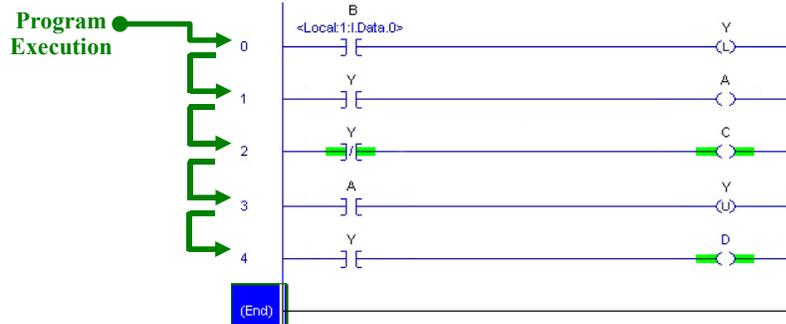
# Ladder Logic Program Execution




\* – The PLC has two primary modes of operation, PROGRAM and RUN. When switched to PROGRAM mode, the controller stops executing its Ladder Logic program.


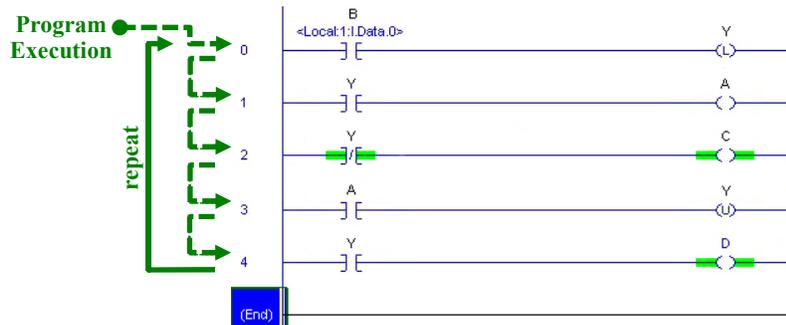
# Ladder Logic Program Execution

When the controller reaches the End rung, it jumps back to the top of the ladder (Rung 0) and the process begins again.

The controller will repetitively keep stepping through the ladder as long as the PLC remains in RUN mode.





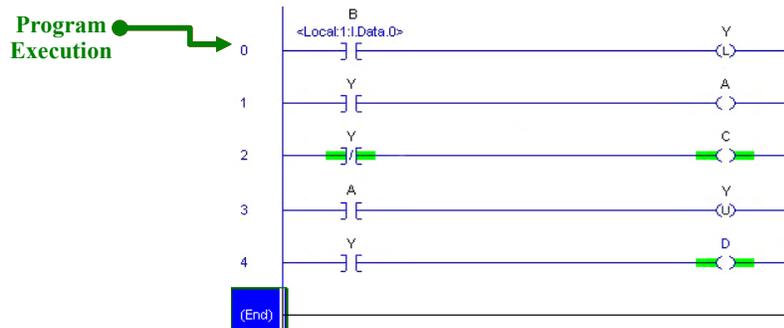
# Individual Rung Execution


Thus, beginning with Rung 0, the controller:

- Determines the **Rung-Condition** based on the state of the rung's **Logic Instructions**, and
- Completes any required tasks based on the **Rung-Condition** and the **Output Instruction(s)** on that rung.


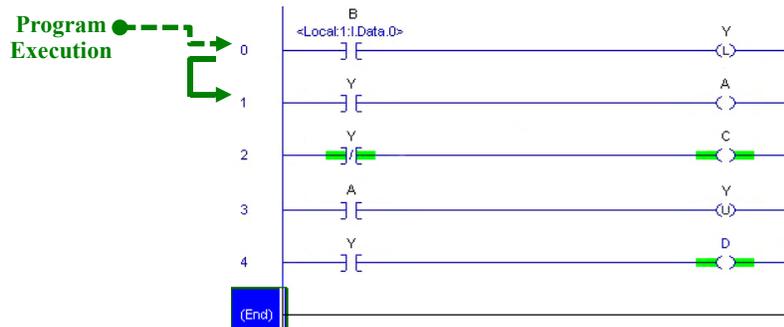
# Ladder Diagram Order of Execution

Once the controller completes the execution of a rung, it then moves to and executes the next rung by determining the **Rung Condition** on that rung and then applying the results to that rung's **Output Instruction(s)**.





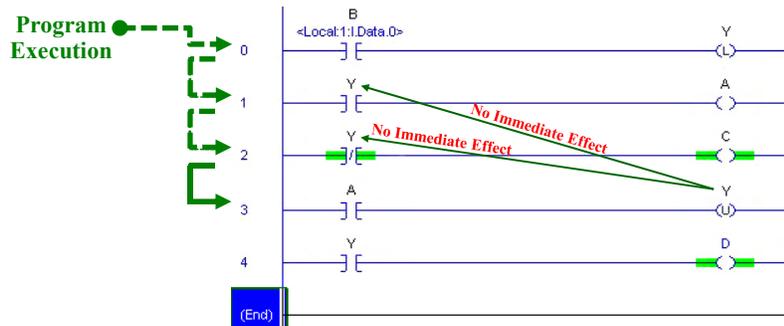
# Ladder Diagram Order of Execution


Although the execution of a rung may affect the state of the **Logic Instructions** on any previously-executed rungs, those changes are not acted upon until those rungs are re-executed.

I.e. – Once executed, a rung will not be re-evaluated until after the entire ladder has been executed and the controller sequentially steps through to that rung again.




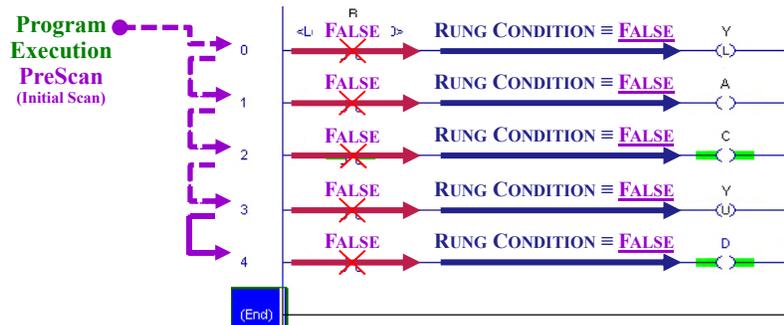
# PRESCAN Mode

Note that, if the PLC transitions from PROGRAM → RUN mode or if the PLC powers up in RUN mode, the **first (initial) scan** of the ladder diagram is executed in **PRESCAN** mode, during which all **Logic Instructions** return a **FALSE** state, in-turn resulting in all **FALSE Rung Conditions**.





## PRESCAN Mode

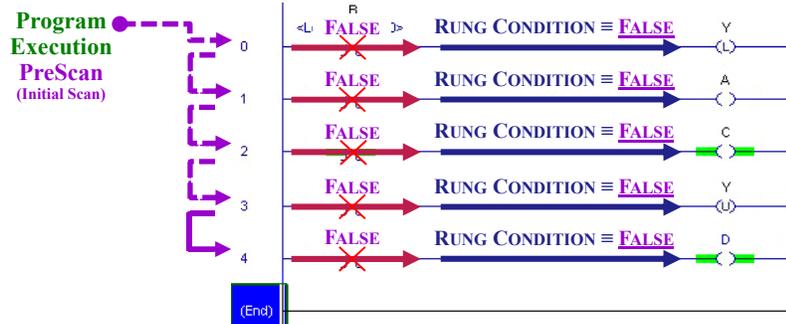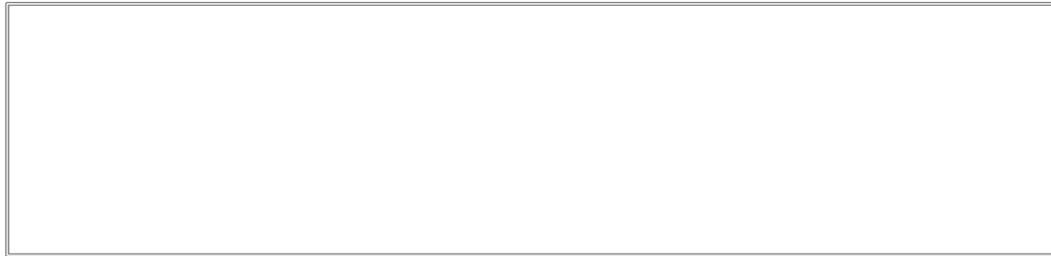

## Ladder Logic Instructions

Thus, the operation of the following three, commonly used, Ladder Logic Instructions will now be presented:

- | | the **Examine if Closed (XIC)** instruction,
- |/| the **Examine if Open (XIO)** instruction, and
- ( ) the **Output Energize (OTE)** instruction.

Note – an analogy is often made between the look/operation of these instructions and that of a relay's Normally-Open (NO) contact, Normally-Closed (NC) contact, and Field Coil.

Although this analogy may be utilized during the associated lecture for this material, the analogy will NOT be discussed within this presentation because it can lead to several common misconceptions regarding their operation within a Ladder Diagram; instead, they will always be presented and discussed as “Instructions within a Ladder Logic Program”.



## Icons Used for Ladder Instructions


Note that the icon shown in this presentation for a various instruction will be the version displayed within the RSLogix (Allen-Bradley / Rockwell Software) environment.

Although other manufacturers (Siemens, Automation Direct, etc.) may use different icons, the overall operation of the various instructions should be consistent across all of the platforms.


Shown below are some of the various Icons utilized for an “On-Delay Timer” in a Ladder Diagram:



RSLogix (Allen-Bradley)

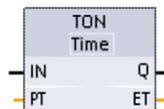

Siemens

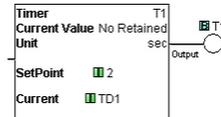

Automation Direct

## Logic Instructions – XIC

The **XIC (Examine If Closed)** instruction:



is a **Logic Instruction** that takes on either a **TRUE** or **FALSE** state depending on the value stored in a bit of memory.

But, in order to define the specific bit of memory upon which the **XIC**'s state is based, the **XIC** must be assigned a Tag.


An **XIC** is a Boolean instruction because it can only take on one of two states, **TRUE** or **FALSE**.


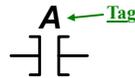
## Tags

**Tags** contain information that identifies and characterizes data stored in memory, allowing that data to be linked to the operation of one or more specific instructions.

For example, if the following **XIC** is assigned tag “A”:



The tag is displayed immediately above the icon for the instruction.

then Tag “A” identifies a specific bit in memory upon which this **XIC**’s state is based.

Tag “A” is a **Boolean** tag because it addresses a single bit that can only take on one of two values, **0** or **1**.



## Logic Instructions – XIC

If tag “A” is assigned to the **XIC** (**Examine If Closed**) instruction:



then the logic state (**TRUE** or **FALSE**) of that instruction is defined as follows:

When evaluated:  
(by the controller)

If bit A=1, then **XIC-A** → **TRUE**

If bit A=0, then **XIC-A** → **FALSE**

The XIC is TRUE when A=1.





## Instructions – Icons vs. Current State

For example, given the bit values: **A = 0 B = 0 C = 1**  
and the following rungs:



If displayed while the PLC is in **RUN** mode, then:

Rung-0: **XIC-A → FALSE, XIO-B → TRUE**  
Rung-1: **XIC-C → TRUE, XIO-C → FALSE**



## Output Instructions – OTE

The following **Output Instruction** is an **OTE (Output Energize)** instruction and it has been assigned tag “C”:



An **OTE** will either set or reset (store a 1 or 0 in) the bit identified by its assigned tag based on the **Rung Condition** as follows:

If the **Rung Condition** is **TRUE**, then **OTE-C** sets bit C → 1  
(when evaluated by the controller)

If the **Rung Condition** is **FALSE**, then **OTE-C** resets bit C → 0


If a bit is “set”, it is changed to a one (1).  
If a bit is “reset”, it is changed to a zero (0).


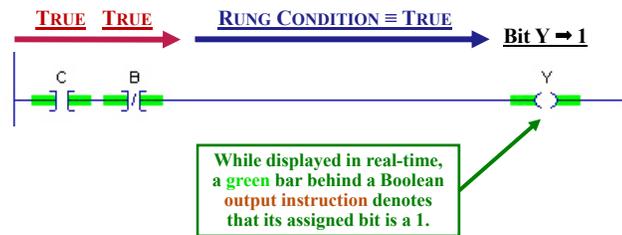
## OPE – TRUE Rung Condition

If the **Rung-Condition** for an **OPE** is **TRUE**, then the OPE will set its assigned bit to 1.

Thus, given the bit values:  $A = 0$   $B = 0$   $C = 1$   
when the following rung is executed, both **XIC-C** and **XIO-B** will be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, in-turn causing the OPE to set bit  $Y \rightarrow 1$ .



## OPE – FALSE Rung Condition

If the **Rung-Condition** for an **OPE** is **FALSE**, then the OPE will reset its assigned bit to 0.

Thus, given the bit values:  $A = 0$   $B = 0$   $C = 1$   
when the following rung is executed, both **XIC-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**, in-turn causing the OPE to reset bit  $X \rightarrow 0$ .





Part 1 of Hold-In Example

## OTE with Hold-In Example (Part 1)

Look closely at the following rung from a ladder diagram:



If bits A, B, and C are all zero ( $A=B=C=0$ ) when the rung is executed, **XIC-B** and **XIC-C** will both be evaluated **FALSE**, resulting in a **FALSE Rung Condition**.

Since bit C was already a 0, it isn't changed.

Since the **Rung Condition** is **FALSE**, **OTE-C** resets bit C  $\rightarrow 0$ , and since bit C=0, the results will be the same the next time the rung is executed provided bit B remains zero ( $B=0$ ).



Part 2 of Hold-In Example

## OTE with Hold-In Example (Part 2)

Given the same rung, what if bit B changes to a one ( $B \rightarrow 1$ ) and then the rung is executed again (assuming  $A=C=0$ )?

Then, the next time the rung is executed, **XIO-A** and **XIC-B** will both be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, and...



since the **Rung Condition** is now **TRUE**, **OTE-C** sets bit C  $\rightarrow 1$ .



(continued on the next slide)



Part 2 of Hold-In Example (continued)

## OTE with Hold-In Example (Part 2)

Note that, although bit C is now one ( $C=1$ ), **XIC-C** is still shown to be **FALSE** (no green bar).



This is to highlight the fact that, once the state of a specific **Logic Instruction** is evaluated, it will not be re-evaluated until the rung is executed again.

But, once the rung is executed again, assuming that A and B remain unchanged, the rung will appear as:



Part 3 of Hold-In Example

## OTE with Hold-In Example (Part 3)

Now, given the current state of the rung ( $A=0, B=C=1$ ), what if bit B resets ( $B \rightarrow 0$ ) and then the rung is executed again?

Although **XIC-B** now evaluates **FALSE**, **XIO-A** and **XIC-C** still provide a **TRUE** path, maintaining the **TRUE Rung Condition**, and...



since the **Rung Condition** stays **TRUE**, **OTE-C** keeps bit C set.





Part 4 of Hold-In Example

## OTE with Hold-In Example (Part 4)

But, given the current state of the rung ( $A=B=0, C=1$ ), what if bit A changes to a one ( $A \rightarrow 1$ ) and the rung is executed again?

The next time the rung executes, **XIO-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**, and



since the **Rung Condition** is **FALSE**, **OTE-C** resets bit  $C \rightarrow 0$ .



(continued on the next slide)



Part 4 of Hold-In Example (continued)

## OTE with Hold-In Example (Part 4)

Note that, although C is now a zero ( $C=0$ ), **XIC-C** was still shown to be **TRUE** (with a **green bar**).



This is also to highlight that the state of the **Logic Instruction** is not re-evaluated until the rung is executed again.

But, if the rung is executed again and **XIC-C** is re-evaluated, the rung will appear as (assuming A and B remain unchanged):





Part 5 of Hold-In Example

## OTE with Hold-In Example (Part 5)

And finally, what if bit A resets ( $A \rightarrow 0$ ) before the rung executes again?

The next time the rung executes, **XIO-A** will be evaluated **TRUE**, but the **Rung Condition** will remain **FALSE**.




Thus, the rung is back to the same overall state at that existed at the beginning of this example.



Analysis of Hold-In Example
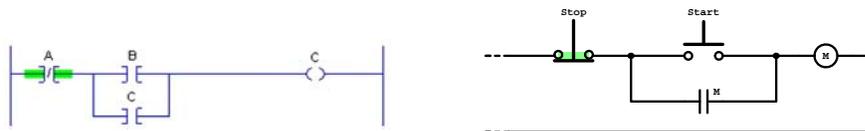
## OTE with Hold-In Example (Analysis)

Does the operation of the rung in this example remind you of the operation of a basic stop-start motor controller?



This rung-structure is often used in a PLC-based control system for which a “hold-in” function is required.

The trick is to somehow associate the value of bit A with the state of a “Stop” button, the value of bit B with the state of a “Start” button, and the value of bit C with the state of a contactor’s field coil.

How this is done will be discussed in Part B of this presentation.





## OTL Example

Given the following rung that contains an OTL (Output Latch):



If bit A changes to a one ( $A=1$ ) before the rung executes, then when the rung is executed, **XIC-A** will be evaluated **TRUE**, resulting in a **TRUE Rung Condition**.



Since the **Rung Condition is TRUE**, **OTL-B** sets bit  $B \rightarrow 1$ .



## OTL Example

On the other hand, given the following rung:



If bit A resets ( $A=0$ ) before the rung executes, then when the rung is executed, **XIC-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**.



But, **OTL-B** does nothing when the **Rung Condition is FALSE**, so bit B remains set ( $B=1$ ).




# Output Unlatch (OTU)
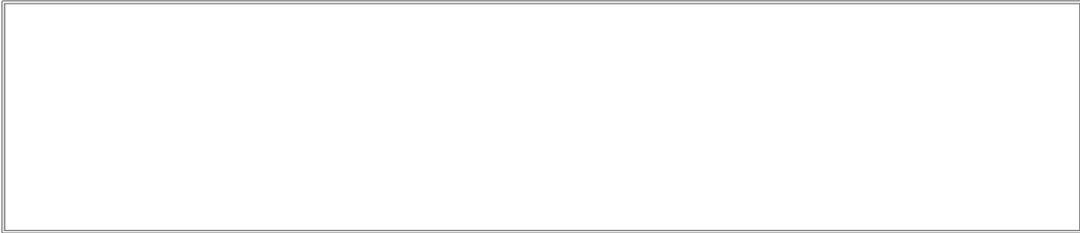
## OTU – Output Unlatch

$\overset{B}{-(U)-}$

An Output Unlatch (OTU) is an **Output Instruction** that can reset a bit (B → 0), but cannot set a bit to a one.



\* – Note that the **OTU** resets a bit when the **Rung Condition** becomes **TRUE**. On the other hand, an **OPE** resets a bit when the **Rung Condition** becomes **FALSE**. This is a critical distinction between the abilities of OTUs and OPEs to reset a bit, and often provides a challenge for beginning Ladder Logic programmers.



## OTU Example

Given a rung that contains one **OTU (Output Unlatch)** (A=0, B=1):



If bit A changes to a one (A=1), then the next time that the rung is executed, **XIC-A** will be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, and



since the **Rung Condition** is **TRUE**, **OTU-B** resets bit B → 0.





## OTU Example

Given the same rung when  $A=1$  and  $B=0$ :



If bit A resets ( $A=0$ ), then the next time that the rung is executed, **XIC-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**.




But, **OTU-B** does nothing when the **Rung Condition** is **FALSE**, so bit B remains reset ( $B=0$ ).




## On-Delay Timer (TON)

**TON** – On-Delay Timer

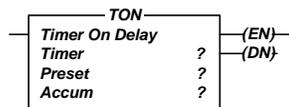

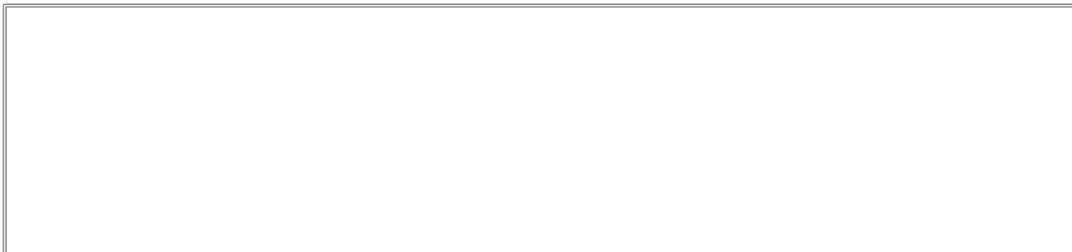
The **On-Delay Timer (TON)** is an **Output Instruction** that functions as a “non-retentive” timer.





## TON – Base Tag & Sub-Tags

### TON – On-Delay Timer

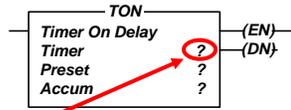

When a **Base Tag** is created for the **TON**, the name of which appears in the *Timer* field, several **sub-Tags** are automatically created by the RSLogix software:


The sub-Tags include:

*Base\_Tag.PRE*      *Base\_Tag.EN*      *Base\_Tag.TT*  
*Base\_Tag.ACC*      *Base\_Tag.DN*



## TON – Preset & Accumulator

### TON – On-Delay Timer

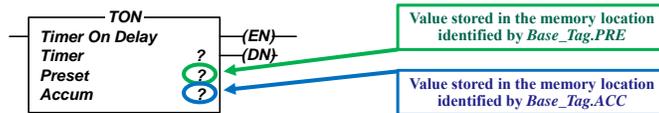

In addition to the *Timer* field that contains the Base Tag name, there are two user-defined fields shown in the icon:


- **Preset** – Contains the time-delay value (specified in msec) **(.PRE)** up to which the **TON** will count.
- **Accum** – Contains the initial time value (also in msec). **(.ACC)**

Note that the *Accum* field displays the current value stored in the accumulator when viewed “online” (in real time).



# TON – Operational State Bits

## TON – On-Delay Timer

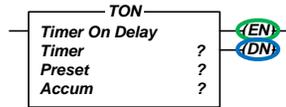

The *.TT* bit is not shown on the TON icon


Three sub-Tags characterize the **TON's** operational state:

- *Base\_Tag.EN* – The *.EN (Enable)* bit is set to 1 when the **TON** is enabled, and reset to 0 when it's disabled.
- *Base\_Tag.DN* – The *.DN (Done)* bit is set to 1 when the *Accum* equals the *Preset*, otherwise it's reset to 0.
- *Base\_Tag.TT* – The *.TT (Time Transitioning)* bit is set to 1 when the **TON** is actively counting, otherwise it's reset to 0.



# TON – Documentation

## TON – On-Delay Timer

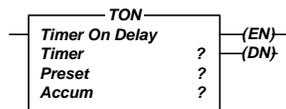


The following information can be found by using the Help tab within the RSLogix 5000 software:

Instruction:	Relay Ladder:	Function Block:	Structured Text:	Description:
TON Timer On Delay		see TONR	see TONR	The TON instruction is a non-retentive timer that accumulates time when the instruction is enabled (rung-condition-in is true).
<b>Operand:</b>	<b>Type:</b>	<b>Format:</b>	<b>Description:</b>	
Timer	TIMER	tag	timer structure	
Preset	DINT	immediate	how long to delay (accumulate time)	
Accum	DINT	immediate	number of msec the timer has counted; initial value is typically 0	
<b>Arithmetic Status Flags:</b>	<b>Major Faults:</b>			
not affected	Type 4	Code 34	• PRE < 0 • ACC < 0	



## TON – Detailed Operation

### TON – On-Delay Timer

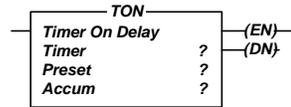


The **TON** is “enabled” when its **Rung Condition** is **TRUE**.

Once enabled, its *Enable* bit is set ( $.EN \rightarrow 1$ ) and the **TON** begins “actively” counting (accumulating time).



## TON – Detailed Operation

### TON – On-Delay Timer

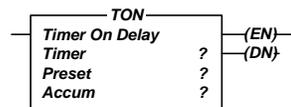

As long as the **TON** remains enabled, its accumulator will continue incrementing until it reaches the *Preset* value.


Note that, while the **TON** is “actively” accumulating time, the *Time Transitioning* bit will be set ( $.TT \rightarrow 1$ ).

But, if the **TON** is not accumulating time, either because it’s disabled or its accumulator has reached the *Preset* value, then the *.TT* bit will be reset ( $.TT \rightarrow 0$ ).



# TON – Detailed Operation

## TON – On-Delay Timer

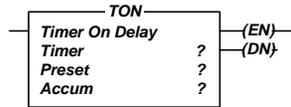

Once the **TON's** accumulator reaches the Preset value, it will stop incrementing and the *Accum* value will remain equal to the *Preset* value as long as the timer is enabled.


Additionally, as long as  $.ACC = .PRE$ , the timer's *Done* bit will be set ( $.DN \rightarrow 1$ ).

But, if for any reason  $.ACC \neq .PRE$ , such as the timer being disabled or reset, the *Done* bit will be reset ( $.DN \rightarrow 0$ ).


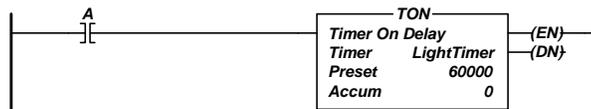
# TON Example

Given the **TON** that has been placed on a rung with **XIC-A**:



If the timer is configured as follows:

- the name of the Base Tag is “LightTimer”,
- the *Preset* value is 60,000 (60,000 msec = 60 sec), and
- the initial *Accum* value is 0.


describe, in detail:

- 1) the timer's initial conditions while bit A = 0,
- 2) the operation of the timer when bit A is set ( $A \rightarrow 1$ ), and
- 3) the operation of the timer if bit A is reset ( $A \rightarrow 0$ ).


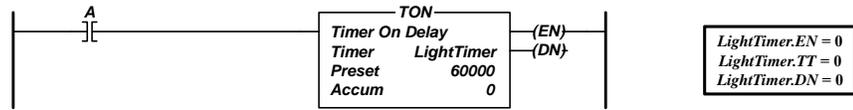
## TON Example – Initial Conditions

Given the **TON** that has been placed on a rung with **XIC-A**:



If bit **A** is initially zero ( $A=0$ ), then:

- both **XIC-A** and the **Rung Condition** will be **FALSE**, and
- the **TON** will be disabled.


Since the timer is disabled:

- the status bits, *Enable*, *Time Transitioning*, and *Done*, will all be **zero** ( $.EN=0, .TT=0, .DN=0$ ), and
- the accumulator value will remain at **zero** ( $.ACC=0$ ).


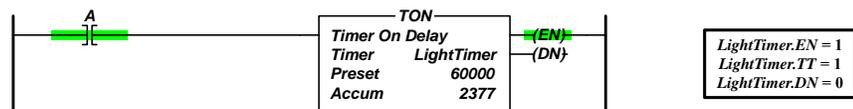
## TON Example – Timer Enabled

Given the **TON** that has been placed on a rung with **XIC-A**:



If bit **A**  $\rightarrow$  1, then the next time the rung is executed, **XIC-A** will be evaluated **TRUE**, making the **Rung Condition TRUE**, and the **TON** will be **enabled**.


When the **timer is enabled**:

- the *Enable* bit will be **set** ( $.EN \rightarrow 1$ ),
- the accumulator will begin **incrementing**, and
- the *Time Transitioning* bit will be **set** ( $.TT \rightarrow 1$ ).


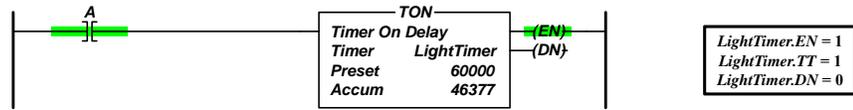
## TON Example – Time Transitioning

Given the **TON** that has been placed on a rung with **XIC-A**:




As long as the **TON** remains enabled and the *Accum* value is less than the *Preset* value ( $.ACC < 60,000$ ), then accumulator will keep incrementing until it reaches the *Preset* value.

Thus, while the accumulator is incrementing:

- the *Enable* bit will remain set ( $.EN = 1$ ), and
- the *Time Transitioning* bit will remain set ( $.TT = 1$ ).
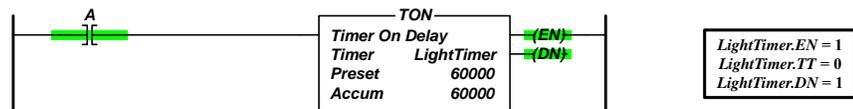
## TON Example – Timer Done

Given the **TON** that has been placed on a rung with **XIC-A**:



When the *Accum* value reaches the *Preset* value ( $.ACC = 60,000$ ), which will occur 60 seconds after the timer is enabled:


- the accumulator stops incrementing and remains at 60,000,
- the *Enable* bit will remain set ( $.EN = 1$ ),
- the *Time Transitioning* bit will reset ( $.TT \rightarrow 0$ ), and
- the *Done* bit will be set ( $.DN \rightarrow 1$ ).




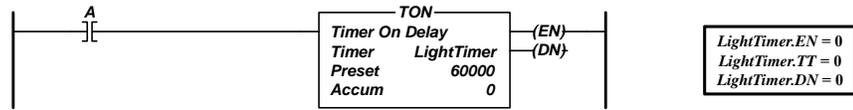
## TON Example – Timer Done

Given the **TON** that has been placed on a rung with **XIC-A**:



At any point in time, if bit  $A \rightarrow 0$ , then the next time the rung is executed, **XIC-A** will be evaluated **FALSE**, making the **Rung Condition FALSE**, and the **TON** will be disabled.

If the timer is disabled:

- the *Enable* bit will be reset ( $.EN \rightarrow 0$ ),
- the accumulator will reset back to its initial value,
- the *Done* bit will be reset ( $.DN \rightarrow 0$ ), and
- the *Time Transitioning* bit will be reset ( $.TT \rightarrow 0$ ) if it was set.



## Reset (RES)

**RES – Reset**



The Reset instruction is an **Output Instruction** that can be used to reset the accumulator (**.ACC**) and the status bits (**.EN**, **.DN**, etc.) of a timer or counter.

The Base Tag (name) associated with either the timer or counter that the **RES** instruction is being used to reset must be placed in the **Reset's tag field**.

For example, a **RES** instruction could be used to reset **LightTimer's** accumulator if assigned the tag **LightTimer**.



## RES – Operation

### RES – Reset



The operation of the **Reset** instruction is based upon the **Rung Condition** on the rung.


When the rung is executed:

If the **Rung Condition** is **TRUE**, the **RES** will reset the accumulator of its associated timer (counter) back to its initial value, but



## RES – Operation

### RES – Reset

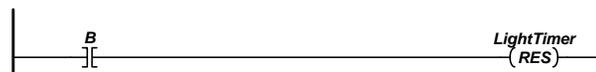


Note that:

Although a **RES** instruction does not technically disable a timer (counter) since the timer's rung-condition is not affected when the timer is reset, it causes roughly the same effect as the timer being instantaneously disabled and then re-enabled during its next scan.


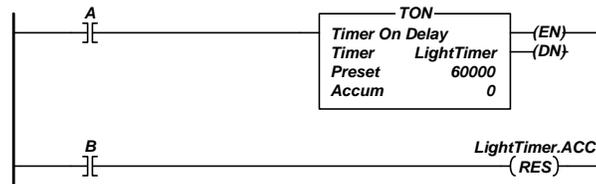
## RES Example (with TON)

Given the following rungs that contain a **TON** and a **RES**:




both of which are in the initial state shown in the figure.

If bits A and B are both zero ( $A=B=0$ ), in-turn making the Rung Conditions for both rungs **FALSE**, then the timer is disabled and the **Reset** instruction does nothing.


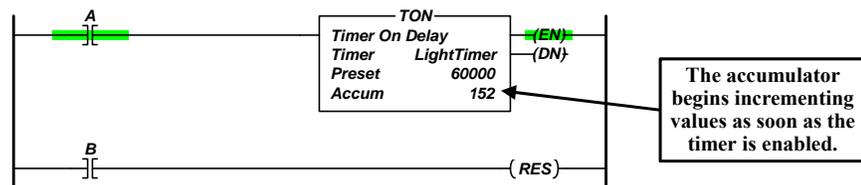
## RES Example – TON Enabled

Given the following rungs that contain a **TON** and a **RES**:




- If bit A  $\rightarrow$  1  $\Rightarrow$  **XIC-A  $\equiv$  TRUE**
- $\Rightarrow$  the Rung Condition for the 1<sup>st</sup> rung is **TRUE**
  - $\Rightarrow$  **TON-LightTimer** is enabled
  - $\Rightarrow$  the *Enable* bit is set ( $.EN \rightarrow 1$ )
  - $\Rightarrow$  the timer's accumulator begins incrementing
  - $\Rightarrow$  the *Time Transitioning* bit is set ( $.TT \rightarrow 1$ )


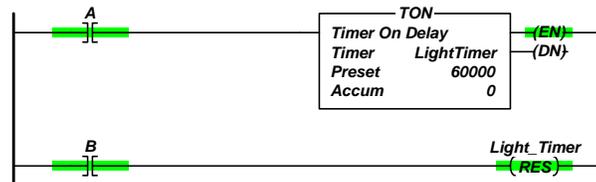
## RES Example – TON Reset

Given the following rungs that contain a **TON** and a **RES**:




- If bit B → 1
- ⇒ **XIC-B** ≡ **TRUE**
  - ⇒ the **Rung Condition** for the 2<sup>nd</sup> rung is **TRUE**
  - ⇒ **TON-LightTimer** resets **LightTimer's** accumulator to its initial value
  - ⇒ If the *Accum* was 60,000 (and *.DN*=1) when the timer was reset, the *Done* bit is reset (*.DN* → 0)


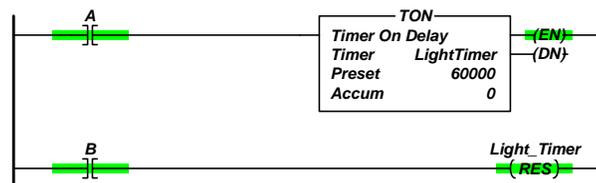
## RES Example – TON Reset

Given the following rungs that contain a **TON** and a **RES**:




If bit B remains set (B=1), then the **RES** will keep resetting the accumulator back to its initial value and it will appear as if the timer is disabled despite its **TRUE Rung Condition**.




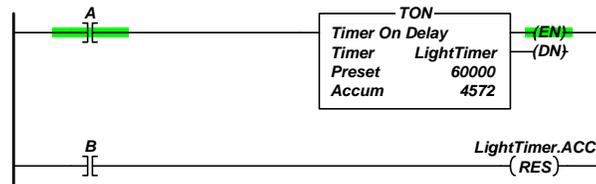
## RES Example – TON Reset

Given the following rungs that contain a **TON** and a **RES**:



But, if bit B is reset ( $B \rightarrow 0$ ) while **LightTimer** is still enabled, then the timer's accumulator will begin incrementing again until either it reaches the *Preset* value, the timer is reset again, or the timer is disabled.



## Numerical Comparison Instructions

There are many **Logic Instructions** available the return either TRUE or FALSE states based on a comparison of two values.

These instructions include:


- **GRT** – Greater Than
- **GEQ** – Greater Than or Equal To
- **LES** – Less Than
- **LEQ** – Less Than or Equal To
- **EQU** – Equal To
- **NEQ** – Not Equal To

Only the **Greater Than (GRT)** instruction is covered in this presentation since the other comparison-type instructions function similarly.



# Greater Than (GRT)

## GRT – Greater Than

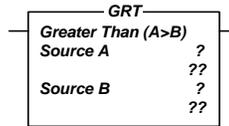


The **GRT (Greater Than)** instruction is used to compare the values of two numbers, A and B.

- If  $A > B$ , then the **GRT** returns a TRUE state.
- If  $A \leq B$ , then the **GRT** returns a FALSE state.



# GRT – Configuration

## GRT – Greater Than

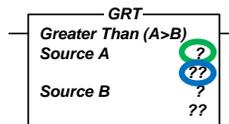


The **GRT (Greater Than)** instruction is used to compare the values of two numbers, A and B.

- Source A – This field contains either the numerical value of A or the tag name relating to the data that contains the value of A.
- If the Source A field contains a tag name, the second field shows the value currently stored in that Tag.



## GRT – Configuration

### GRT – Greater Than

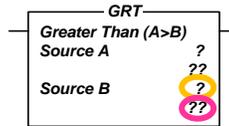


The **GRT** (**Greater Than**) instruction is used to compare the values of two numbers, A and B.

- Source B – This field contains either the numerical value of A or the tag name relating to the data that contains the value of B.
- If the Source B field contains a tag name, the second field shows the value currently stored in that Tag.


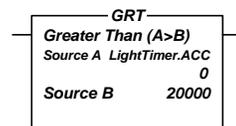
## GRT Example

The **GRT** shown above is configured to compare the current value stored in **LightTimer's** accumulator to 20,000.



When evaluated:


The **GRT** return a TRUE state whenever *LightTimer.ACC* is greater than 20000, and

The **GRT** return a FALSE state whenever *LightTimer.ACC* is less than 20000.




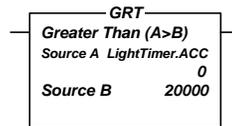
## GRT Example

The **GRT** shown above is configured to compare the current value stored in **LightTimer's** accumulator to 20,000.




Thus:

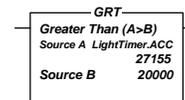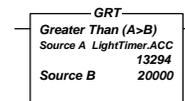- While *LightTimer.ACC* is < 20000, the **GRT** returns a FALSE LOGIC state.
- While *LightTimer.ACC* is > 20000, the **GRT** returns a TRUE logic state.



## Other Instructions – Counter Up (CTU)

The **CTU (Counter Up)** is an **Output Instruction** whose function is similar to that of the On-Delay Timer:

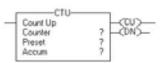Instruction:	Relay Ladder:	Function Block:	Structured Text:	Description:
CTU Counter Up		see CTUD	see CTUD	The CTU instruction counts upward.
<b>Operand:</b>	<b>Type:</b>	<b>Format:</b>	<b>Description:</b>	
Counter	COUNTER	tag	counter structure	
Preset	DINT	immediate	how high to count	
Accum	DINT	immediate	number of times the counter has counted; initial value is typically 0	
<b>Arithmetic Status Flags:</b>	<b>Major Faults:</b>			
not affected	none			

The Counter Up (CTU) is useful for keeping track of the number of specific events that occur, such as the number of items passing by an optical detector.

When the CTU's rung-condition becomes TRUE, the CTU's accumulator is incremented by one (1).

Note that, for the CTU to count up again, the CTU's rung-condition must first become FALSE and then TRUE again.