



ECET 3000

*Electrical
Principles*

Complex Power




AC Power – General Case

As previously stated, the **general expression** for the **power** produced by an AC source is:

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= V_{peak} \cdot I_{peak} \cdot \sin(\omega \cdot t + \phi) \cdot \sin(\omega \cdot t + \delta) \end{aligned}$$

where: $v(t) = V_{peak} \cdot \sin(\omega \cdot t + \phi)$
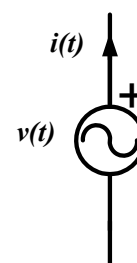
$$i(t) = I_{peak} \cdot \sin(\omega \cdot t + \delta)$$






AC Power – General Case

If the voltages & currents are expressed in terms of their **RMS magnitudes**, the power expression becomes:

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= \sqrt{2} \cdot V \cdot \sqrt{2} \cdot I \cdot \sin(\omega \cdot t + \phi) \cdot \sin(\omega \cdot t + \delta) \\ &= 2 \cdot V \cdot I \cdot \sin(\omega \cdot t + \phi) \cdot \sin(\omega \cdot t + \delta) \end{aligned}$$

which may be modified using several trigonometric identities into the following form:
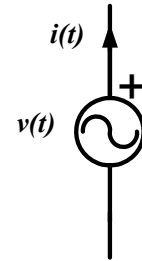
$$\begin{aligned} p(t) &= V \cdot I \cdot \cos(\phi - \delta) \\ &\quad - V \cdot I \cdot \cos(\phi - \delta) \cdot \cos(2 \cdot \omega \cdot t) \\ &\quad + V \cdot I \cdot \sin(\phi - \delta) \cdot \sin(2 \cdot \omega \cdot t) \end{aligned}$$




AC Power – General Case

The modified power expression is often simplified by defining a new variable, θ , where:

$$\theta = \phi - \delta$$

and substituting it into the equation, resulting in the **general power expression**:
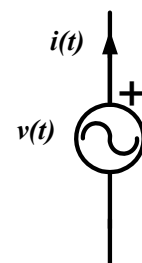
$$\begin{aligned} p(t) &= V \cdot I \cdot \cos(\theta) \\ &\quad - V \cdot I \cdot \cos(\theta) \cdot \cos(2 \cdot \omega \cdot t) \\ &\quad + V \cdot I \cdot \sin(\theta) \cdot \sin(2 \cdot \omega \cdot t) \end{aligned}$$





AC Power – General Case

The angle θ :


$$\theta = \phi - \delta$$

which is defined by the difference between the phase angles of the voltage and current,

$$v(t) = V_{peak} \cdot \sin(\omega \cdot t + \phi)$$

$$i(t) = I_{peak} \cdot \sin(\omega \cdot t + \delta)$$

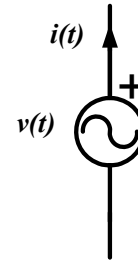is often referred to as the **power angle**:



AC Power and Sources


This general expression defines the instantaneous **power produced by an AC source**.

$$p(t) = V \cdot I \cdot \cos(\theta)$$

$$-V \cdot I \cdot \cos(\theta) \cdot \cos(2 \cdot \omega \cdot t)$$

$$+V \cdot I \cdot \sin(\theta) \cdot \sin(2 \cdot \omega \cdot t)$$

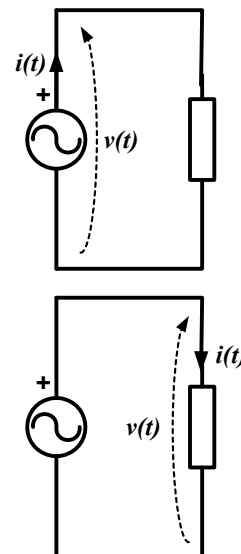Likewise, if the source is connected across a load that may have resistive, capacitive, and/or inductive components, then the solution also defines the instantaneous **power consumed by the AC supplied load**.





AC Power and Resistors

If an AC source is connected to a resistive load,


$$v_R(t) = \sqrt{2} \cdot V_R \cdot \sin(\omega \cdot t + \phi)$$

then the resistor current will be:

$$i_R(t) = \sqrt{2} \cdot \frac{V_R}{R} \cdot \sin(\omega \cdot t + \phi)$$

and the power consumed by the resistor will be:
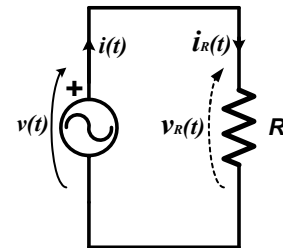
$$p_R(t) = V_R \cdot I_R - V_R \cdot I_R \cdot \cos(2 \cdot \omega \cdot t)$$




AC Power and Resistors


The resultant power waveform has two terms:

$$p_R(t) = \boxed{V_R \cdot I_R} - \boxed{V_R \cdot I_R \cdot \cos(2 \cdot \omega \cdot t)}$$

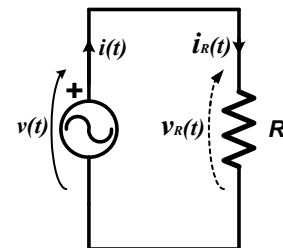- the first of which is a **constant** that provides the **average** power supplied to the resistor, which is defined to be **Real Power**, P_R , and
- the second of which is a **purely sinusoidal** term that has a **zero average** value and varies at 2x the frequency of the source voltage.


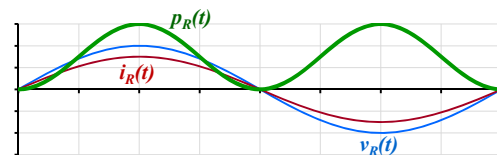
$$P_R = V_R \cdot I_R \quad \text{Watts}$$





AC Power and Inductors

If the AC source is connected to an inductive load,


$$v_L(t) = \sqrt{2} \cdot V_L \cdot \sin(\omega \cdot t + \phi)$$

then the inductor current will be:

$$i_L(t) = \sqrt{2} \cdot \frac{V_L}{\omega \cdot L} \cdot \sin(\omega \cdot t + \phi^\circ - 90^\circ)$$

and the power consumed by the inductor will be:
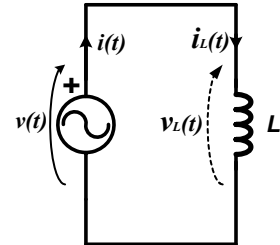
$$p_L(t) = V_L \cdot I_L \cdot \sin(2 \cdot \omega \cdot t)$$



AC Power and Inductors

The resultant power waveform has only one term:



$$p_L(t) = V_L \cdot I_L \cdot \sin(2 \cdot \omega \cdot t)$$

which is a **purely sinusoidal** term that has a **zero average (real power)** value and varies at twice (2x) the frequency of the source voltage.

Although the inductor consumes zero **real power**:

$$P_L = 0 \text{ Watts}$$

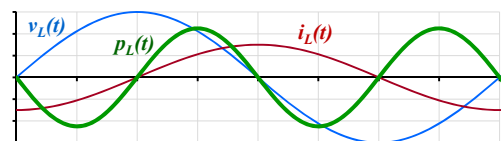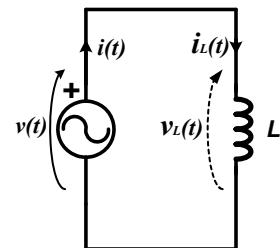power is instantaneously flowing into and out of the inductor.





AC Power and Capacitors

If the AC source is connected to an capacitor load,


$$v_C(t) = \sqrt{2} \cdot V_C \cdot \sin(\omega \cdot t + \phi)$$

then the capacitor current will be:

$$i_C(t) = \sqrt{2} \cdot V_C \cdot \omega \cdot C \cdot \sin(\omega \cdot t + \phi^\circ + 90^\circ)$$

and the power consumed by the capacitor will be:
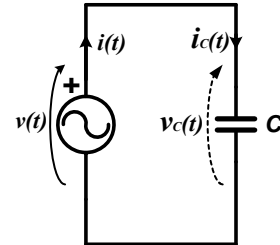
$$p_C(t) = -V_C \cdot I_C \cdot \sin(2 \cdot \omega \cdot t)$$



AC Power and Capacitors

The resultant power waveform has only one term:



$$p_C(t) = -V_C \cdot I_C \cdot \sin(2 \cdot \omega \cdot t)$$

which is a **purely sinusoidal** term that has a **zero average (real power)** value and varies at twice (2x) the frequency of the source voltage.

Although the capacitor consumes zero **real power**:

$$P_C = 0 \text{ Watts}$$

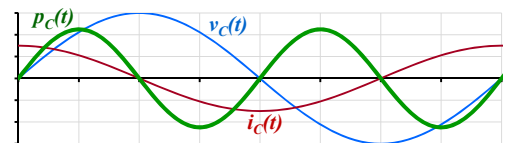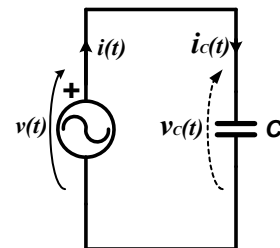power is instantaneously flowing into and out of the capacitor.







AC Power and Reactive Loads

Although the (average) **real power consumed by both inductors and capacitors is zero**, there is power flowing in and out of these elements when supplied by an AC source:

$$p_L(t) = V_L \cdot I_L \cdot \sin(2 \cdot \omega \cdot t)$$

$$p_C(t) = -V_C \cdot I_C \cdot \sin(2 \cdot \omega \cdot t)$$

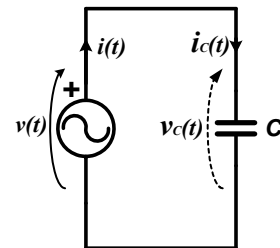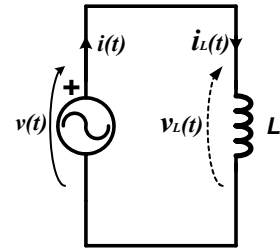The term **Reactive Power** is used to characterize the amount of energy that is being temporarily stored and then released by a “*reactive load*” (capacitive or inductive).



Reactive Power

Reactive Power (Q) is defined as the magnitude of the power that is flowing into and out of a reactive load when supplied by an AC source.



Thus, given: $p_L(t) = V_L \cdot I_L \cdot \sin(2 \cdot \omega \cdot t)$

$$p_C(t) = -V_C \cdot I_C \cdot \sin(2 \cdot \omega \cdot t)$$

the reactive power for the inductive and capacitive loads can be defined as:

$$Q_L = +V_L \cdot I_L \text{ Vars}$$

$$Q_C = -V_C \cdot I_C \text{ Vars}$$

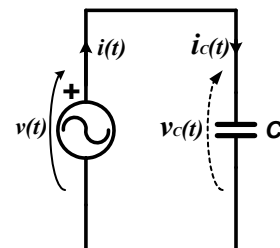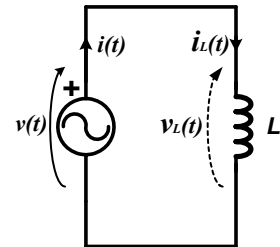



Reactive Power

Reactive Power is given the unit of “Vars”, which stands for:



“*Volt-Amps-Reactive*”.

$$Q_L = +V_L \cdot I_L \text{ Vars}$$

$$Q_C = -V_C \cdot I_C \text{ Vars}$$

Note that the reactive power for an inductor is **positive** while the reactive power for a capacitor is **negative**.

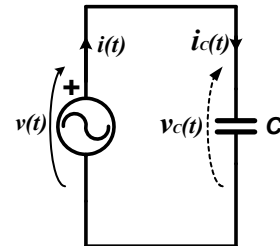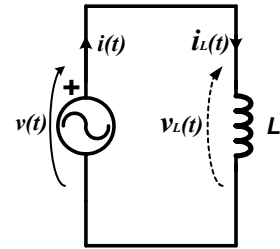Thus, it is often stated that an inductor “consumes” reactive power while a capacitor “produces” reactive power.



AC Power – General Case

If an AC source is connected to a complex impedance:


$$v(t) = \sqrt{2} \cdot V \cdot \sin(\omega \cdot t + \phi)$$

the resultant current can be expressed as:

$$i(t) = \sqrt{2} \cdot I \cdot \sin(\omega \cdot t + \delta)$$

and the power waveform as:
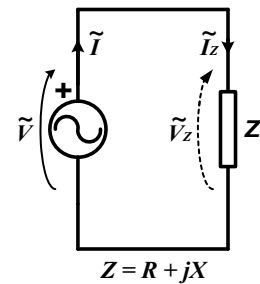
$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= 2 \cdot V \cdot I \cdot \sin(\omega \cdot t + \phi) \cdot \sin(\omega \cdot t + \delta) \end{aligned}$$






AC Power – General Case

The power expression:

$$p(t) = 2 \cdot V \cdot I \cdot \sin(\omega \cdot t + \phi) \cdot \sin(\omega \cdot t + \delta)$$

may be modified using several trigonometric identities into the following form:
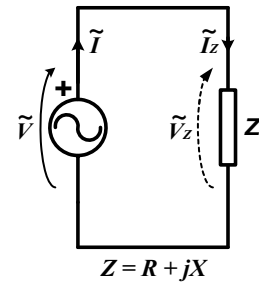
$$\begin{aligned} p(t) &= V \cdot I \cdot \cos(\phi - \delta) \\ &\quad - V \cdot I \cdot \cos(\phi - \delta) \cdot \cos(2 \cdot \omega \cdot t) \\ &\quad + V \cdot I \cdot \sin(\phi - \delta) \cdot \sin(2 \cdot \omega \cdot t) \end{aligned}$$



AC Power – General Case

The modified power expression is often simplified by defining a new variable, θ , often referred to as the “power angle”, where:


$$\theta = \angle \tilde{V} - \angle \tilde{I} = \phi - \delta$$

and substituting the variable into the equation:

$$\begin{aligned} p(t) &= V \cdot I \cdot \cos(\phi - \delta) \\ &\quad - V \cdot I \cdot \cos(\phi - \delta) \cdot \cos(2 \cdot \omega \cdot t) \\ &\quad + V \cdot I \cdot \sin(\phi - \delta) \cdot \sin(2 \cdot \omega \cdot t) \end{aligned}$$

Note that the angle θ is also equal to the angle of the impedance \mathbf{Z} when expressed in polar form.

$$\mathbf{Z} = R + jX = |Z| \angle \theta$$

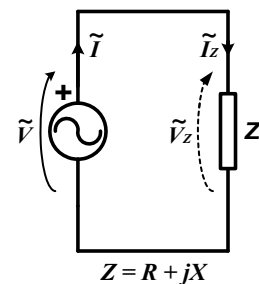




AC Power – General Case

The solution also provides both the instantaneous power produced by a source and the instantaneous power consumed by a load.
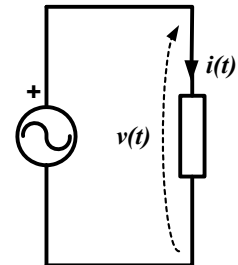
$$p(t) = \boxed{V \cdot I \cdot \cos(\theta)}$$
$$-V \cdot I \cdot \cos(\theta) \cdot \cos(2 \cdot \omega \cdot t)$$
$$+V \cdot I \cdot \sin(\theta) \cdot \sin(2 \cdot \omega \cdot t)$$



The first term is a **constant** that provides the average power or **Real Power** that is consumed by the resistive portion of the load:


$$P = V \cdot I \cdot \cos(\theta) \text{ Watts}$$



AC Power – General Case

The solution also provides both the instantaneous power produced by a source and the instantaneous power consumed by a load.
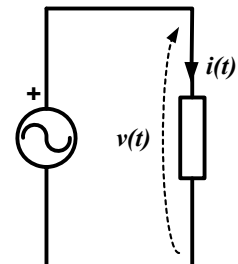
$$p(t) = V \cdot I \cdot \cos(\theta)$$
$$\boxed{-V \cdot I \cdot \cos(\theta) \cdot \cos(2 \cdot \omega \cdot t)}$$
$$+V \cdot I \cdot \sin(\theta) \cdot \sin(2 \cdot \omega \cdot t)$$



The second term is **purely sinusoidal** and provides the time-varying portion of the power that is consumed by the resistive portion of the load.




AC Power – General Case

The solution also provides both the instantaneous power produced by a source and the power consumed by a load.

$$\begin{aligned}
 p(t) &= V \cdot I \cdot \cos(\theta) \\
 &\quad - V \cdot I \cdot \cos(\theta) \cdot \cos(2 \cdot \omega \cdot t) \\
 &\quad + V \cdot I \cdot \sin(\theta) \cdot \sin(2 \cdot \omega \cdot t)
 \end{aligned}$$

The third term is also purely sinusoidal, the magnitude of which provides the **Reactive Power** consumed by the reactive portion of the load.
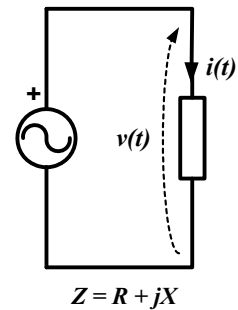
$$Q = V \cdot I \cdot \sin(\theta) \text{ Vars}$$



Complex Power


The term **Complex Power** is used to characterize both the Real Power and the Reactive Power in an AC system that is being supplied to a complex load impedance (that may have a resistive and/or a reactive component).

$$Z = R + jX$$

Complex Power (S) is a complex number and is defined by:

$$S = P + jQ$$

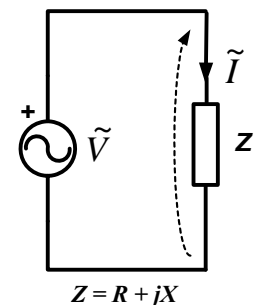where: P is Real Power, and
 Q is Reactive Power.






Complex Power

Complex Power (S):

$$S = P + jQ$$

may be solved directly from the applied phasor voltage and the resultant phasor current as:
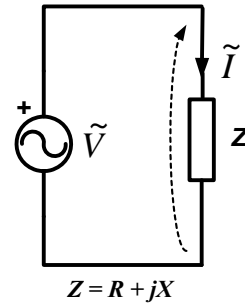
$$\begin{aligned}
 S &= \tilde{V} \cdot \tilde{I}^* \\
 &= (V \angle \phi) \cdot (I \angle -\delta) \\
 &= V \cdot I \angle (\phi - \delta) = V \cdot I \angle \theta \\
 &= V \cdot I \cdot \cos \theta + jV \cdot I \cdot \sin \theta \\
 &= P + jQ
 \end{aligned}$$




Complex Power

Note that \tilde{I}^* is the complex conjugate of \tilde{I} and is defined as:

$$\tilde{I}^* = (I \angle \delta)^* = (I \angle -\delta)$$

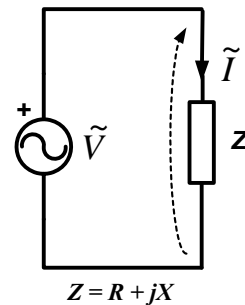In other words, the **complex conjugate** of a complex number in polar form has the same magnitude as the original number but its angle is negated.



For example, given the current:

$$\tilde{I} = 24 \angle 30^\circ \text{ amps}$$

The **complex conjugate** of the current, \tilde{I}^* , is:

$$\tilde{I}^* = (I \angle \delta)^* = (I \angle -\delta) = 24 \angle -30^\circ \text{ amps}$$



Apparent Power

Apparent Power ($|S|$) is defined to be the magnitude of complex power:

$$|S| = V \cdot I = \sqrt{P^2 + Q^2} \quad \text{VA}$$


Apparent power is often specified as part of the ratings of an electric machine, such that:

$$|S|_{\text{rated}} = V_{\text{rated}} \cdot I_{\text{rated}} \quad \text{VA}$$

Note that, given two of these rated values (voltage, current, apparent power), the third can be calculated from the above equation.

For example, given a **500VA** transformer whose primary winding is rated at **208V**, the **rated current** for the primary winding is:

$$I_{\text{rated}} = \frac{|S|_{\text{rated}}}{V_{\text{rated}}} = \frac{500 \text{ VA}}{208 \text{ V}} = 2.40 \text{ A}$$

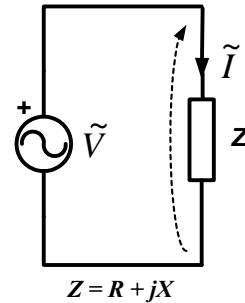

Power Factor


Power Factor (pf) is defined as the ratio of the real power over the apparent power:

$$pf = \frac{P}{|S|}$$

Thus, power factor may be solved as:

$$pf = \frac{P}{|S|} = \frac{V \cdot I \cdot \cos \theta}{V \cdot I} = \cos \theta$$

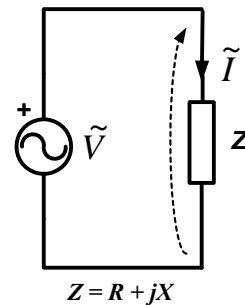Power Factor is often characterized by a qualifier, either **leading** or **lagging**, which is used to describe the phase angle relationship between the applied voltage and the resultant current waveforms.






Power Factor

A **leading** power factor exists when the current “leads” the voltage, which occurs when the load impedance has an overall **capacitive** aspect, resulting in a negative angle θ :

$$Z = R - jX_C \quad -90^\circ \leq \theta < 0^\circ$$

A **lagging** power factor exists when the current “lags” the voltage, which occurs when the load impedance has an overall **inductive** aspect, resulting in a positive angle difference for θ :
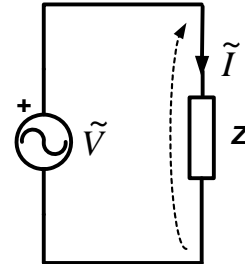
$$Z = R + jX_L \quad 0^\circ < \theta \leq +90^\circ$$



$$\tilde{V} = V \angle \phi^\circ$$

$$\tilde{I} = I \angle \delta^\circ$$

$$Z = R + jX = |Z| \angle \theta$$

$$\theta = \phi - \delta$$

Power Factor

Note that a **purely resistive load** results in a zero value for the angle θ , which is neither leading nor lagging.

$$Z = R \quad \theta = 0^\circ$$


This is often referred to as a **unity power factor** since the value of power factor under this condition equals one.

$$\cos(\theta) = \cos(0^\circ) = 1$$

Note that, in the case of a **purely resistive load**, **rated real power** may be specified in place of rated apparent power since, for a **purely resistive load**:

$$\theta = 0^\circ \Rightarrow P = V \cdot I \cdot \cos \theta = V \cdot I \cdot \cos 0^\circ = V \cdot I$$
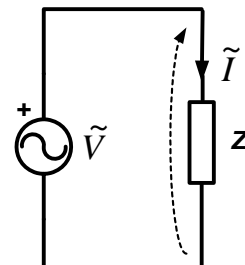
$$\therefore P_{rated} = V_{rated} \cdot I_{rated} \quad (\text{purely resistive loads only})$$



$$\tilde{V} = V \angle \phi^\circ$$

$$\tilde{I} = I \angle \delta^\circ$$

$$Z = R + jX = |Z| \angle \theta$$

$$\theta = \phi - \delta$$



Summary of Complex Power Equations

Complex Power (S): $S = \tilde{V} \cdot \tilde{I}^* = P + jQ$

Real Power (P): $P = V \cdot I \cdot \cos \theta$

Reactive Power (Q): $Q = V \cdot I \cdot \sin \theta$

Apparent Power ($|S|$): $|S| = V \cdot I = \sqrt{P^2 + Q^2}$

Power Factor (pf): $pf = \cos \theta$


Be careful using these equations

The formulas shown for **Real Power** and **Reactive Power** are often mistakenly applied. For that reason, I highly recommend calculating Complex Power whenever either Real or Reactive Power is required, and then:
 setting **Real Power** equal to the **real portion** of the **Complex Power**, and
 setting **Reactive Power** equal to the **imaginary portion** of the **Complex Power**.

$$S = P + jQ \quad \therefore \quad P = \text{Real}\{S\} \quad Q = \text{Imag}\{S\}$$


Complex Power

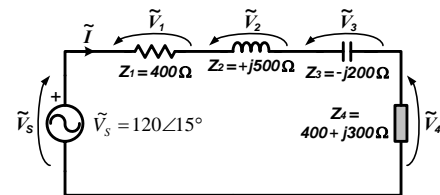Determine the **complex power** produced by the **source** in the following circuit:



$$\begin{aligned} Z_{eq} &= Z_1 + Z_2 + Z_3 + Z_4 \\ &= (400) + (+j500) + (-j200) + (400 + j300) \\ &= (800 + j600)\Omega \end{aligned}$$

$$\tilde{I} = \frac{\tilde{V}_s}{Z_{eq}} = \frac{120\angle 15^\circ}{800 + j600} = 0.12\angle -21.87^\circ \text{ amps}$$

The **apparent power** produced by the source is:
 $|S_S| = V_S \cdot I = (120) \cdot (0.12) = 14.4 \text{ VA}$

$$S_{Source} = \tilde{V}_s \cdot \tilde{I}^* = (120\angle 15^\circ) \cdot (0.12\angle +21.87^\circ) = 11.52 + j8.64$$

$$P_{Source} = 11.52 \text{ watts}$$

$$Q_{Source} = 8.64 \text{ VARs}$$



Complex Power

Determine the **complex power** consumed by loads Z_1 and Z_2 .

$$\begin{aligned}\tilde{V}_1 &= \tilde{I} \cdot Z_1 = (0.12 \angle -21.87^\circ) \cdot (400) \\ &= 48 \angle -21.87^\circ \text{ volts}\end{aligned}$$

$$\begin{aligned}S_1 &= \tilde{V}_1 \cdot \tilde{I}^* \\ &= (48 \angle -21.87^\circ) \cdot (0.12 \angle +21.87^\circ) \\ &= \boxed{5.76 + j0}\end{aligned}$$

$$P_1 = 5.76 \text{ watts}$$


$$Q_1 = 0 \text{ VARs}$$

$$\begin{aligned}\tilde{V}_2 &= \tilde{I} \cdot Z_2 = (0.12 \angle -21.87^\circ) \cdot (+j500) \\ &= 60 \angle 68.13^\circ \text{ volts}\end{aligned}$$

$$\begin{aligned}S_2 &= \tilde{V}_2 \cdot \tilde{I}^* \\ &= (60 \angle 68.13^\circ) \cdot (0.12 \angle +21.87^\circ) \\ &= \boxed{0 + j7.2}\end{aligned}$$

$$P_2 = 0 \text{ watts}$$

$$Q_2 = 7.2 \text{ VARs}$$

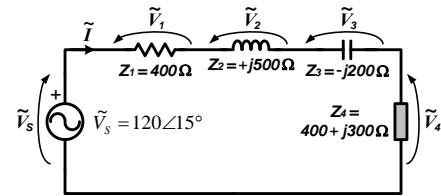

Complex Power

Determine the **complex power** consumed by loads Z_3 and Z_4 .

$$\begin{aligned}\tilde{V}_3 &= \tilde{I} \cdot Z_3 = (0.12 \angle -21.87^\circ) \cdot (-j200) \\ &= 24 \angle -111.87^\circ \text{ volts}\end{aligned}$$

$$\begin{aligned}S_3 &= \tilde{V}_3 \cdot \tilde{I}^* \\ &= (24 \angle -111.87^\circ) \cdot (0.12 \angle +21.87^\circ) \\ &= \boxed{0 - j2.88}\end{aligned}$$

$$P_3 = 0 \text{ watts}$$


$$Q_3 = 2.88 \text{ VARs}$$

$$\begin{aligned}\tilde{V}_4 &= \tilde{I} \cdot Z_4 \\ &= (0.12 \angle -21.87^\circ) \cdot (400 + j300) \\ &= 60 \angle 15^\circ \text{ volts}\end{aligned}$$

$$\begin{aligned}S_4 &= \tilde{V}_4 \cdot \tilde{I}^* \\ &= (60 \angle 15^\circ) \cdot (0.12 \angle +21.87^\circ) \\ &= \boxed{5.76 + j4.32}\end{aligned}$$

$$P_4 = 5.76 \text{ watts}$$


$$Q_4 = 4.32 \text{ VARs}$$

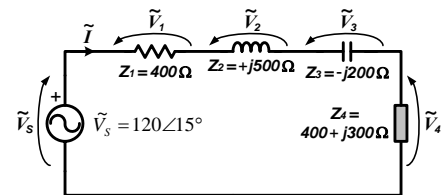



Complex Power

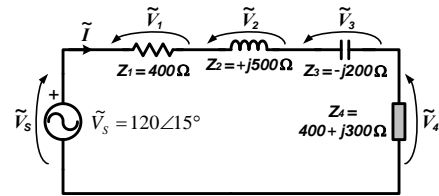Compare the **complex power** produced by the **source** and the **complex powers** consumed by the **loads**.



$$S_{Source} = 11.52 + j8.64$$


$$S_1 = 5.76 + j0 \quad S_2 = 0 + j7.2 \quad S_3 = 0 - j2.88 \quad S_4 = 5.76 + j4.32$$

$$\begin{aligned} S_{Total(Loads)} &= S_1 + S_2 + S_3 + S_4 \\ &= (5.76 + j0) + (0 + j7.2) + (0 - j2.88) + (5.76 + j4.32) \\ &= 11.52 + j8.64 \end{aligned}$$

Note that: $P_{Total(Loads)} = P_1 + P_2 + P_3 + P_4 = P_{Source}$
 $Q_{Total(Loads)} = Q_1 + Q_2 + Q_3 + Q_4 = Q_{Source}$

Complex Power

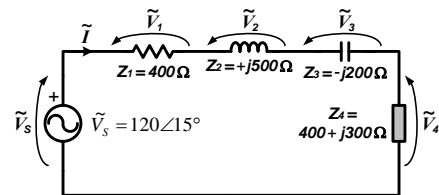Determine the **power factor** of the **source** when supplying the four loads.



$$\tilde{V}_s = 120 \angle 15^\circ \text{ volts} = V \angle \phi^\circ$$

$$\tilde{I} = 0.12 \angle -21.87^\circ \text{ amps} = I \angle \delta^\circ$$

$$\theta_s = \angle \tilde{V}_s - \angle \tilde{I} = \phi^\circ - \delta^\circ = 15^\circ - (-21.87^\circ) = 36.87^\circ$$

$$pf = \cos \theta_s = \cos(36.87^\circ) = 0.8 \text{ lagging}$$

The power factor is **lagging** because the overall equivalent load is **resistive and inductive**, resulting in a positive angle θ_s .
 $0^\circ < \theta \leq +90^\circ$

Note that the **power angle** θ_s calculated for the source:
 $\theta_s = \angle \tilde{V}_s - \angle \tilde{I} = \phi^\circ - \delta^\circ = 15^\circ - (-21.87^\circ) = 36.87^\circ$
 is equal to the angle of the overall equivalent load when expressed in polar form:
 $Z_{eq} = |Z_{eq}| \angle \theta_{eq} = (800 + j600) = (1000 \angle 36.87^\circ) \Omega$