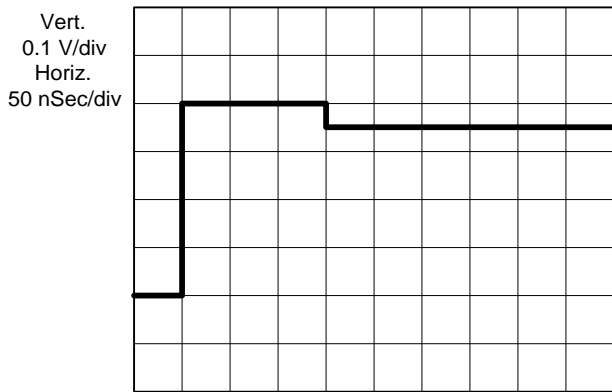


| Coaxial Cables | | | | | | | | | | | |
|----------------|--------------|------------------------|-----------|-------------|------------------|------------------|--------------------|--------------------|---------------------------|-----|------------------------|
| RG # | AWG Material | Insulation | # Shields | Jacket | Nom. O.D. (inch) | Nom. Imp. (Ohms) | Nom. Vel. Of Prop. | Nom. Cap. (pF/ft.) | Nom. Attenuation per 100' | | Standard Spool Lengths |
| | | | | | | | | | MHz | dB | |
| 14/U | 20 Copper | Poly-ethylene | 1 | Black Vinyl | .420 | 95 | 66% | 16.0 | 100 | 3.0 | 100, 500 |
| | | | | | | | | | 200 | 4.5 | |
| | | | | | | | | | 400 | 6.0 | |
| 14A/U | 20 Copper | Poly-ethylene | 1 | Black Vinyl | .420 | 92 | 66% | 16.0 | 100 | 3.5 | 100, 500 |
| | | | | | | | | | 200 | 5.0 | |
| | | | | | | | | | 400 | 7.0 | |
| 16A/U | 18 Copper | Cellular Poly-ethylene | 1 | Black Vinyl | .195 | 50 | 78% | 30.8 | 100 | 5.0 | 100,500 |
| | | | | | | | | | 200 | 7.0 | 1000 |
| | | | | | | | | | 400 | 9.5 | |
| 18/U | 18 Copper | Cellular Poly-ethylene | 1 | Black Vinyl | .280 | 75 | 78% | 24 | 100 | 2.0 | 100,500 |
| | | | | | | | | | 200 | 3.0 | 1000 |
| | | | | | | | | | 400 | 4.5 | |



Problem #1) A TDR test was performed on a piece of **RG 16A/U** cable of unknown length, terminated with a purely resistive load. The results of the test are as follows (assume the cable is lossless):



Determine the **length** of the cable in meters and the **load impedance** in ohms.

Length = 17.55 (m)
 $R_{load} = \underline{38.9} \Omega$

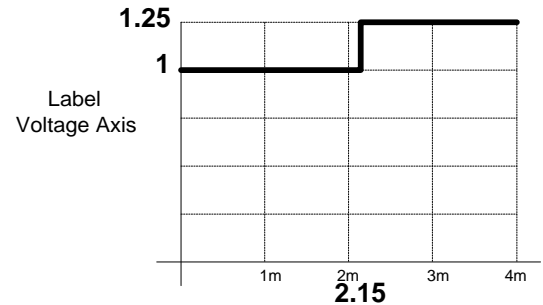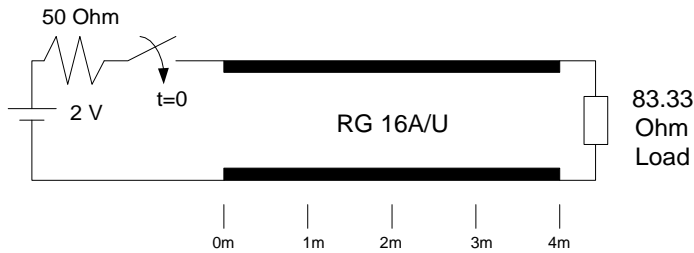Problem #2) Given the system shown below containing a transmission line (due to the short length of the line, you may assume the line is lossless for this problem), Plot the **voltage** along the line as a function of position at a time of $t = 25$ nsec.




Problem #3) A coaxial cable has an inner-conductor diameter of 0.5mm, an outer diameter of 5mm, and is filled with polyurethane ($\epsilon_r = 1.9$). Determine the **characteristic impedance (Z_0)** of the cable.

$Z_0 = \underline{100} (\Omega)$

Problem #4) A 6 meter, RG 14/U type coaxial cable is excited by a 450 MHz source. Determine the **electrical length (L)** of the line in wavelengths.

$L = \underline{\hspace{2cm}} \mathbf{13.636} \underline{\hspace{2cm}} (\lambda)$

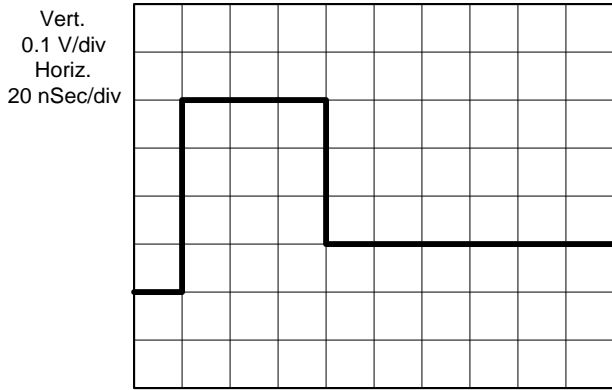Problem #5) A TDR test was performed on a piece of **RG 14A/U** cable of unknown length, terminated with a purely resistive load. The results of the test are as follows (assume the cable is lossless):





Determine the **length** of the cable in meters and the **load impedance** in ohms.


Length = **5.94** (m)

$R_{load} = \underline{\hspace{2cm}} \mathbf{13.14} \underline{\hspace{2cm}} \Omega$

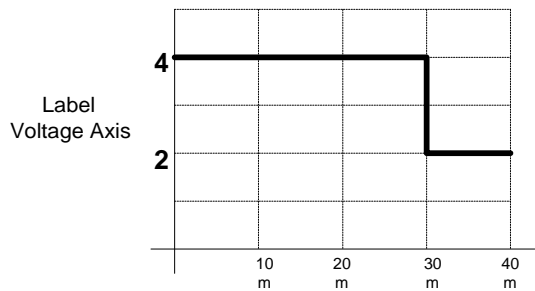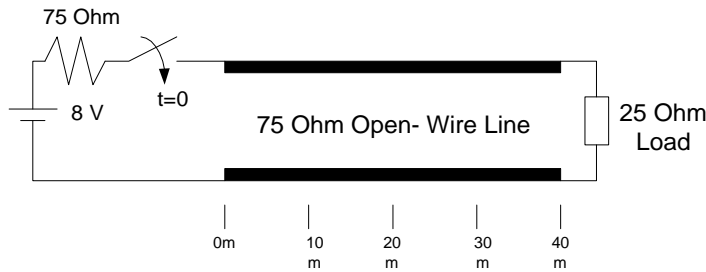Problem #6) Given the system shown below containing a lossless line, Plot the **voltage** along the line as a function of position at a time of $t = 167$ nsec.



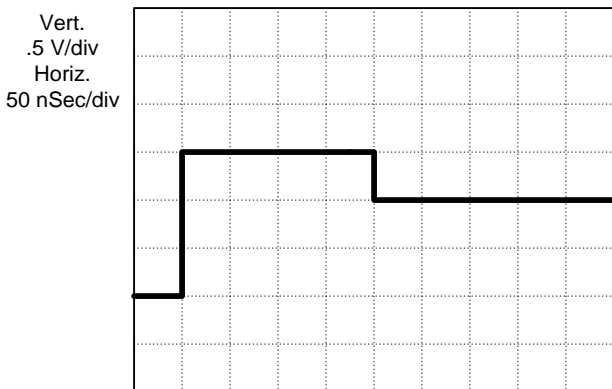Problem #7) A TDR test was performed on a piece of **RG 16A/U** cable of unknown length, terminated with a purely resistive load. The results of the test are as follows (assume the cable is lossless):




Determine the **length** of the cable in meters and the **load impedance** in ohms.

Length = **23.4** (m)

$R_{load} = \underline{\hspace{2cm}} \mathbf{25} \underline{\hspace{2cm}} \Omega$

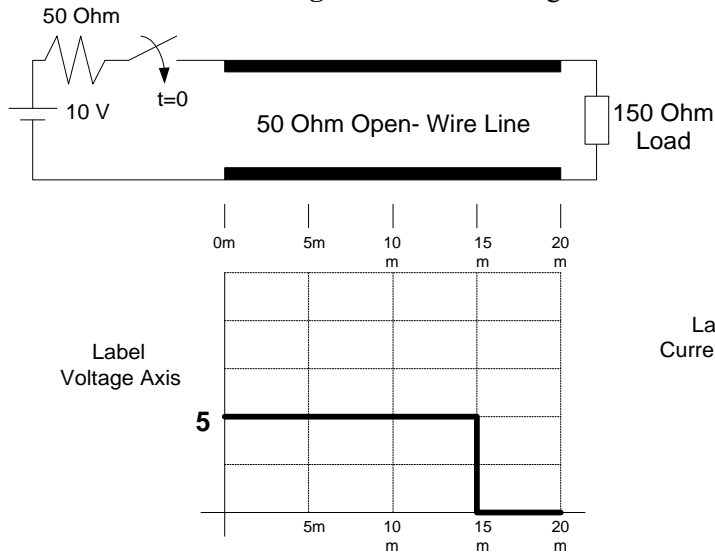Problem #8) Given the system shown below containing a lossless line,
 Plot the **voltage** and **current** along the line as a function of position at $t = 0.05 \mu\text{sec}$.



Problem #9) Define the “Characteristic Impedance” of a transmission line. (Do NOT provide formulas)

(See textbook)


Problem #10) A long piece of **RG 14/U** cable is measured to have an attenuation value of 12.5 dB at 200 MHz.
 Determine the unknown **length** of the cable.

Length = 277.8 ft.

Problem #11) It is determined that a transient propagates down the entire length of a 200 meter spool of coaxial cable in 1.075 μsec . Assuming a unity relative permeability ($\mu_r=1$) for the cable, determine the **relative permittivity** (ϵ_r) of the insulation within the cable.

$\epsilon_r =$ 2.6

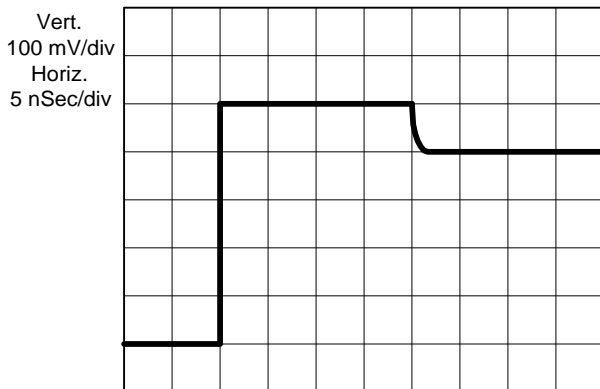Problem #12) A TDR test was performed on a piece of RG 16A/U cable terminated with an unknown load. The results of the test are as follows (assume the cable is lossless):



Determine the **length** of the cable in meters and the **load impedance** in ohms.

length = 2.34 (m)

$Z_R =$ 33.3 Ω

Problem #13) A 4 mW r.f. wave is applied to the input of a transmission line with a matched load.

- a) **Convert** this value to **dBm**.
- b) If the transmission line is a 200' section of RG 14/U and the frequency of the wave is 100MHz, how much r.f. power will reach the **receiving end** of the line (in dBm)

a) $P_{in} = \underline{\quad 6 \quad}$ (dBm)




b) $P_{out} = \underline{\quad 0 \quad}$ (dBm)

Problem #14) Determine the attenuation constant and the propagation constant for a section of RG 14A/U at a frequency of 400 MHz. (1 ft = 0.3048 m)


$\alpha = \underline{\quad 0.00805 \quad}$ (Np/ft)

$\beta = \underline{\quad 3.86 \quad}$ (rad/ft)

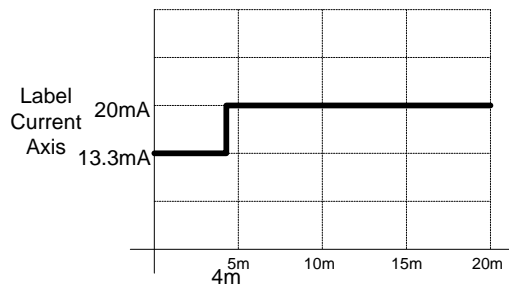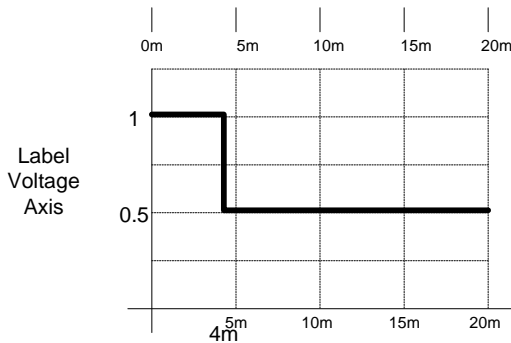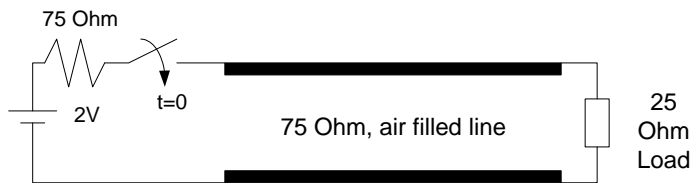Problem #15) Given the system shown below containing a transmission line (assume the line is lossless), Plot the **voltage** and **current** along the line as a function of position at a time of $t = 0.12 \mu\text{sec}$ after the switch closes.



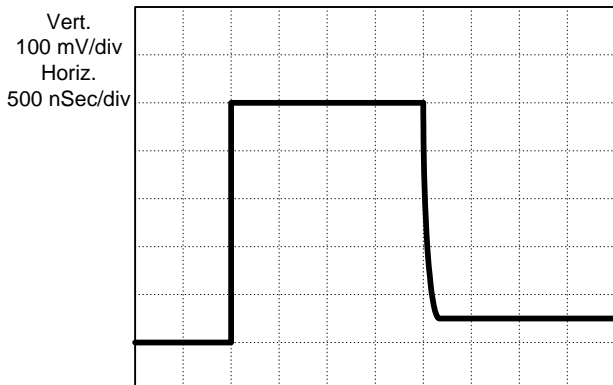Problem #16) A TDR test was performed on a piece of RG 18/U cable terminated with an unknown load. The results of the test are as follows (assume the cable is lossless):




Determine the **length** of the cable in meters and the **load impedance** in ohms.

length = (m)

$Z_R = \underline{\hspace{2cm}}$ Ω

If the cable is not assumed lossless, would your answers change? (circle one) \rightarrow (Yes / No)
Justify your answer in the space below:

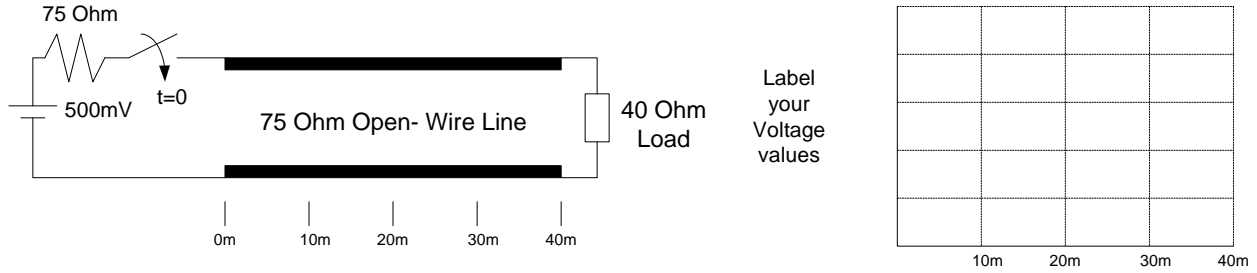Problem #17) Given the system shown below containing a lossless line,
Plot the **voltage** as a function of position at a time of $t = 467$ nsec after the switch closes.



Problem #18) A 20mW r.f. wave is applied to the input of a transmission line terminated with a matched load.

- c) **Convert** this input power value to **dBm**.
- d) If the transmission line is a 150' section of **RG 16A/U** and the frequency of the wave is 400MHz, how much r.f. power will reach the **receiving end** of the line (in dBm)
- e) **Convert** the dBm output power to its equivalent **milliwatts** value.

c) $P_{in} = \underline{\hspace{2cm}}$ (dBm)

d) $P_{out} = \underline{\hspace{2cm}}$ (dBm)

e) $P_{out} = \underline{\hspace{2cm}}$ (mW)

Problem #19) For each of the following, specify whether or not each of the responses is true by writing either **TRUE** or **FALSE** in the blank preceding each response.

 The magnitude of a **reflection coefficient** due to a load can never be greater than one.

 The **characteristic impedance** of a transmission-line defines the ratio of voltage to current of an incident or a reflected waveform.

 For normal transmission-lines, the **permeability** of the material surrounding the line is assumed to be one.

 Given a source connected to a coaxial line; if the source frequency is increased, the **wavelength** on the line will also increase.

 The **nominal velocity** (as given in table 1-3 of the text) defines the velocity of a wave on a coaxial-cable as a percent (%) of the speed of light in "air" (free-space).

 When expressed in decibels, **attenuation** on a coaxial-cable is linearly proportional to length.

 Both the **attenuation constant** (α) and the **phase delay** (β) may be assumed to be zero on a lossless transmission-line.

Answers to True/False:

True
True
True
False
True
True
False

Last ← First

Additional True/False Problems)

_____ The *magnitude* of the *reflection coefficient* due to a termination must be less than one.

_____ A *lossless* transmission-line will always have a propagation velocity of 3×10^8 m/sec or less.

_____ Given a source connected to a coaxial line; if the source frequency is increased, the *wavelength* on the line will also increase.

_____ When expressed in decibels, *attenuation* on a coaxial-cable is linearly proportional to length.

_____ The *velocity of propagation* is assumed to be 3×10^8 m/sec for an air-filled coaxial cable.

_____ The *attenuation constant* (α) and the *phase delay* (β) must both be non-zero on a lossy transmission line.

_____ For normal coaxial transmission-lines, the *relative permittivity* of the material between the conductors is assumed to be one.

Answers to True/False:

False
True
False
True
False
False

Last ← First .