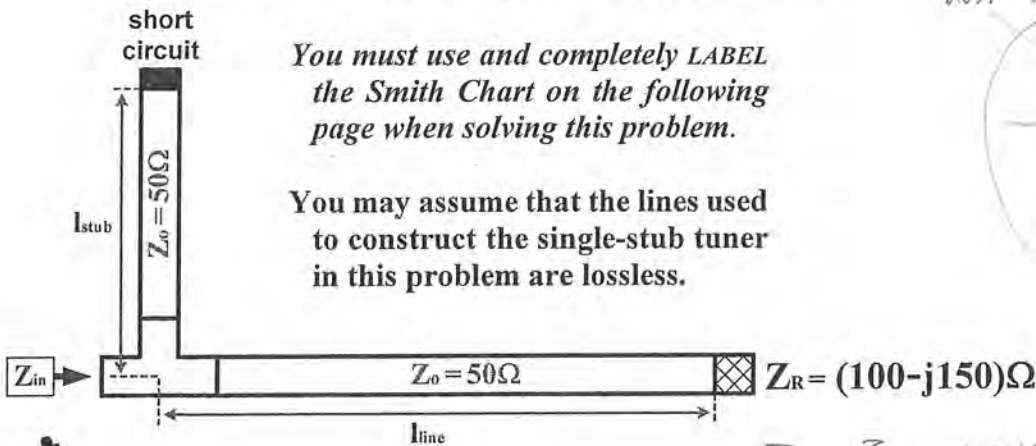


Instructions: Show all of your work, making sure that your work is legible and that your reasoning can be followed. No credit will be given for illegible or illogical work, or for final answers that are not justified by the work shown. Place all final answers in the spaces provided. This exam is closed book, except for a single 8.5"x11" sheet of handwritten notes which may NOT contain any numerically-solved problems.


Coaxial Cables											
RG #	AWG Material	Insulation	# Shields	Jacket	Nom. O.D. (inch)	Nom. Imp. (Ohms)	Nom. Vel. Of Prop.	Nom. Cap. (pF/ft.)	Nom. Attenuation per 100'		Standard Spool Lengths
									MHz	dB	
14A/U	20 Copper	Poly-ethylene	1	Black Vinyl	.420	92	66%	16.0	100 200 400	3.5 5.0 7.0	100, 500
16A/U	18 Copper	Cellular Poly-ethylene	1	Black Vinyl	.195	50	78%	30.8	100 200 400	2.5 3.5 5.0	100,500 1000
18/U	18 Copper	Cellular Poly-ethylene	1	Black Vinyl	.280	75	78%	24	100 200 400	2.0 3.0 4.5	100,500 1000

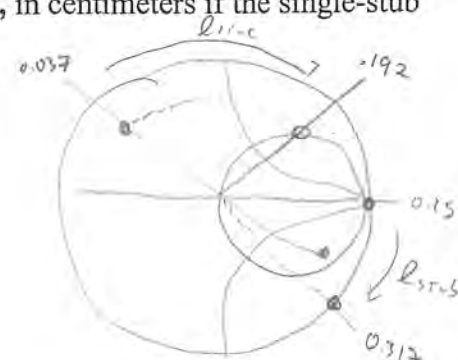Problem #1) A single-stub tuner, consisting of a 50Ω main “line” connected in parallel with a 50Ω short-circuited “stub” is used to match a load of $Z_R = (100 - j150)\Omega$ to a 50Ω, 400MHz system. Determine the lengths of the “line” and “stub”, l_{line} and l_{stub} , in centimeters if the single-stub tuner is constructed using air-filled, coaxial lines.



You must use and completely LABEL the Smith Chart on the following page when solving this problem.

You may assume that the lines used to construct the single-stub tuner in this problem are lossless.




Convert $\lambda \rightarrow cm$

$$l_{line} = 0.155 \lambda \times 75 \frac{cm}{\lambda} = 11.6 cm$$

$$l_{stub} = 0.067 \lambda \times 75 = 5.0 cm$$

$$\bar{Z}_R = \frac{Z_R}{Z_0} = \frac{100 - j150}{50} = 2 - j3$$
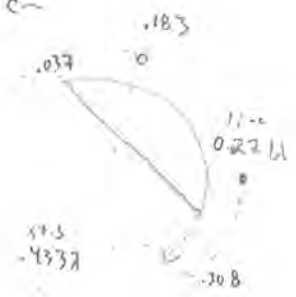
$$\lambda = \frac{3 \times 10^8}{400 \times 10^6} = 75 cm$$



- 2) $\Gamma_{in} = 13.2 \angle \pi$
 $V_{SWR} = 6.9 \times 3.8$
- 3) $Z_{in} = 112.5 \Omega$
 $l_{line} = 10 cm$
- 4) Γ_{in}
- 5) $\bar{Z}_R = 2 - j3 \Omega$
 $\Gamma_R = 0.524 \angle -36^\circ$
 $f = 1364 MHz$

Solve for


$l_{line} =$	11.6	20.3	cm
$l_{stub} =$	5.0	32.5	cm

LINE
 END 0.192
 START -0.037
 $l_{line} = 0.155\lambda$


$\bar{Y}_{line} = 1 + j2.22$

$\therefore L \rightarrow \bar{Y}_{stub} = -j2.22$

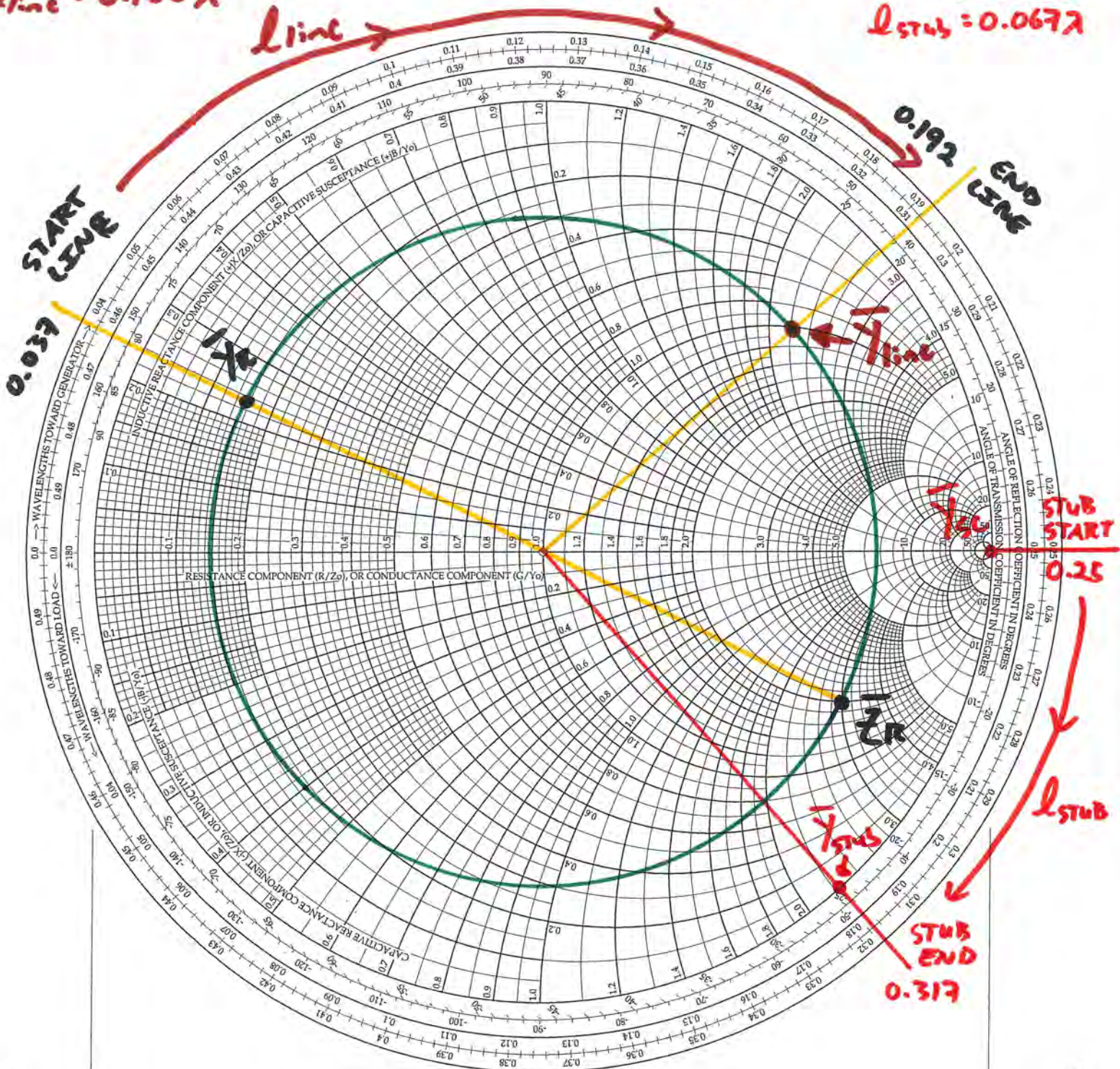STUB
 END 0.317
 START -0.250
 $l_{stub} = 0.067\lambda$




RADIALLY SCALED PARAMETERS

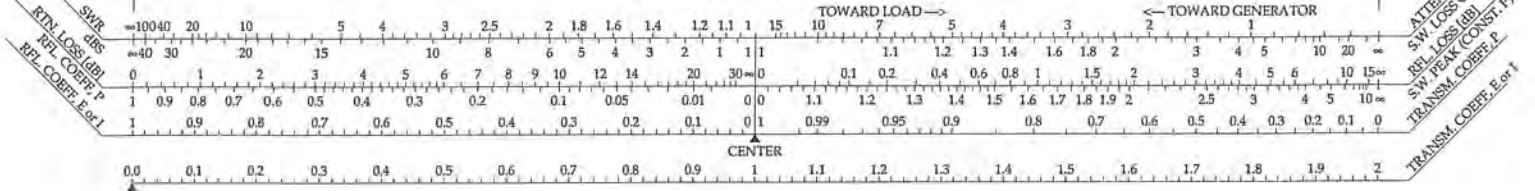

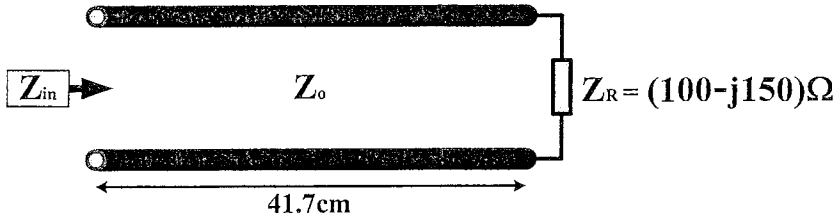Problem #2) A 41.7cm long, lossy transmission line with the following characteristics:
 $Z_0 = 50\Omega$, $\gamma = 0.3 + j10.74$ (Np/m and rad/m respectively)
 is terminated with a load $Z_R = (100 - j150)\Omega$ and supplied by a 400MHz source.
 Determine the **input impedance**, Z_{in} , of the line and the **VSWR** on the line.

You must use and completely LABEL the Smith Chart on the following page when solving all parts of this problem.




$$\bar{\epsilon}_R = 2 - j3$$

$$\lambda = \frac{c}{f} = 0.585 \text{ m} = 58.5 \text{ cm}$$

$$l = \frac{41.7 \text{ cm}}{58.5 \text{ cm}} = 0.713 \lambda$$

$$\frac{-0.5}{0.213 \lambda}$$

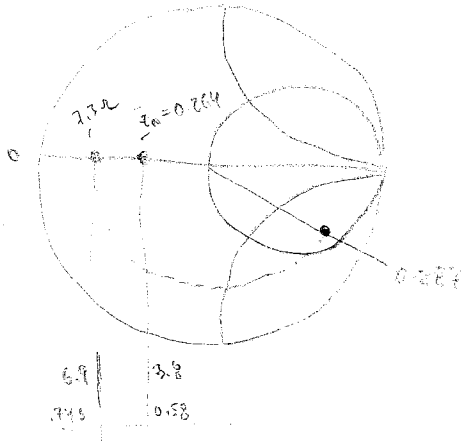

$$|\Gamma| = 0.7152$$

$$|\Gamma_{in}| = 0.2547 \text{ e}^{-2(0.3)(0.417)}$$

$$= (0.7452) \text{ e}^{-0.2502}$$

$$= (0.7452)(0.7787)$$


$$= 0.58$$

$$Z_{in} = \bar{\epsilon}_R \cdot Z_0 = (0.264 + j0)(50) = \boxed{13.2 \Omega}$$

$$Z_{in} = \frac{13.2}{\text{(Load) (in)}} \Omega$$

$$\text{VSWR} = \frac{6.9 \text{ or } 3.8}{\text{(in)}}$$

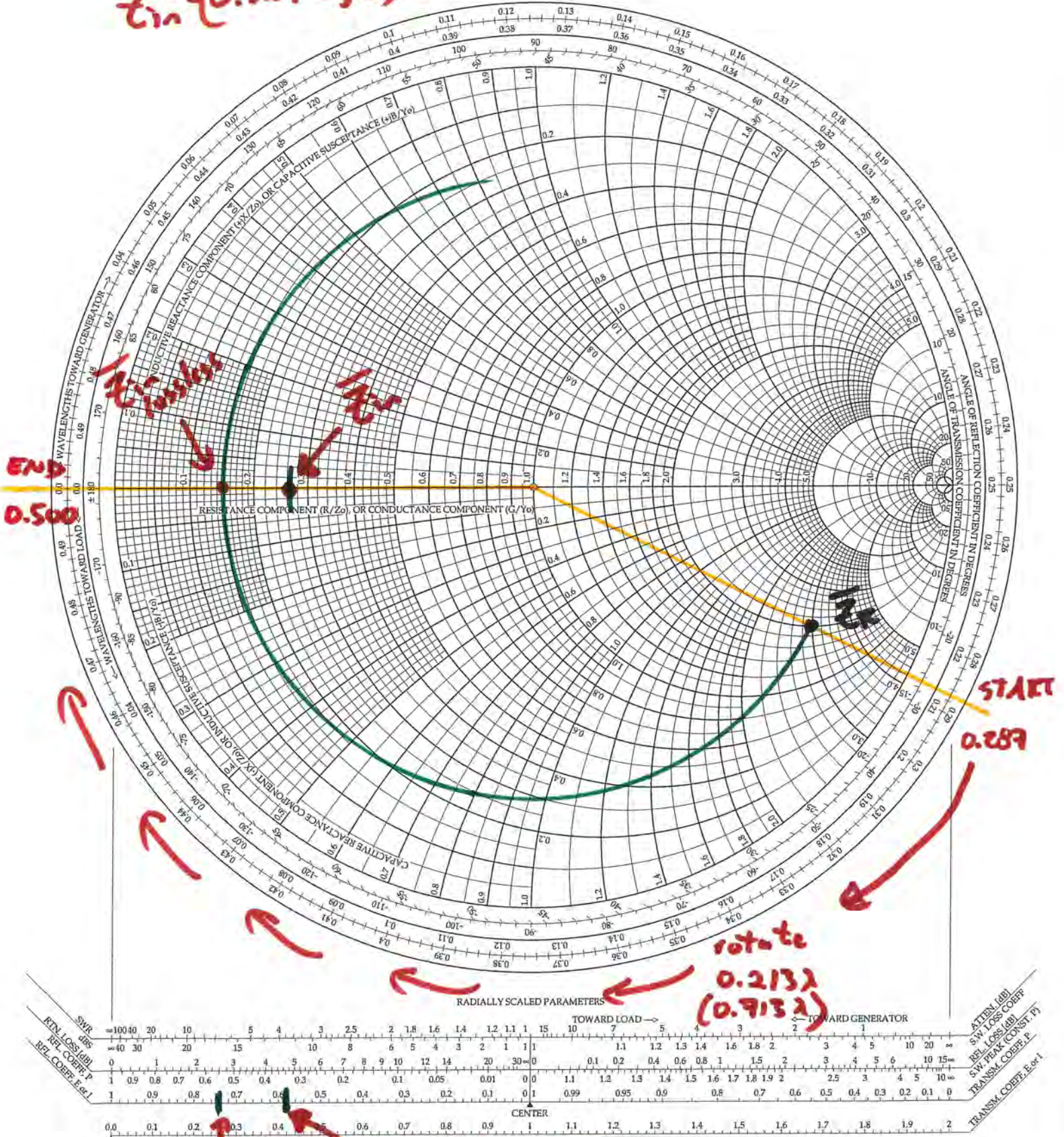$\bar{\Gamma}_{in} = (0.264 + j0)\epsilon$



END
0.500

Γ_{in}

Γ_{in}

Γ_{in}

START
0.287

rotate
0.213λ
(0.713λ)

$|\Gamma_R| = 0.745$ $|\Gamma_{in}| = 0.58$

Problem #3) A section of **RG 18/U** coaxial cable will be used as a $\frac{1}{4}$ -wavelength tuner to match a load to a **50Ω, 585MHz source**. Assuming that the coaxial cable may be considered lossless due to its short length, determine the value of the **load impedance, Z_R** , and the **length of the $\frac{1}{4}$ -wavelength tuner, l_{tuner}** , in centimeters.

$$\epsilon_{\text{tot}} = \sqrt{\epsilon_0 \epsilon_r}$$

$$\hookrightarrow Z_0 = \frac{Z_0^2}{\epsilon_r} = \frac{75^2}{50} = \boxed{112.5 \Omega}$$

$$v = 0.78c = 2.34 \times 10^8 \text{ m/s}$$

$$\lambda = \frac{v}{f} = \frac{2.34 \times 10^8}{585 \times 10^6} = 0.4 \text{ m} = 40 \text{ cm}$$

$$l = \frac{1}{4}\lambda = \frac{1}{4}(40) = \boxed{10 \text{ cm}}$$

$$Z_{\text{Load}} = \underline{112.5} \Omega$$

$$l_{\text{tuner}} = \underline{10} \text{ cm}$$

Problem #4) Specify whether each of the statements are **TRUE** or **FALSE**.

False Compared to a $\frac{1}{4}$ -wavelength tuner, a **single-stub tuner** will theoretically provide a better match for a purely real load impedance to a purely real source impedance.

• TRUE A (lossless) **short-circuited stub** of length L can have any desired, purely inductive, input impedance value depending on the length L of the stub.

• TRUE The set of normalized load impedances formed by drawing a circle centered at the origin of a Smith Chart will all result in the same **VSWR** on the transmission-line.

False The set of normalized load impedances formed by drawing a circle centered at the origin of a Smith Chart will all result in the same **reflection coefficient** on a transmission-line.

False Adding **one wavelength** to the length of a line terminated by a load will result in an additional rotation of 1 revolution on a Smith Chart when solving for Z_{in} .

False A $\frac{1}{4}$ -wavelength tuner may be used to match a purely imaginary load (such as the load $Z_R = 0 + j200\Omega$) to a 50Ω source.

False The **circle** that provides the **outer-boundary** of the Smith Chart defines the set of impedances that all have imaginary values of zero (I.e. – purely resistive impedances).


• TRUE The point having the **largest magnitude** within the set of impedances formed by drawing a circle centered at the origin of the Smith Chart will be the "right-most" point on the circle.

Problem #5) When an air-filled, 50Ω , slotted-line is terminated with a "short-circuit", voltage minima (nulls) are measured at positions of 33cm and 44cm on the line.

When the "short-circuit" is replaced by an unknown load, the measured VSWR on the line is 3.2 and a voltage minimum is detected at 39.6cm .


Determine the load impedance (in rectangular form), the reflection coefficient of the load (in polar form), and the frequency of operation.

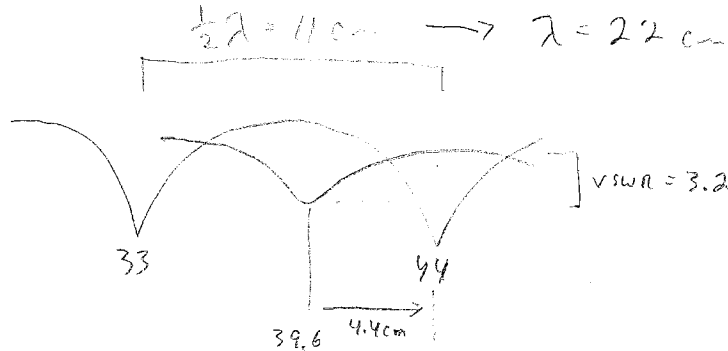You must use and completely LABEL the Smith Chart on the following page when solving all parts of this problem (except for the frequency).



$$\frac{4.4\text{cm}}{22\text{cm}/2} = 0.2\lambda \text{ Towards load}$$
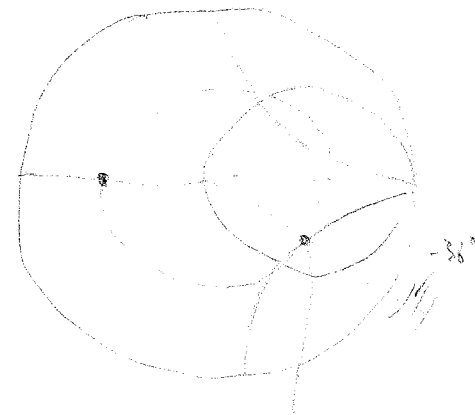
$$\lambda = \frac{v}{f} \rightarrow f = \frac{v}{\lambda} = \frac{3 \times 10^8}{0.22} = \boxed{1364\text{MHz}}$$



$$\bar{Z}_R = 1.7 - j0.72$$

$$Z_R = \bar{Z}_R \cdot Z_0 = \boxed{85 - j72}$$

$$\Gamma_R = \boxed{0.524 \angle -36^\circ}$$

$$Z_R = \underline{85 - j72} \quad \Omega$$


$$\Gamma_R = \underline{0.524 \angle -36^\circ}$$

$$f = \underline{1364} \quad \text{MHz}$$

Do NOT Write Below This Line

1) _____/25 2) _____/25 3) _____/10 4) _____/15 5) _____/25 Total) _____/100

$$\bar{\Gamma}_R = 1.7 - j1.44$$

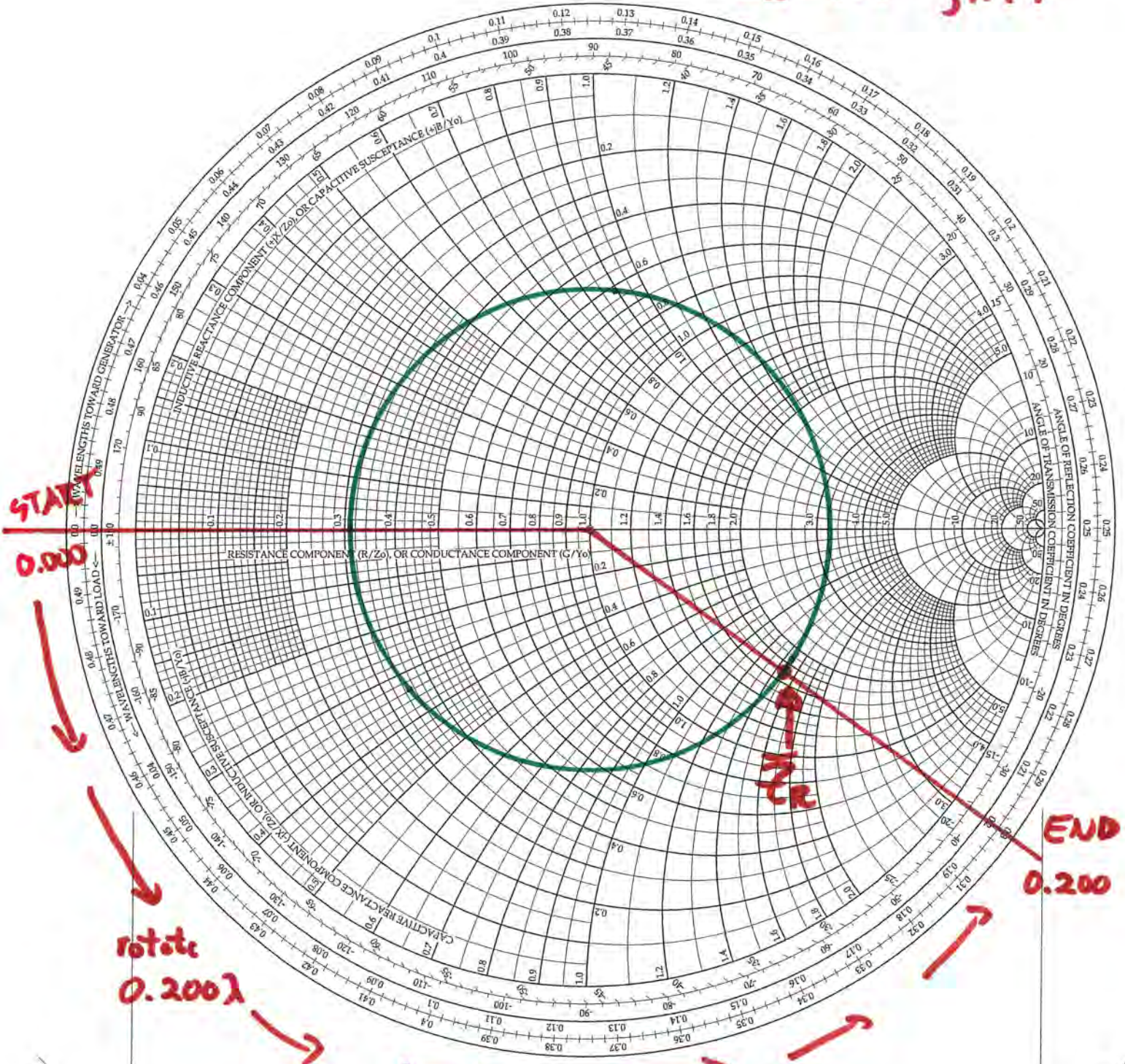

RADIALLY SCALED PARAMETERS

