



# *ECET 3410*

## *High Frequency Systems*

### *Transmission Line Analysis using Smith Charts*

1




## **Transmission Line Analysis using Smith Charts**

To find the **input impedance** of a lossless transmission-line using a Smith Chart:

- 1) Plot the **normalized load impedance**.
- 2) Draw the **constant  $|\Gamma|$  circle**.
- 3) Rotate “Towards the Generator” (CW) the **length of the line (in wavelengths)** referenced to the  $\frac{1}{2}$ -wavelength scale provided in the outer band.
- 4) Read the **normalized input impedance**.

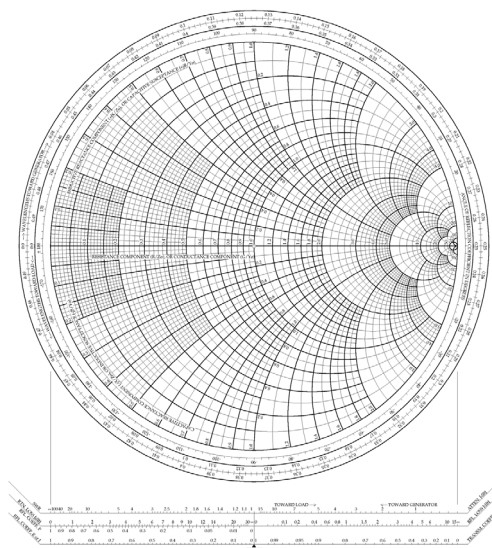
**Note that the reverse procedure can be utilized to determine the load impedance from the input impedance.**




2



## Textbook Example 4-1

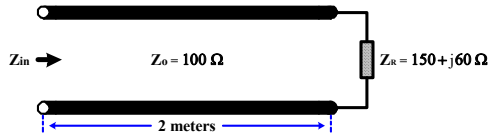

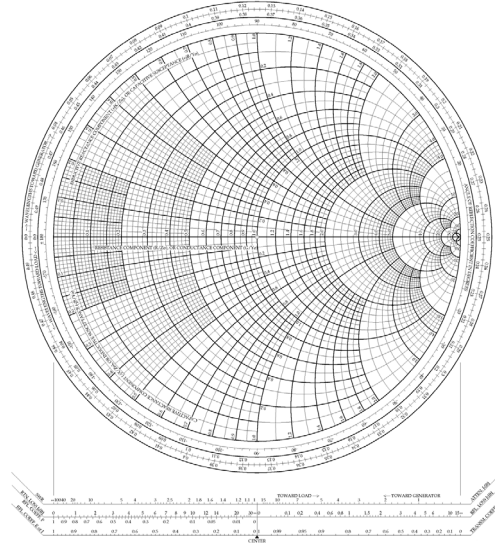
Determine the **input impedance** of a **2-meter** long, **air-filled, lossless, 100Ω** transmission line that is terminated by a load  $Z_R = (150 + j60)\Omega$  and supplied by a source that is operating at a frequency of **50MHz**.



3



## Textbook Example 4-1

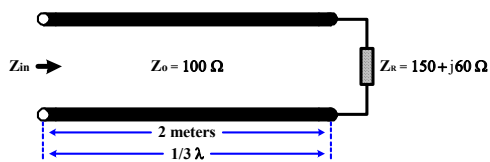


**Step 0:** If not expressed in wavelengths, convert the **line length** from physical units (meters) to electrical units (wavelengths).

$$v_{air} = c = 3 \cdot 10^8 \frac{\text{meters}}{\text{sec}}$$

$$\lambda = \frac{v}{f} = \frac{3 \cdot 10^8}{50 \cdot 10^6} = 6 \text{ meters}$$

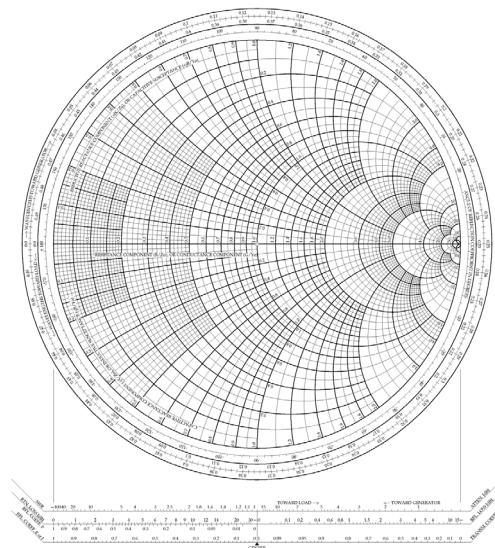
$$L = \frac{2 \text{ meters}}{6 \frac{\text{meters}}{\text{wavelength}}} = \frac{1}{3} \text{ wavelength}$$



4




## Textbook Example 4-1

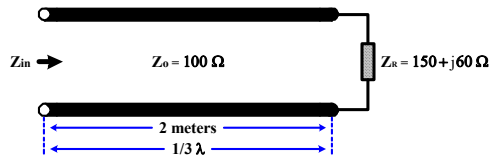

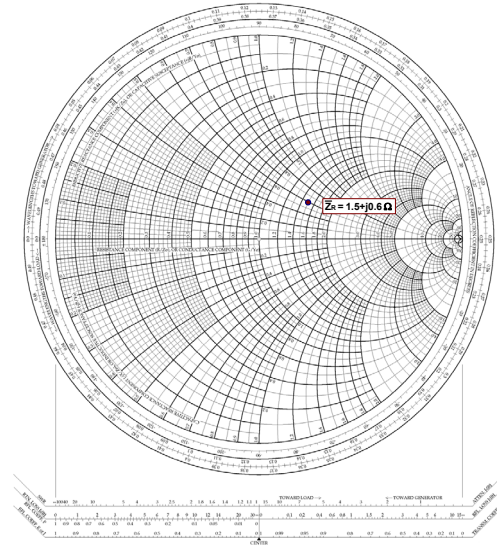**Step 1: Normalize and plot the known (load) impedance.**

$$\bar{Z}_R = \frac{Z_R}{Z_o} = \frac{150 + j60}{100} = (1.5 + j0.6)\Omega$$


Since a Smith Chart with an impedance of 1 at its origin provides a mapping of normalized impedance to reflection coefficient, the load impedance must first be normalized and then plotted.



5




## Textbook Example 4-1

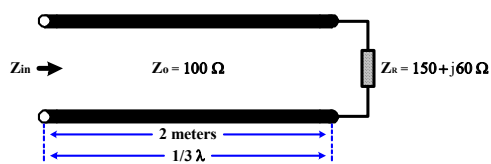

**Step 2: Draw a constant  $|\Gamma|$  circle that is centered at the origin of the Smith Chart and passes through the plotted impedance  $\bar{Z}_R$ .**


On a lossless line,  $|\Gamma_{in}| = |\Gamma_R|$ . Since the magnitude of the reflection coefficient is defined by the distance from the origin, the normalized load impedance and the normalized input impedance must both fall on a circle centered about the origin.

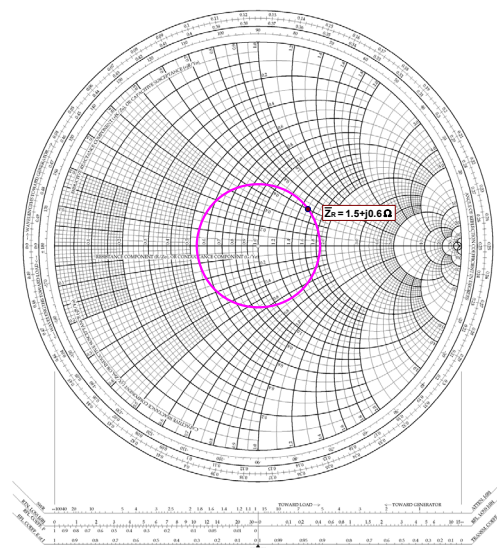

6




## Textbook Example 4-1

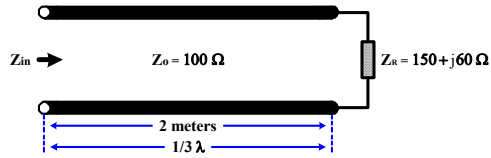

**Step 3a:** Draw a line from the origin, through the known impedance, to the 1<sup>st</sup> band and determine the STARTING marker position.

START      0.199

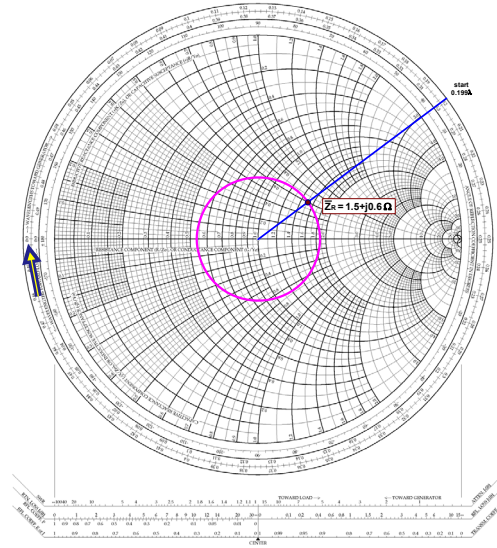
Since the input reflection coefficient,  $\Gamma_{in}$ , will rotate one complete revolution clockwise from  $\Gamma_R$  for each  $1/2$ -wavelength of line-length, the 1<sup>st</sup> band (Wavelengths Toward Generator) can be utilized to determine the required rotation.



7




## Textbook Example 4-1

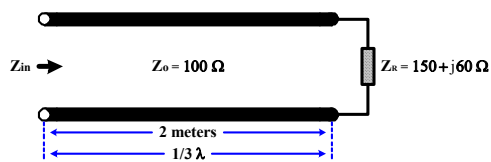

**Step 3b:** Locate the ENDING marker position on the 1<sup>st</sup> band and draw a line from the origin to the ENDING marker.

START	0.199
length	+ 0.333
END	0.532
	- 0.500
Equivalent END	0.032

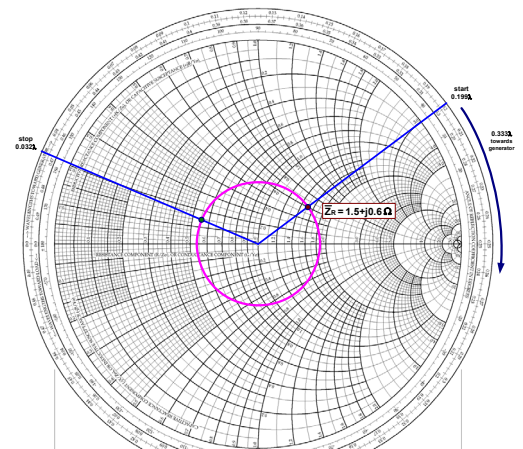


If the ending marker position is greater than 0.500, then subtract whole multiples of 0.5 to find an equivalent ending position since the scale on the 1<sup>st</sup> band resets back to 0.000 at the 0.500 marker.

8






## Textbook Example 4-1

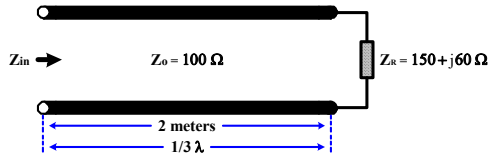

**Step 4:** Read the **normalized** value of the unknown impedance ( $\bar{Z}_{in}$ ) at the point where the **END line intersects the constant  $|\Gamma|$  circle.**

$$\bar{Z}_{in} = (0.55 + j0.14)\Omega$$

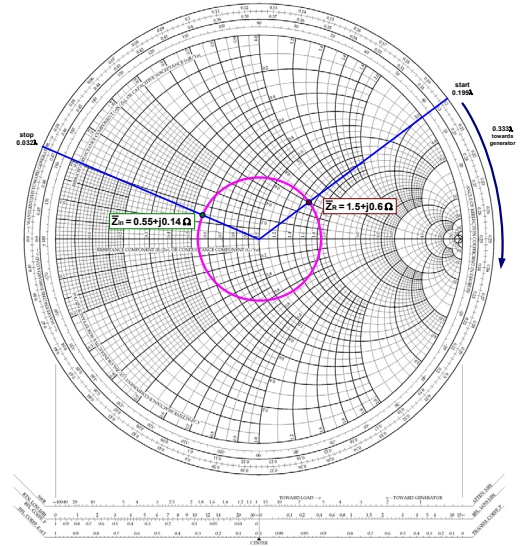
$$Z_{in} = \bar{Z}_{in} \cdot Z_o = (55 + j14)\Omega$$



9




## Textbook Example 4-1

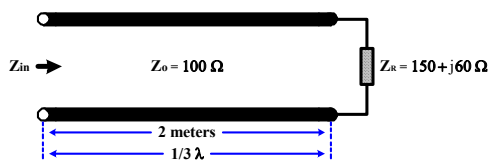

The **Reflection Coefficients**  $\Gamma_R$  and  $\Gamma_{in}$  on the line can be determined from the Smith Chart solution by using both the **3<sup>rd</sup> scale (RFL COEFF E or I)** provided at the **bottom left side** of the chart and the **3<sup>rd</sup> band (ANGLE OF RFL COEFF IN DEGS)** provided around the outer portion of the Smith Chart.

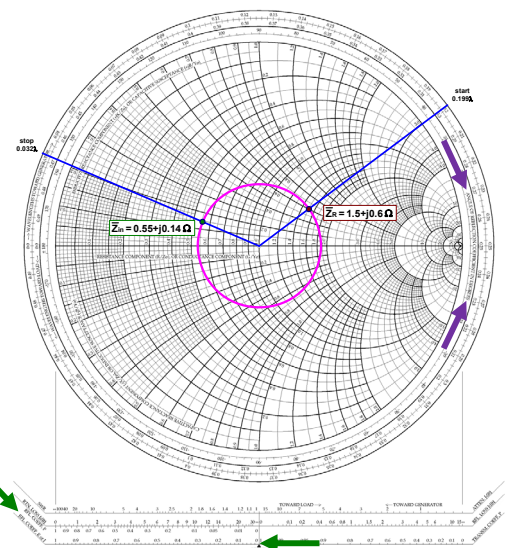
Note that the 4<sup>th</sup> band has been erased and a 4<sup>th</sup> scale has been removed from the Smith Charts shown in this presentation.



10




## Textbook Example 4-1

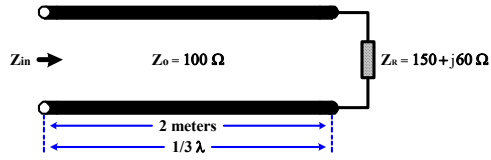

The  $|\Gamma_R|$  is found by **measuring** the **distance** from  $\bar{Z}_R$  to the **origin** and then **reading** the **value** that corresponds to the same **distance** to the **left of center** on the **3<sup>rd</sup> scale (RFL COEFF E or I)** that is provided at the bottom left side of the Smith Chart.

$$|\Gamma_R| = 0.3$$


$$\Theta_R = 36.8^\circ$$

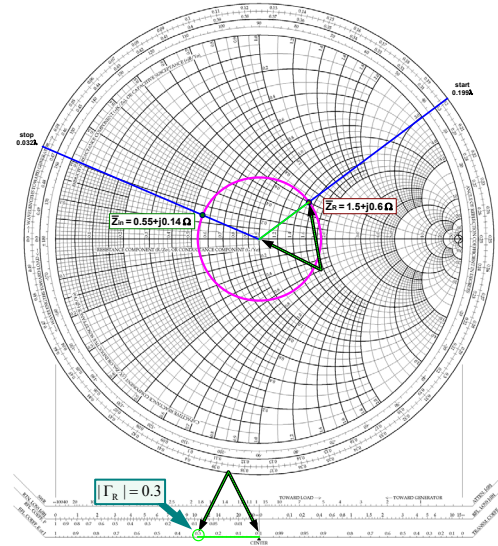

11




## Textbook Example 4-1

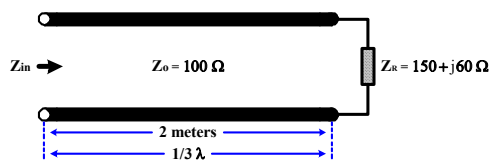

The  $\angle \Gamma_R$  is the **angle** that the **START line** (drawn from the **origin**, through  $\bar{Z}_R$ , to the outer bands) forms with the right-hand side of the horizontal axis.

This **angle** can be found by **reading** the **value** corresponding to the point at which the **START line** crosses the **3<sup>rd</sup> band**.


$$\Theta_R = 36.8^\circ$$

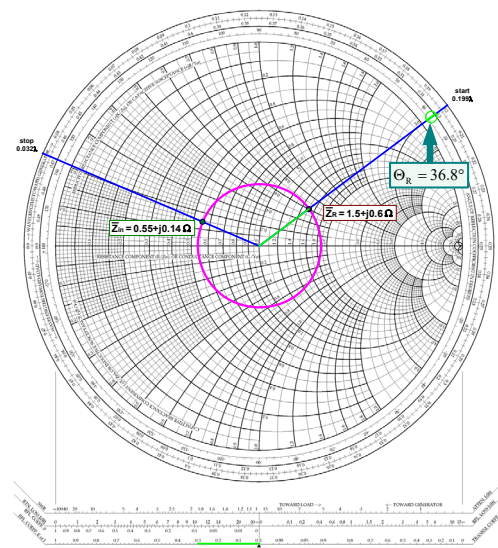

12



## Textbook Example 4-1

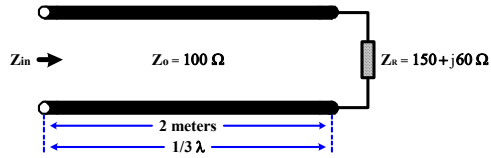


Thus,  $\Gamma_R$ , the reflection coefficient of the load is:

$$\Gamma_R = 0.3 \angle 36.8^\circ$$


A **mathematical check** can be used to verify the accuracy of the result:
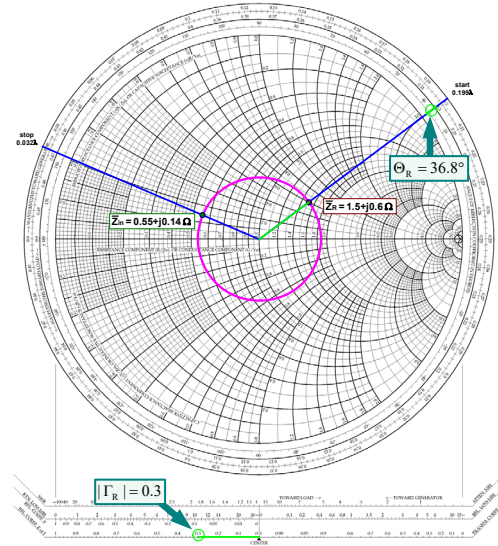
$$\Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o} = \frac{50 + j60}{250 + j60} = 0.304 \angle 36.7^\circ$$



13

## Textbook Example 4-1

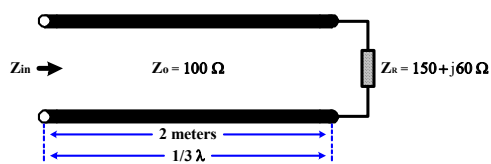


Similarly,  $\Gamma_{in}$ , the reflection coefficient at the **input** has the same magnitude as  $\Gamma_R$  but a different angle:

$$\Gamma_{in} = 0.3 \angle 157^\circ$$

**Checking** the result:

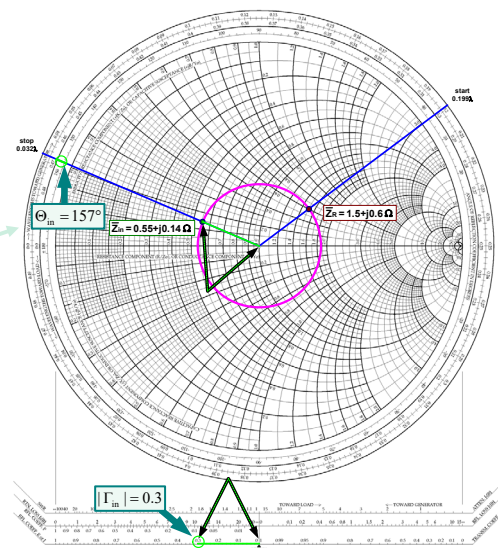
$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{-45 + j14}{155 + j14} = 0.303 \angle 157.6^\circ$$



14




## Textbook Example 4-2

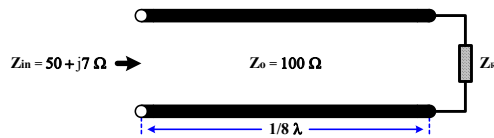

Determine the **load impedance** the terminates a 1/8-wavelength long, 100 $\Omega$ , lossless line if the input impedance of the line is  $Z_{in} = (50 + j7)\Omega$ .

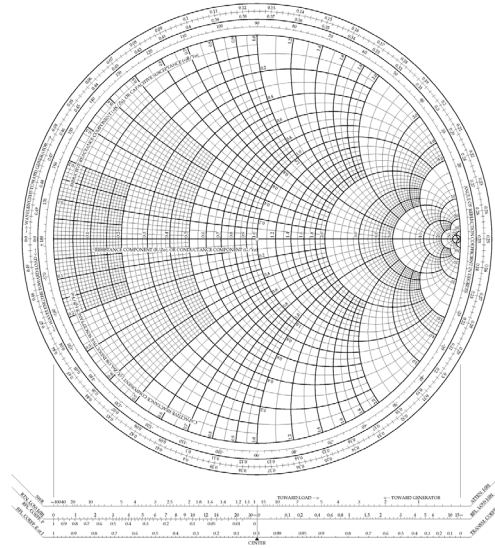
Since the length of the line is already expressed in wavelengths, neither frequency nor velocity is needed in order to solve this problem.



15




## Textbook Example 4-2

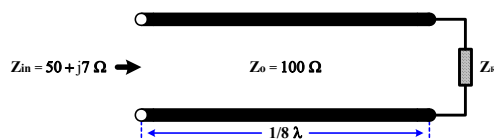

**Step 1: Normalize and plot the known input impedance.**

$$\bar{Z}_{in} = \frac{Z_{in}}{Z_0} = \frac{50 + j7}{100} = (0.50 + j0.07)\Omega$$

**Step 2: Draw a constant  $|\Gamma|$  circle that passes through the normalized input impedance.**

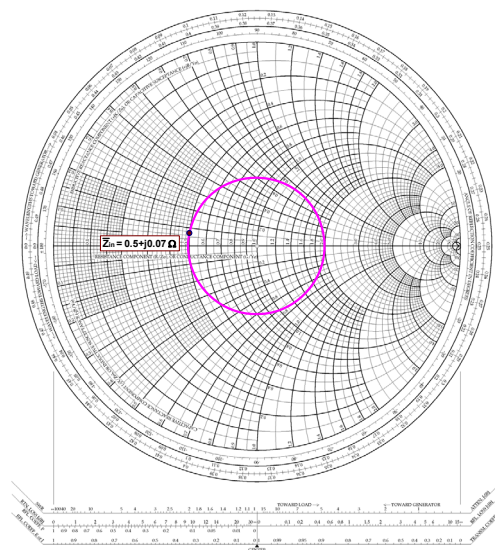


16






## Textbook Example 4-2

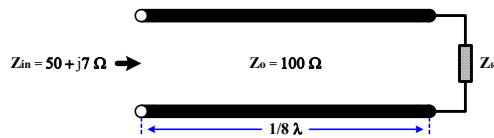

**Step 3: Draw a line from the origin, through the known impedance, to the 2<sup>nd</sup> band and determine the starting marker position.**


START 0.485

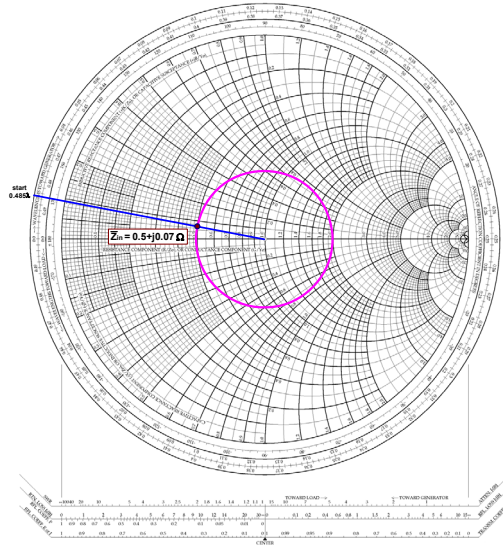

17




## Textbook Example 4-2

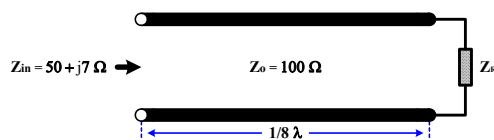

**Step 4: Rotate the length of the line (toward generator) and draw a line from the origin to the ending marker.**


START	0.485
length	+ 0.125
END	0.610
	- 0.500
Equivalent END	0.110

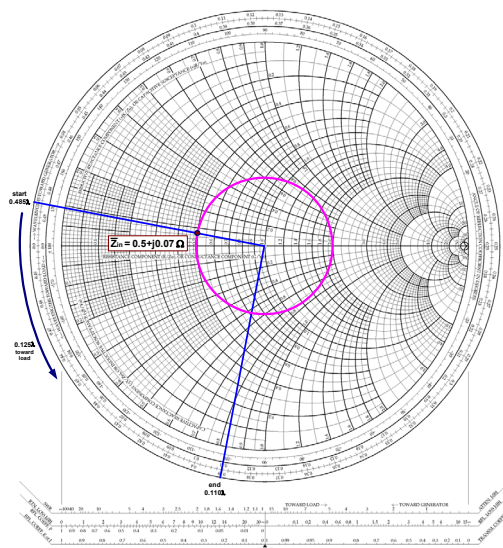

18




## Textbook Example 4-2

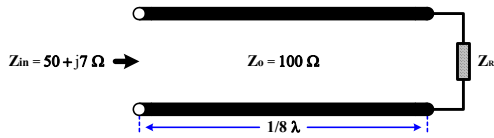

Step 5: Read the value of the unknown impedance at the point where the ending line crosses the constant  $|\Gamma|$  circle.

$$\bar{Z}_R = (0.72 - j0.53)\Omega$$

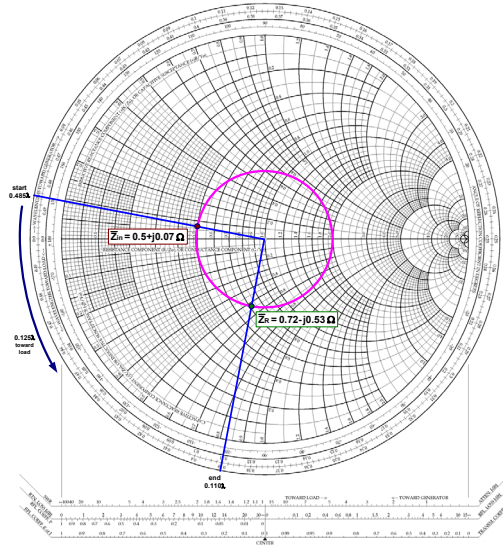
$$Z_R = \bar{Z}_R \cdot Z_0 = (72 - j53)\Omega$$




19



## Textbook Example 4-3

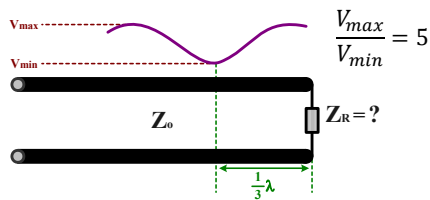

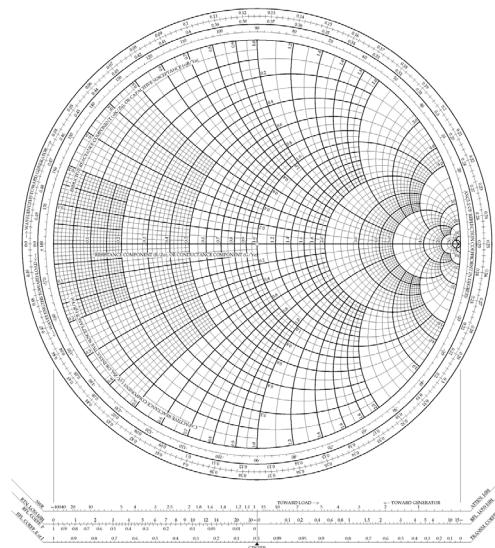
If the VSWR is measured to be 5 on a lossless, 50Ω line and a voltage minima occurs 1/3 of a wavelength from the load, determine the value of the load  $Z_R$ .



20



## Textbook Example 4-3

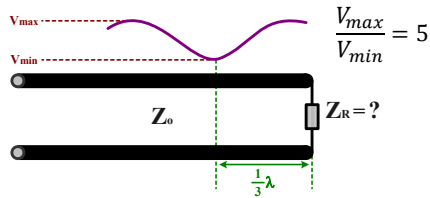


If the VSWR is measured to be 5 on a lossless,  $50\Omega$  line and a voltage **minima** occurs  $1/3$  of a wavelength from the load, determine the value of the load  $Z_R$ .

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad |\Gamma| = \frac{VSWR - 1}{VSWR + 1}$$

$$|\Gamma| = \frac{VSWR - 1}{VSWR + 1} = \frac{5 - 1}{5 + 1} = \frac{4}{6} = 0.667$$


The 1<sup>st</sup> and 3<sup>rd</sup> bottom-left scales provide a mapping from  $|\Gamma| \leftrightarrow VSWR$

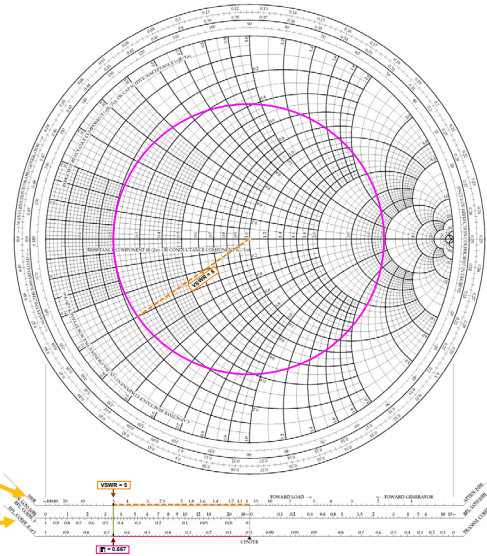

21




## Textbook Example 4-3

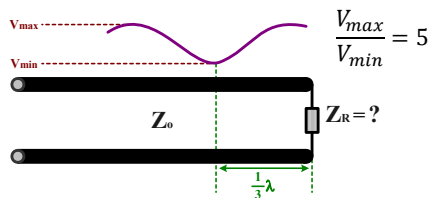

If the VSWR is measured to be 5 on a lossless,  $50\Omega$  line and a voltage **minima** occurs  $1/3$  of a wavelength from the load, determine the value of the load  $Z_R$ .

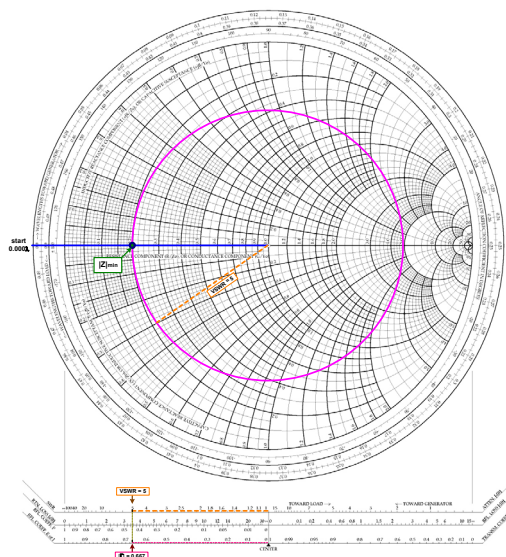
Note that a **voltage minima** in the SWR pattern occurs wherever there is an **impedance minimum** on the line.



22



## Textbook Example 4-3

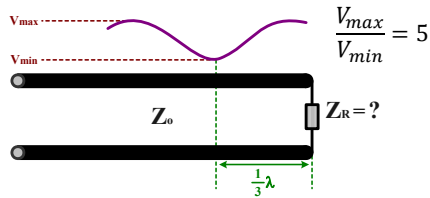


If the VSWR is measured to be 5 on a lossless, 50Ω line and a voltage minima occurs 1/3 of a wavelength from the load, determine the value of the load  $Z_R$ .

Therefore, rotate  $1/3\lambda$  from  $Z_{min}$  towards the load to find  $Z_R$ .

$$\bar{Z}_R = (0.77 + j1.48)\Omega$$

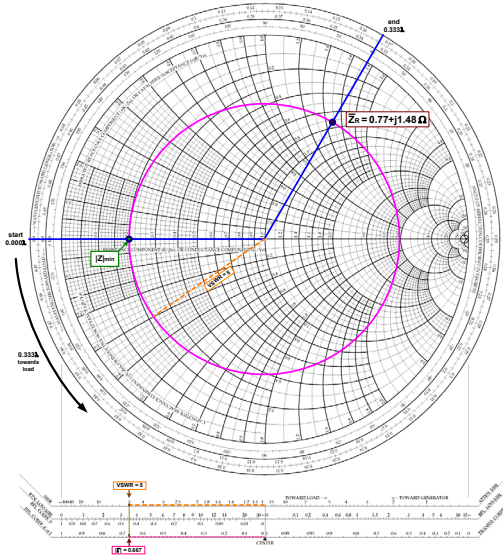
$$Z_R = \bar{Z}_R \cdot Z_o = (38.5 + j74)\Omega$$



23



## Textbook Example 4-5

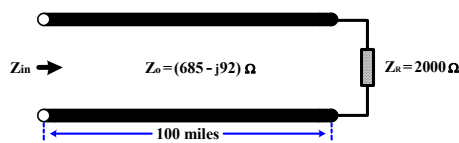


Determine the **input impedance** of a 100-mile long, lossy line that is terminated with a 2000Ω load if the line's propagation constant is:

$$\gamma = \alpha + j\beta = 0.00497 \frac{\text{nepers}}{\text{mile}} + j0.0352 \frac{\text{radians}}{\text{mile}}$$

and its **characteristic impedance** is:

$$Z_o = (685 - j92)\Omega$$

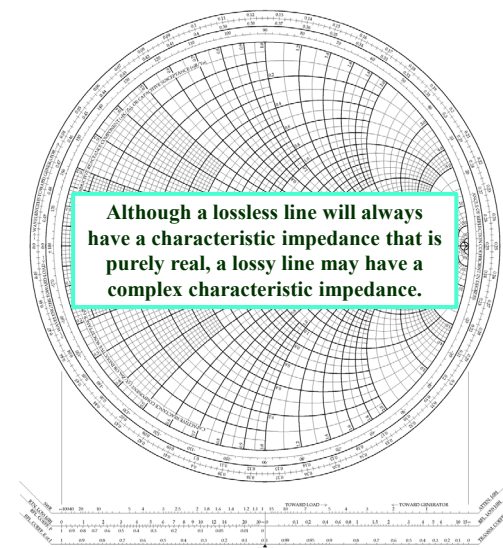


24






## Textbook Example 4-5

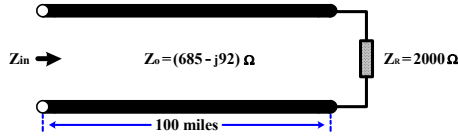

**Step 2: Normalize and plot the known load impedance.**

$$\bar{Z}_R = \frac{Z_R}{Z_o} = \frac{2000}{685 - j92} = (2.87 + j0.39)\Omega$$


Although it is not necessary to draw the constant  $|\Gamma|$  circle, it may help when performing the first part of the solution.

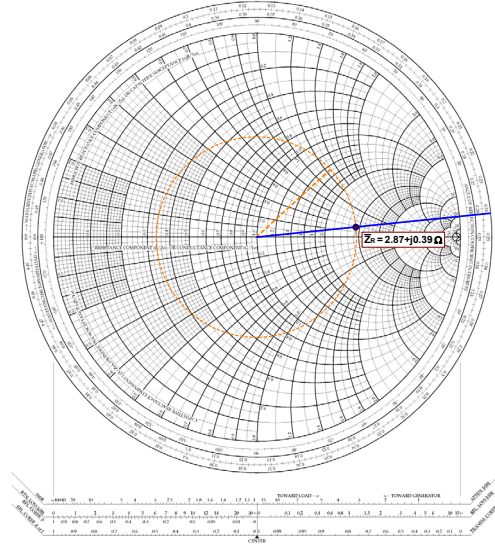

25




## Textbook Example 4-5

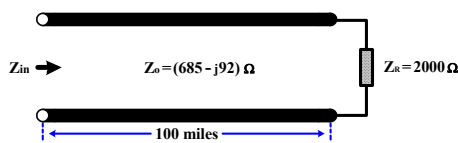

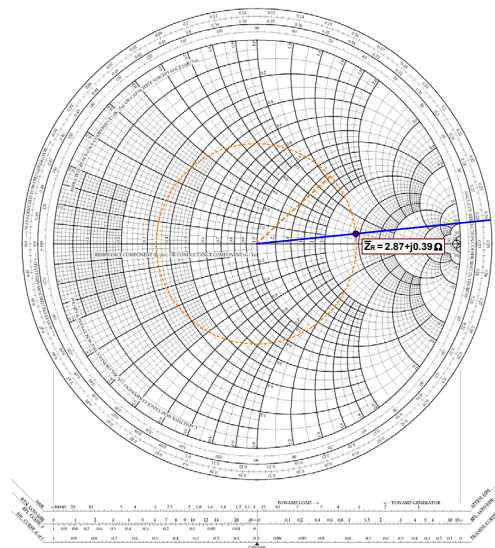**Step 3: Determine the length of the line in wavelengths:**

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.0352} = 178.4 \text{ miles}$$


$$L = \frac{100 \text{ miles}}{178.4 \frac{\text{miles}}{\text{wavelength}}} = 0.561 \text{ wavelengths}$$



26




## Textbook Example 4-5

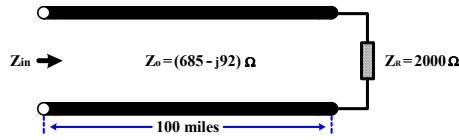

Step 4: Determine the starting and ending marker positions on the 1<sup>st</sup> band (Toward Generator).


START	0.242
length	+ 0.561
END	0.803
	- 0.500
Equivalent END	0.303

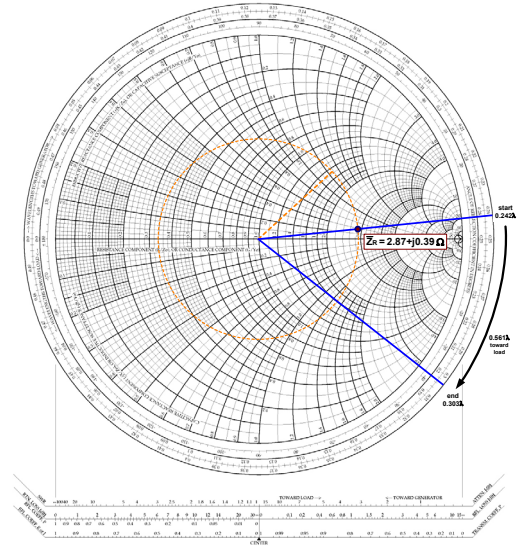

27




## Textbook Example 4-5

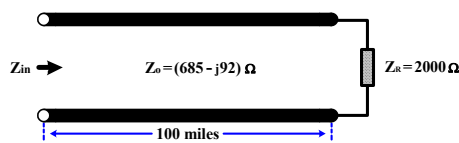

Note: If you determine the value of the impedance where the ending line crosses the constant  $|\Gamma|$  circle that passes through the normalized load, the result would be the normalized input impedance for a lossless line.

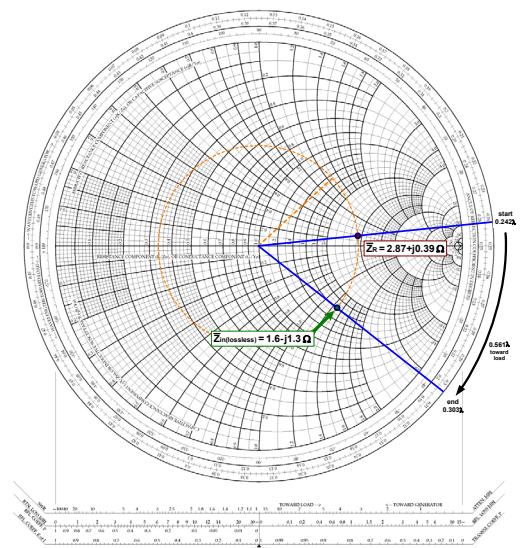
$$\bar{Z}_{in(\text{lossless})} = (1.6 - j1.3)\Omega$$



28




## Textbook Example 4-5

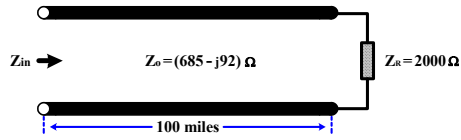

Step 5: Determine the  $|\Gamma_R|$  using the 3<sup>rd</sup> scale and calculate the  $|\Gamma_{in}|$ .


$$|\Gamma_R| = 0.49$$

$$\begin{aligned} |\Gamma_{in}| &= |\Gamma_R| e^{-2\alpha \cdot L} \\ &= (0.49) \cdot e^{-2 \cdot (0.00497) \cdot (100)} \\ &= (0.49) \cdot (0.37) = \mathbf{0.18} \end{aligned}$$

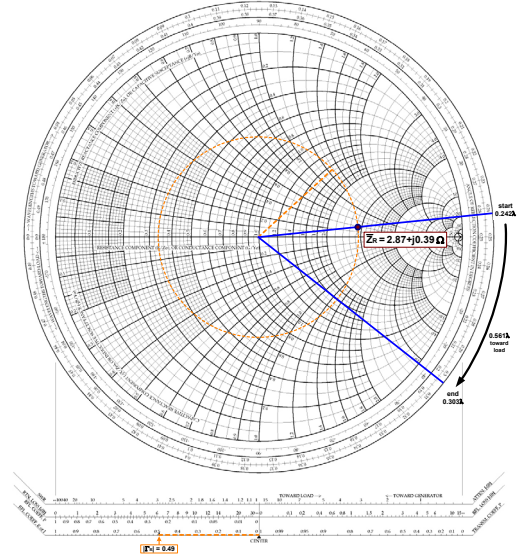

29

## Textbook Example 4-5

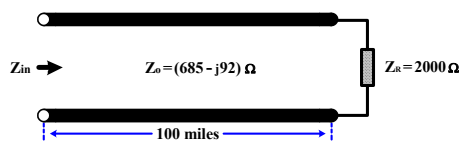


Step 6: Using the 3<sup>rd</sup> scale to determine the distance relating to  $|\Gamma_{in}|$ .

$Z_{in}$  will be located this distance from the origin on the ending line.

$$\bar{Z}_{in} = (1.3 - j0.31) \Omega$$

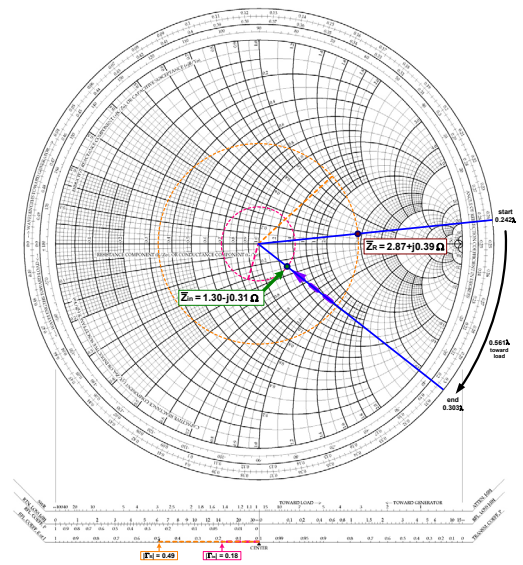
$$Z_{in} = \bar{Z}_{in} \cdot Z_o = (861 - j332) \Omega$$



30




## Textbook Example 5-1

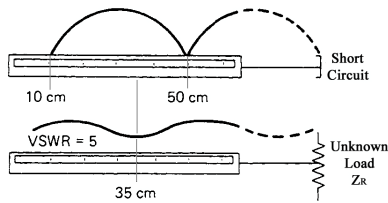

When a slotted-line is terminated with a short-circuit, voltage minima are detected at positions of 10cm and 50cm.

When the short-circuit is replaced by an unknown load, a voltage minimum is located at 35cm and the VSWR is 5.


Determine the value of the load  $Z_R$ .

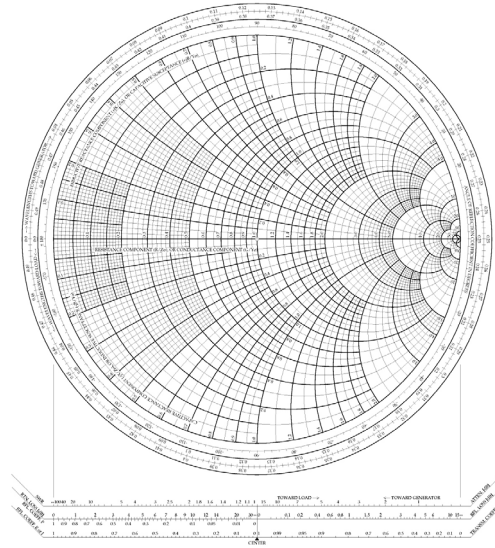

31




## Textbook Example 5-1

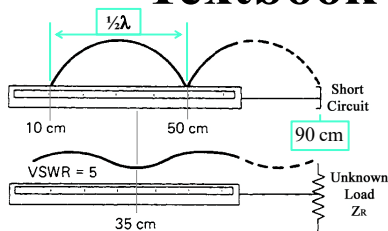

Since the standing-wave pattern repeats every  $\frac{1}{2}$  wavelength, then:

$$\lambda = 2 \cdot (50 - 10) = 80 \text{ cm}$$

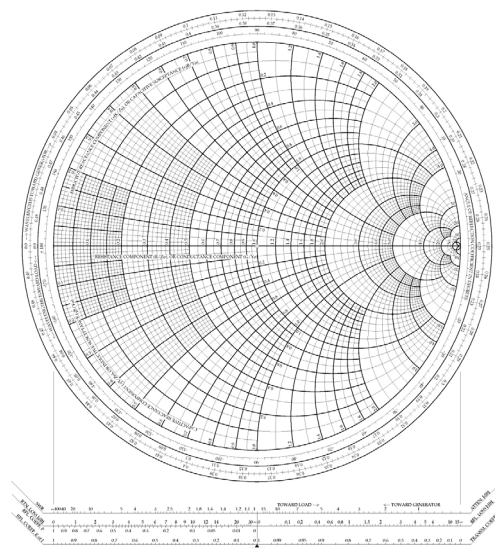Additionally, by extending the pattern in  $\frac{1}{2} \lambda$  increments, the location of the short-circuit is determined to be 90cm.




32






## Textbook Example 5-1

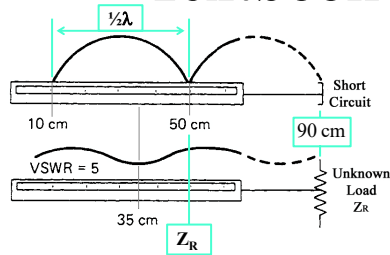

It is assumed that, when the short-circuit is replaced by the load  $Z_R$ , the load will also be located at the 90cm position.

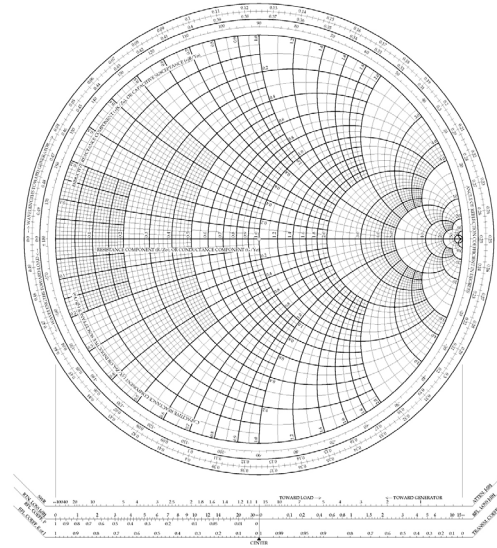
Furthermore, based on transmission-line theory, the same impedance should also be seen every  $\frac{1}{2}$  wavelength down the line... (at 50cm and 10cm).



33




## Textbook Example 5-1

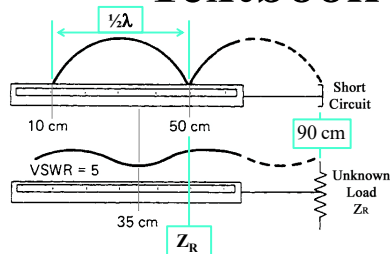

To determine the value of the load  $Z_R$ :

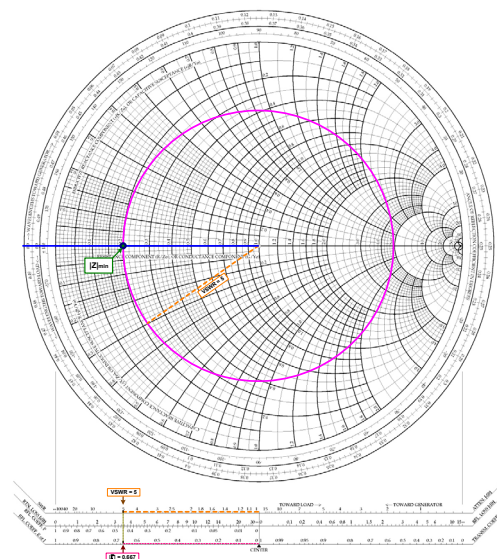- 1) Draw a circle on the Smith Chart that relates to a VSWR of 5.



Note that a minimum in the SWR pattern occurs whenever the magnitude of the impedance on the line is at a minimum, which occurs at marker 0.000 on the SC.



34



## Textbook Example 5-1

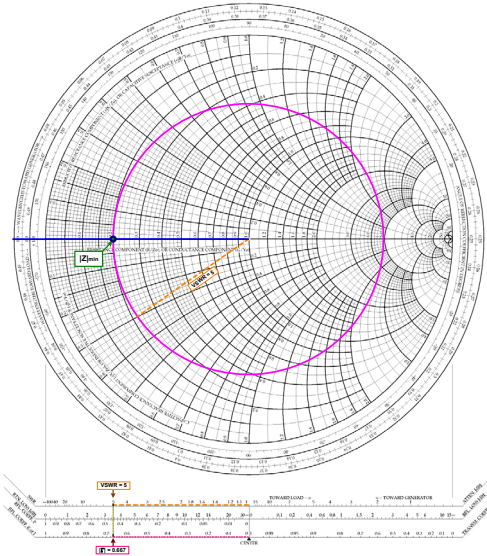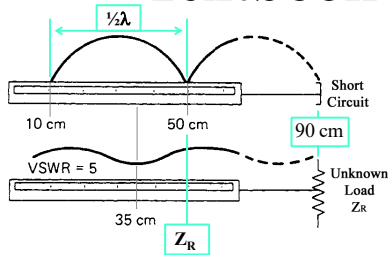

To determine the value of the load  $Z_R$ :



- Determine the distance from the load minimum to the location of the load impedance in wavelengths:

$$d = (50 - 35) = 15\text{cm} = \frac{15\text{cm}}{80 \frac{\text{cm}}{\lambda}} = 0.1875\lambda$$

35



## Textbook Example 5-1

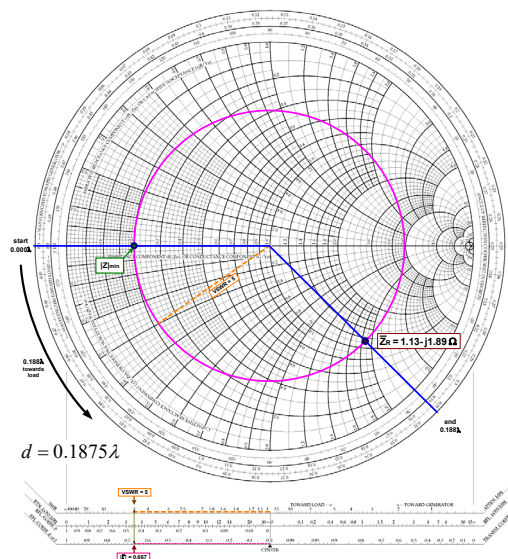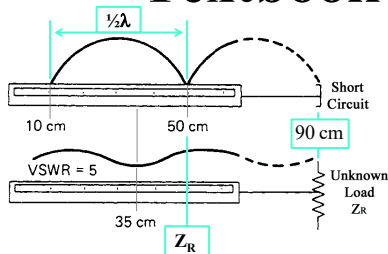

To determine the value of the load  $Z_R$ :

- Beginning at the minimum, rotate that distance (Toward the Load) on the SC to determine the load value:

$$\bar{Z}_R = (1.13 - j1.89)\Omega$$

$$Z_R = \bar{Z}_R \cdot Z_o = (56.5 - j94.5)\Omega$$

36