



# *ECET 3410*


## *High Frequency Systems*

# *Impedance Matching*

1



## Maximum Power Transfer

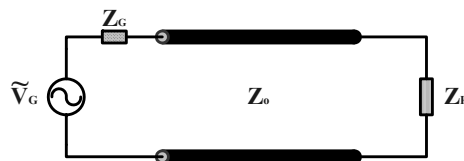

In order to deliver **maximum power** from the source to the load along a transmission line, both the source and load impedances must be **matched** to the characteristic impedance of the line (assuming all “real” values).


$$Z_G = Z_o = Z_R$$

This concept is equivalent to the Maximum Power Transfer Theorem that is typically presented during an introductory Circuits course.

2



## Maximum Power Transfer

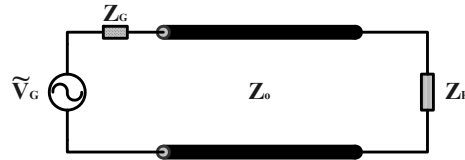

When a line is not matched to a source, less than maximum power will be transferred from the source onto the line.

**Commercial sources are typically well-matched to standard line impedances.**


When a load is not matched to a line, some of the incident power will reflect back toward the source, resulting in less than maximum power being transferred to the load.

**Devices connected to the end of a line are not always well-matched to the line.**

3



## Matching Networks

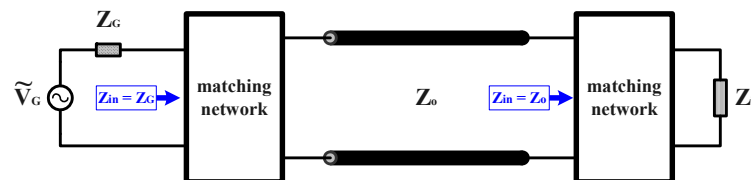

Whenever a transmission-line isn't fully matched, such that:

$$Z_G \neq Z_o \quad \text{and/or} \quad Z_R \neq Z_o$$


a **matching network** can be utilized at one or both ends of the line in order to transform the mismatched impedance(s) to the desired value(s), resulting in maximum power transfer from source  $\rightarrow$  line  $\rightarrow$  load.

4



# Impedance Matching Transformers

$$Z_{in} = a^2 \cdot Z_R$$

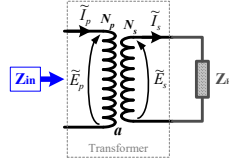

$$a = \frac{N_p}{N_s} = \frac{\tilde{E}_p}{\tilde{E}_s} = \frac{\tilde{I}_s}{\tilde{I}_p}$$

There are commercially available **impedance-matching transformers** that can be used to match “real” impedances at frequencies up to several hundred MHz.


Given an ideal transformer with turns-ratio “ $a$ ” and load  $Z_R$  connected across its secondary terminals, the input impedance of the transformer is:

$$Z_{in} = a^2 \cdot Z_R$$

5



# Impedance Matching Transformers

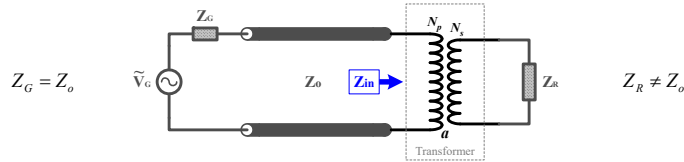

If a load  $Z_R$  is not matched to the line  $Z_o$ , an impedance matching transformer with turns-ratio “ $a$ ” can be placed between the load and the line, such that:

$$a = \sqrt{\frac{Z_o}{Z_R}}$$

$Z_R$  and  $Z_o$  must both be real values.


resulting in:

$$Z_{in} = Z_o$$

6



# Impedance Matching Transformers

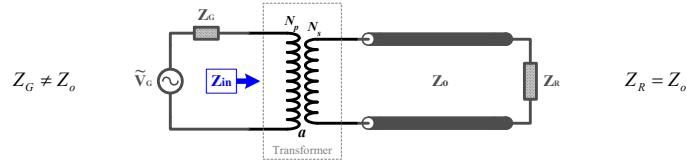

If a line  $Z_o$  is not matched to the source  $Z_G$ , an impedance matching transformer with turns-ratio “ $a$ ” can be placed between the source and the line, such that:

$$a = \sqrt{\frac{Z_G}{Z_o}}$$

$Z_G$  and  $Z_o$  must both be real values.

resulting in:


$$Z_{in} = Z_G$$

provided that the load is matched to the line

7



# Impedance Matching Transformers

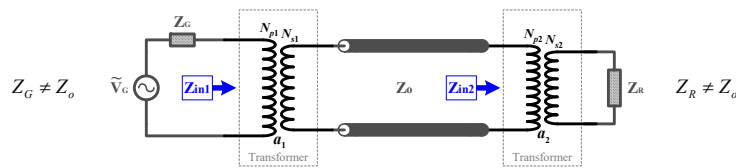

If the source  $Z_G$  and the load  $Z_R$  are not matched to the line  $Z_o$ , impedance matching transformers can be placed at ends of the line, such that:

$$a_1 = \sqrt{\frac{Z_G}{Z_o}} \quad a_2 = \sqrt{\frac{Z_o}{Z_R}}$$

$Z_R$ ,  $Z_G$  and  $Z_o$  must all be real values.


resulting in:

$$Z_{in1} = Z_G \quad Z_{in2} = Z_o$$

8


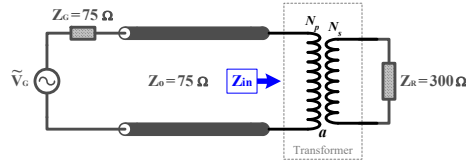
## Impedance Matching Transformer Example



Determine the **turns-ratio “a”** for an impedance matching transformer that can be used to match a 300Ω load to a standard 75Ω line:

$$a = \sqrt{\frac{Z_o}{Z_R}} = \sqrt{\frac{75}{300}} = \frac{1}{2}$$


$$Z_{in} = a^2 \cdot Z_R = \left(\frac{1}{2}\right)^2 \cdot 300 = 75 \Omega$$

Since the primary terminals of the transformer are connected to the receiving-end of the line, a matched load of 75Ω appears to be terminating the line.

9



## Impedance Matching Transformers

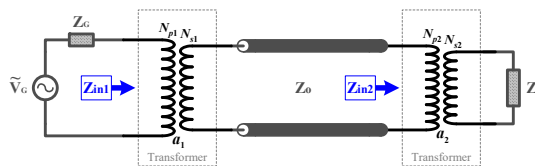

As previously noted, **impedance-matching transformers** that can be used to match “real” impedances at frequencies up to several hundred MHz are readily available.


But, above a few hundred MHz, the ferrite cores utilized in these transformers will often begin to saturate, causing the transformers to act in a non-linear manner, resulting in distortion of the applied signal or waveform.

The ferrite cores may also begin to saturate if the applied signal power becomes too large.

10



# Quarter Wavelength Tuners

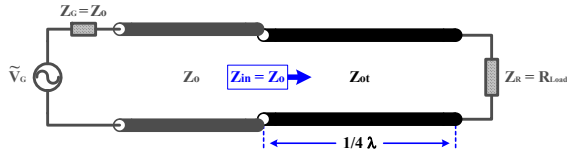

If  $Z_{ot}$  is not close to one of the standard characteristic impedances, it may be difficult to find a line section with the necessary impedance value.

A **Quarter Wavelength Tuner** can also be used to match a resistive load  $Z_R$  to any (purely real) line impedance value.

The tuner consists of a  $1/4$ -wavelength long section of line with characteristic impedance  $Z_{ot}$ , such that:


$$Z_{ot} = \sqrt{Z_{in} \cdot Z_R}$$

Note that the  $1/4$ - $\lambda$  Tuner is assumed to be lossless.

where:  $Z_{in}$  is the desired input impedance of the tuner. (i.e.  $Z_{in} = Z_o$ )



# Quarter Wavelength Tuner Example

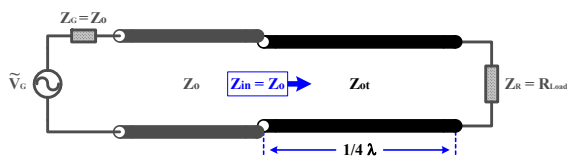


Design a  $1/4$  Wavelength Tuner to match a load of  $Z_R = 300\Omega$  to a  $75\Omega$  system using an air-filled line at 600MHz.

$$Z_{ot} = \sqrt{Z_{in} \cdot Z_R} = \sqrt{75 \cdot 300} = 150\Omega$$


$$\lambda = \frac{v}{f} = \frac{3 \cdot 10^8}{600 \cdot 10^6} = 0.5 \text{ m} = 50 \text{ cm}$$
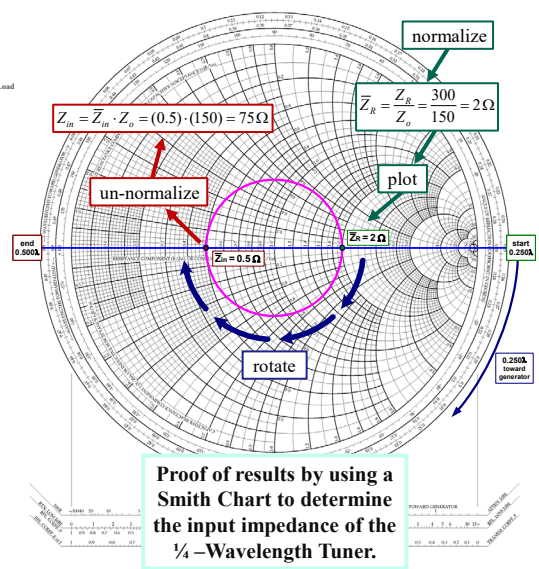
$$L = 0.25\lambda = (0.25) \cdot (50) = 12.5 \text{ cm}$$





## Quarter Wavelength Tuners

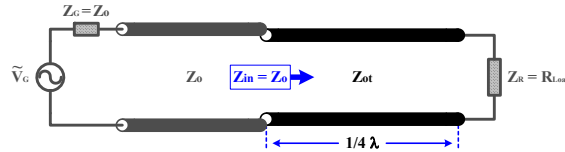

Since the actual (physical) length of a Quarter Wavelength Tuner is a function of the frequency of the applied waveform:

$$L = \frac{1}{4} \lambda = \frac{1}{4} \cdot \frac{v}{f}$$


each tuner is designed to operate at a specific frequency.

At both lower and higher frequencies, the length will no longer be  $\frac{1}{4}\lambda$ , resulting in a **limited operational bandwidth**.

13


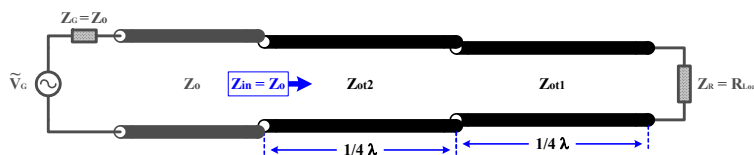
## Multi-Stage $\frac{1}{4}$ Wavelength Tuners



Multi-stage  $\frac{1}{4}$ - $\lambda$  Tuners will **NOT** appear on the course exams.

To reduce the narrow-band effect, multiple  $\frac{1}{4}$ -wavelength sections may be used, such as a 2-stage,  $\frac{1}{4}$  Wavelength Tuner shown in the above figure.


Each stage requires a different characteristic impedance. One choice of impedances that yields good bandwidth results is:

$$\left( \frac{Z_o}{Z_{ot2}} \right)^2 = \frac{Z_{ot2}}{Z_{ot1}} = \left( \frac{Z_{ot1}}{Z_R} \right)^2$$

14



# Single-Stub Tuners

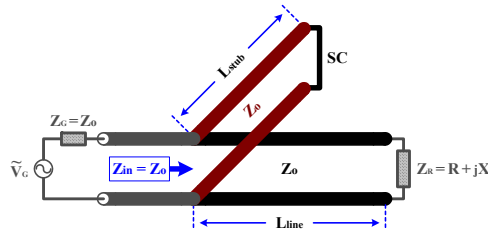

A **Single-Stub Tuner** is used to match a complex load  $Z_R = R + jX$  to any (purely real) system impedance using line sections that have the same characteristic impedance  $Z_o$  as the system.


This tuner consists of a short-circuited “stub” in-parallel with the sending-end of a “line” that is terminated by the load,  $Z_R$ .

15


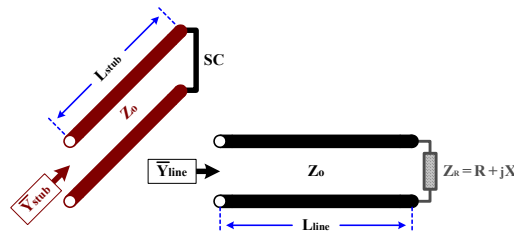
# Single-Stub Tuners

Remember that admittances add for parallel-connected circuit elements.



The length,  $L_{line}$ , is chosen such that the normalized input admittance of the “line” has a real value of one (1).

$$\bar{Y}_{line} = 1 + j\bar{B}_{line}$$

The length,  $L_{stub}$ , is chosen such that the “stub’s” normalized input admittance cancels the imaginary part of the “line’s” input admittance:


$$\bar{Y}_{stub} = -j\bar{B}_{line}$$

16





# Single-Stub Tuners

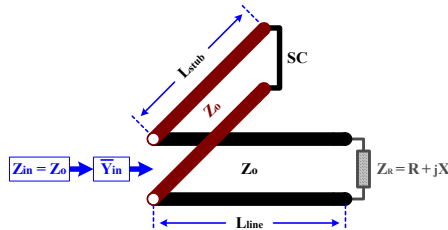

Since **admittances** add in parallel, given:

$$\bar{Y}_{line} = 1 + j\bar{B}_{line} \qquad \bar{Y}_{stub} = -j\bar{B}_{line}$$

then:

$$\bar{Y}_{in} = \bar{Y}_{line} + \bar{Y}_{stub} = (1 + j\bar{B}_{line}) + (-j\bar{B}_{line}) = 1$$

$$\bar{Z}_{in} = \frac{1}{\bar{Y}_{in}} = 1 \Rightarrow Z_{in} = \bar{Z}_{in} \cdot Z_o = 1 \cdot Z_o = Z_o$$


17



# Single-Stub Tuners – “Line” Length

TO DETERMINE THE “LINE” LENGTH:

- 1) Plot the normalized load  $\bar{Z}_R$  and reflect the impedance to the opposite side of a constant  $|\Gamma|$  circle to find the normalized load admittance  $\bar{Y}_R$ .

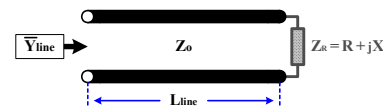

- 2) Rotate the normalized admittance around the constant  $|\Gamma|$  circle (towards generator) until it has a real value of one. This will be the normalized input admittance of the “line” section:

$$\bar{Y}_{line} = 1 + j\bar{B}_{line}$$

- 3) Set the length  $L_{line}$  equal to the distance that the “line” admittance was rotated around the constant  $|\Gamma|$  circle (in wavelengths).

18




# Single-Stub Tuners – “Stub” Length

TO DETERMINE THE “STUB” LENGTH:

- 1) Determine the imaginary value of the normalized input admittance of the “line”:

$$\bar{Y}_{line} = 1 + j\bar{B}_{line}$$

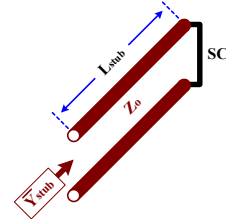

- 2) Starting at the point  $\bar{Y}_{SC} = \infty$ , rotate around the outer circle of the Smith Chart until the normalized input admittance of the “stub” section is equal to:


$$\bar{Y}_{stub} = -j\bar{B}_{line}$$

- 3) Set the length  $L_{stub}$  equal to the distance that the “stub” admittance was rotated around the outer circle (in wavelengths).

19




## Textbook Example 6-1

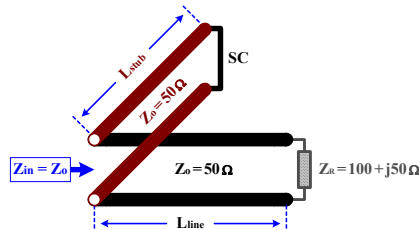

Design a **Single-Stub Tuner** to match a load of  $Z_R = (100 + j50)\Omega$  to a  $50\Omega$  source using  $50\Omega$  transmission line.

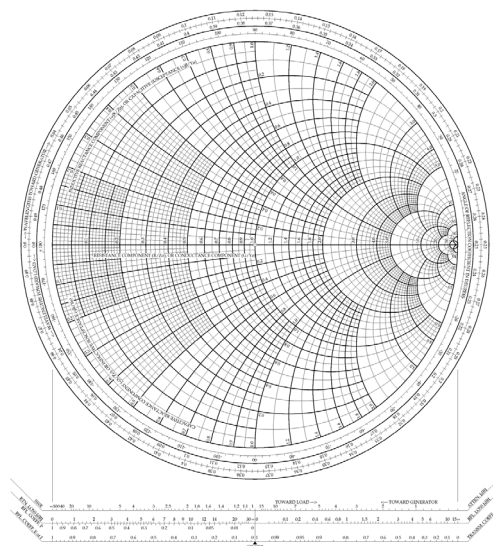
There are **two fundamental solutions** to this problem. One solution will be shown step-by-step in this presentation, followed by a summary of the results for the second solution.




20



## Textbook Example 6-1

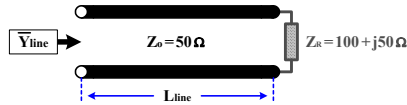


Step 1: Plot the normalized load  $\bar{Z}_R$  and reflect the impedance to the opposite side of a constant  $|\Gamma|$  circle to find the normalized load admittance  $\bar{Y}_R$ .

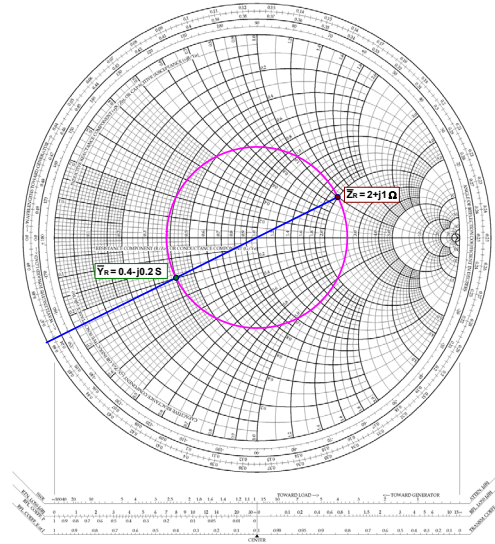

21




## Textbook Example 6-1

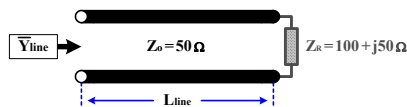

Step 2: Rotate the normalized load admittance  $\bar{Y}_R$  around the constant  $|\Gamma|$  circle it reaches the "Real = 1" circle such that:


$$\bar{Y}_{line} = 1 + j\bar{B}_{line}$$

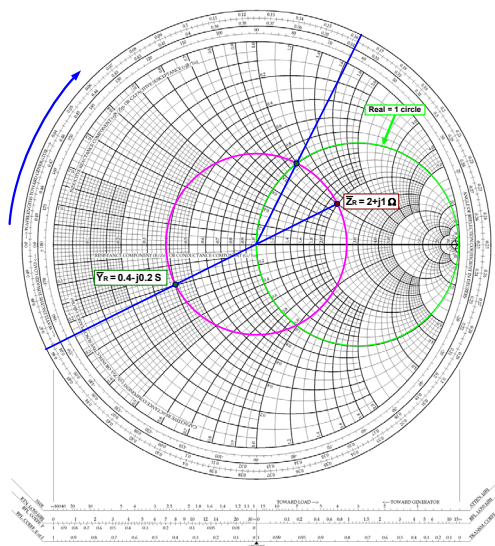

22




## Textbook Example 6-1

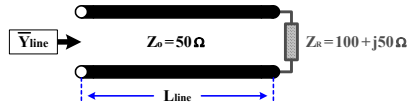

Step 3: Determine the length of the “line” section  $L_{line}$ :

$$\begin{aligned} \text{Line END} & \quad 0.662 \\ \text{Line START} & \quad - 0.463 \\ \hline L_{line} & \quad = 0.199 \lambda \end{aligned}$$

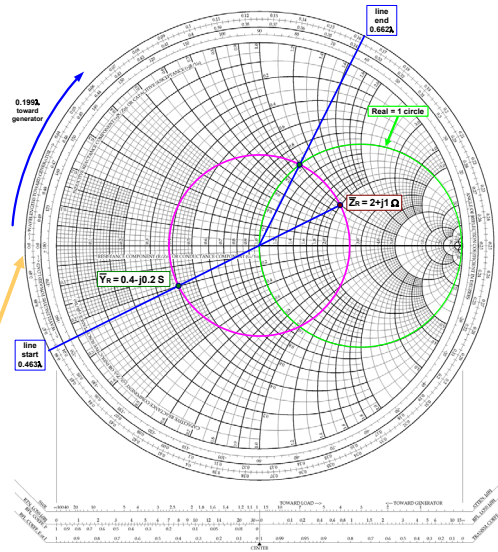
Since the normalized load admittance crossed the 0.000/0.500 marker as it rotated to the “Real = 1” circle, 0.500 should be added to the ending marker value to determine an effective ending position.



23




## Textbook Example 6-1

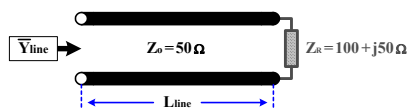

Step 4: Determine the value of the normalized line admittance  $\bar{Y}_{line}$ .

$$\begin{aligned} \bar{Y}_{line} & = 1 + j\bar{B}_{line} \\ & = 1 + j1 \end{aligned}$$


Note that the constant  $|\Gamma|$  circle also crosses the “Real = 1” circle at effective ending position 0.838, resulting in a 2<sup>nd</sup> theoretical solution.

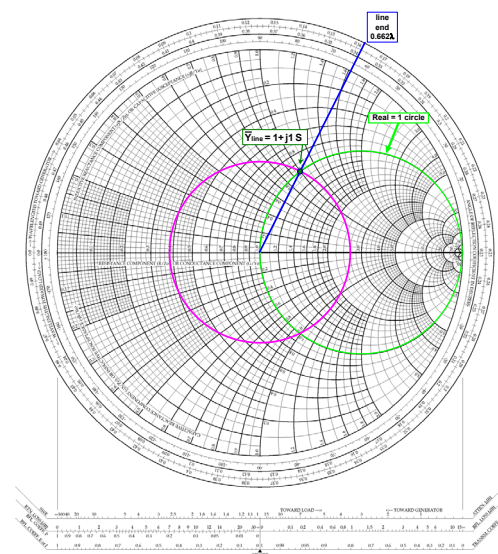

24




## Textbook Example 6-1

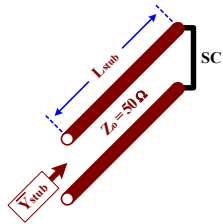

Step 5: Starting at the point  $\bar{Y}_{SC} = \infty$ , rotate around the outer circle of the Smith Chart until the normalized “stub” admittance is equal to:

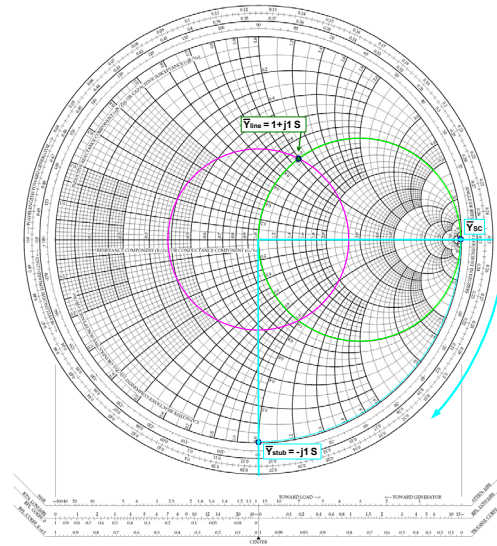
$$\begin{aligned}\bar{Y}_{stub} &= -j\bar{B}_{line} \\ &= -j1\end{aligned}$$



25




## Textbook Example 6-1

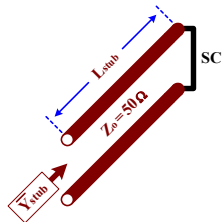

Step 6: Determine the length of the “stub” section  $L_{stub}$ :
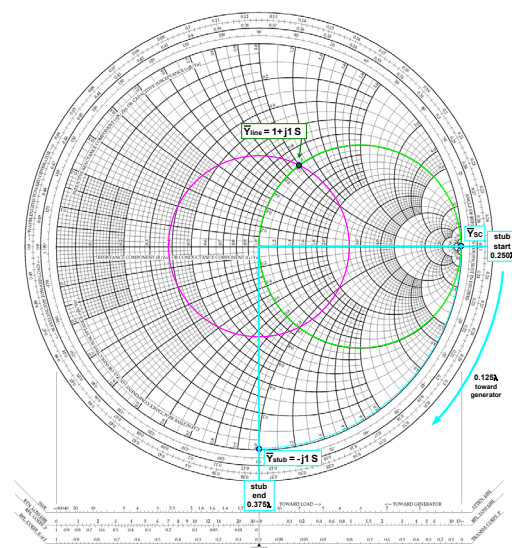
$$\begin{array}{rcl} \text{Stub END} & 0.374 & \\ \text{Stub START} & - 0.250 & \\ \hline L_{stub} & = & 0.125 \lambda \end{array}$$




26





## Textbook Example 6-1

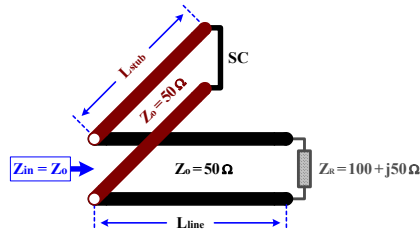


**Solution #1:**  $L_{line} = 0.199 \lambda$   
 $L_{stub} = 0.125 \lambda$

$$\bar{Y}_{line} = 1 + j1 \quad \bar{Y}_{stub} = -j1$$


$$\bar{Y}_{in} = \bar{Y}_{line} + \bar{Y}_{stub} = (1 + j1) + (-j1) = 1$$
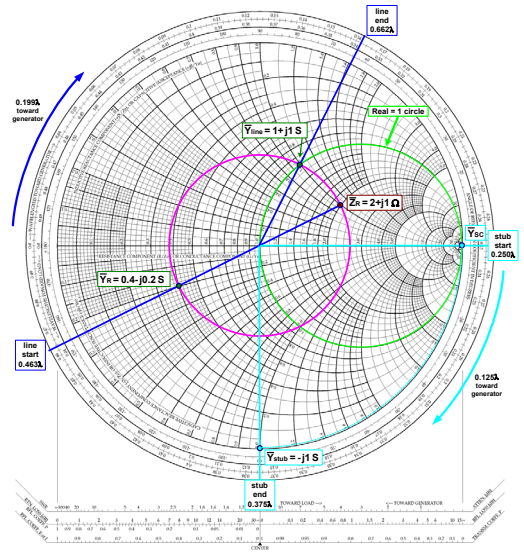
$$\bar{Z}_{in} = \frac{1}{\bar{Y}_{in}} = 1 \Omega \quad Z_{in} = \bar{Z}_{in} \cdot Z_o = 50 \Omega$$



27

## Textbook Example 6-1 Solution #2

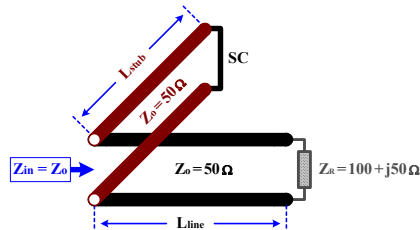


**Solution #2:**  $L_{line} = 0.375 \lambda$   
 $L_{stub} = 0.375 \lambda$

$$\bar{Y}_{line} = 1 - j1 \quad \bar{Y}_{stub} = +j1$$

$$\bar{Y}_{in} = \bar{Y}_{line} + \bar{Y}_{stub} = (1 - j1) + (+j1) = 1$$
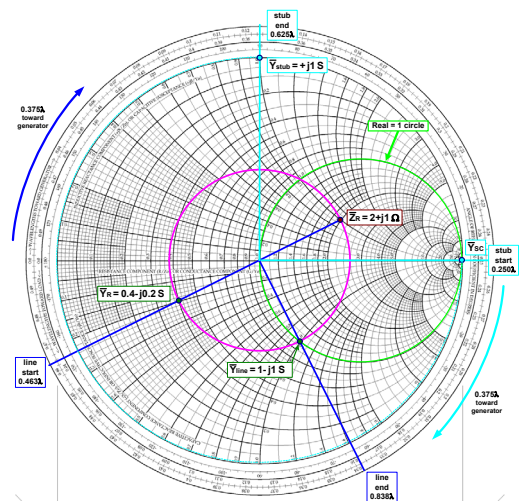
$$\bar{Z}_{in} = \frac{1}{\bar{Y}_{in}} = 1 \Omega \quad Z_{in} = \bar{Z}_{in} \cdot Z_o = 50 \Omega$$



The above Smith Chart shows the complete set of operations required to obtain Solution #2 for this problem.

28