

Instructions: This exam is closed book except for the reference booklet and one 8.5"x11" sheet of notes.

Assume an *ambient temperature of 30°C* if needed for all problems unless stated otherwise.

Problem #1) A three-phase, 208V branch circuit is serving a load that consumes both a continuous and a non-continuous amount of power as follows:

Load Ratings: 200V, 3Φ 25KVA, pf = 0.85 lagging, (continuous operation) $70.2A \times 1.25 = 87.75A$
 20KVA, pf = 0.85 lagging, (non-continuous operation) $57.7A$

a) Determine the *smallest, standard-sized circuit breaker* that can be used to protect this circuit.

$\sim 148A$ adjusted $\rightarrow 150A$ CB

CB rating = 150 A

$\therefore 90A$ adj.
SBA NC

b) Specify the *temperature rating* that should be applied to the conductors of this branch circuit based upon the rating of the load that it is serving. Justify your answer.

$> 100A \therefore 75^\circ C$

Temp rating = 75° °C


Justify your answer in the space below:

c) Specify the *smallest allowable size THHN, copper conductors* that can be utilized for this branch circuit assuming that the circuit is composed of three, individual conductors that are run through aluminum conduit, that the ambient temperature is 30°C, and that no other current-carrying conductors are run in the same conduit with this branch circuit.

Cu $\% 75^\circ C \rightarrow 150A$
no adjustments

Conductor Size = 1/0

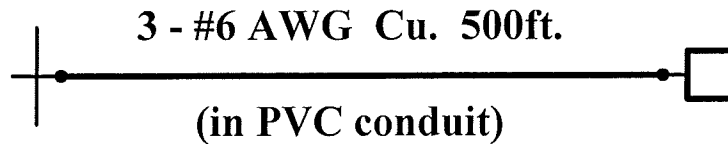Problem #2) Given a 3Φ, 208V branch circuit that consists of three individual, 500' long, #6 AWG, THHN, copper conductors (as shown in the figure below):



Need to account for

If the load supplied by the branch circuit is a continuous load that is rated at 200V, 15kVA and it operates with a power factor *pf = 0.85 lagging*, $43.3A \sim 43A$ actual $\leftarrow 60^\circ C$ Rating

a) Determine the *voltage-drop* that will occur across this branch circuit, in terms of the circuit's line-voltage, under rated-load conditions.

$R_{75} = 0.49$
 $R_{60} = 0.49 / (1 - 0.00123(60-75))$
 $= 0.466$

$$Z_c = (0.466)(0.75) + (0.001)(0.527) = 0.423 \text{ } \frac{\Omega}{1000'}$$

$$V_{drop} = \sqrt{3} \cdot 43 \cdot (0.423) \left(\frac{500}{1000} \right) = 15.75 \text{ V}_{line}$$

$$V_{drop(Line)} = \frac{15.75}{V}$$

$\frac{15.75}{208} \times 100 = 7.6\%$


b) Does the voltage-drop calculated in part (a) fall under *acceptable standards* as defined by the NEC? Justify/explain your answer:

Circle your answer \rightarrow Yes No

(Explain in the space below)

7.6% \leftarrow Total
 $1.25 \times 5\% = 6.25\%$
 $+ 3\% \text{ BC drop} = 9.25\%$

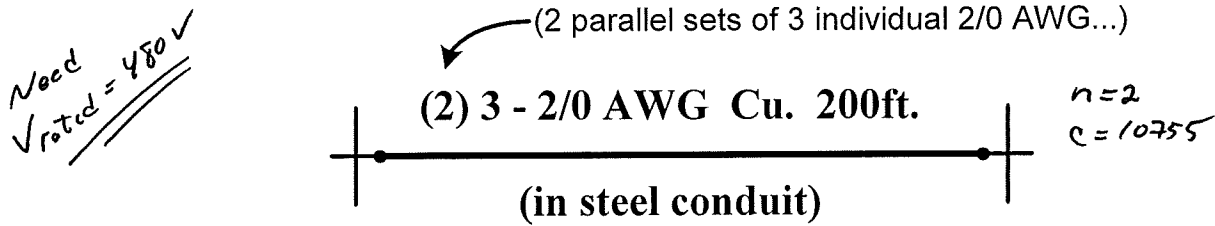Problem #3) Given a 3Φ feeder circuit that is composed of two parallel sets of 200' long, 2/0 AWG, THHN, copper conductors (as shown in the figure below):



If the L-L-L short-circuit current available at the “source-end” of the circuit is 12,000A

Determine the 3Φ, L-L-L *short circuit current* available at “load-end” of the 200’ circuit using the point-to-point method of calculation.

$$f = \frac{\sqrt{3} (200') (12000A)}{(10755) (2) (480)} = 0.4026$$

$$m = \frac{1}{1 + 0.4026} = 0.713 \quad I = (12000)(0.713) = 8555 A$$

$$I_{SCA(Load-End)} = \underline{8555} \text{ amps}$$

Problem #4) Given a 480V, 3Φ branch circuit that consists of three individual, 350kcmil, THHN, aluminum conductors fed that are fed through a steel conduit.

Determine the *AC resistance* and *reactance* of the conductors per 1000’ assuming an operational temperature of 90°C.

$$R_{25} = 0.063 \quad R_{90} = 0.063 (1 + 0.0039(90 - 75)) = 0.063 (1.0495) = 0.06612 \text{ } \Omega/1000'$$

$$R_{AC} = \underline{0.0661} \text{ } \Omega/1000'$$

$$X_L = 0.050$$

$$X_L = \underline{0.050} \text{ } \Omega/1000'$$

Problem #5) Given a 3Φ, 112.5kVA, 13.8kV–480V, Y-Y “step-down” transformer that provides service to an industrial building;

a) Determine the *rated phase-voltage* for the transformer’s secondary winding.

$$I_{R_{13.8kV}} = \frac{112500}{\sqrt{3} (13800)} = 135.3 \sim 135 A$$

$$\sqrt{3} V = \frac{480}{\sqrt{3}} = 277.1V$$

$$V_{Phase(rated)SECONDARY} = \underline{277} \text{ V}$$

b) Determine the *rated line-current* for the transformer’s primary and secondary windings.

$$I_{R_{13.8kV}} = \frac{112500}{\sqrt{3} (13800)} = 4.71 A$$

$$I_{Line(rated)PRIMARY} = \underline{4.71} \text{ A}$$

$$I_{Line(rated)SECONDARY} = \underline{135} \text{ A}$$

c) Assuming that an “infinite bus” supplies the transformer’s primary windings, determine the L-L-L *short-circuit current* available at the secondary terminals of the transformer.

Note – use “Table 1.2 – Impedance Data for 3Φ Transformers” that is provided in the reference booklet in order to get impedance information for this transformer.

$$112.5 \text{ kVA } 1\% Z \quad m = \frac{100\%}{1\%} = \frac{100}{1} = 100$$

$$I_{SCA} = I_{R_{13.8kV}} \cdot m = (135.3) \left(\frac{100\%}{1\%} \right) = 13530 A$$


$$I_{SCA(SEC)} = \underline{13530} \text{ A}$$

Problem #6) Given a raceway that contains three different, 3Φ, 3-wire (current-carrying) circuits, each of which are composed of three individual, #4 AWG, THHN, copper conductors. Determine the effective **ampacity** of the conductors if they have an operational temperature rating of 60°C and the ambient temperature is 42°C.

9 conductors - 70% 42°C amb - 0.71

#4 THHN C. @ 60°C → 70A × (0.7) × (0.71) = 34.8 ~ 35A Ampacity = 35 A

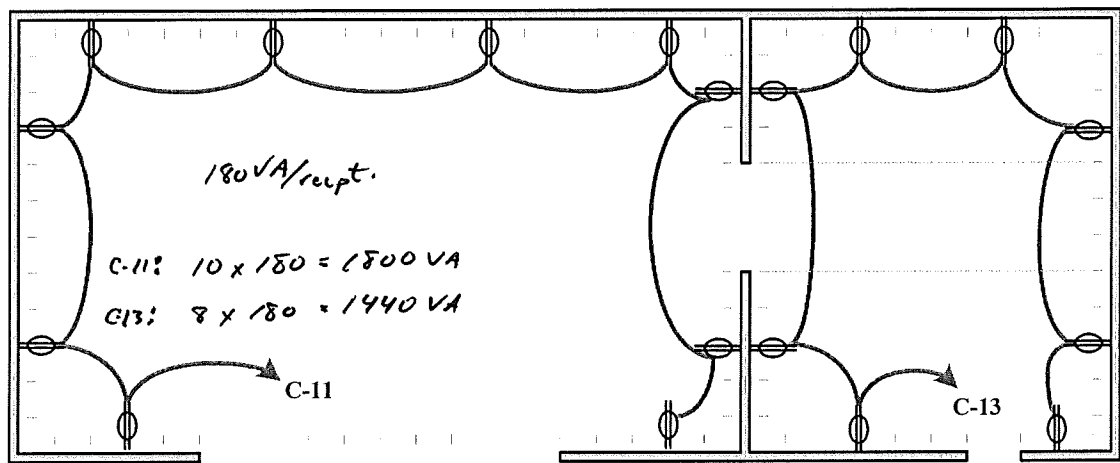Problem #7) The following figure shows the (120V, 1Φ) general purpose receptacles located within two rooms of a dwelling unit along with the circuits to which they are connected.



Based on NEC guidelines, determine the **minimum load rating** that can be applied to the circuits.

C-11 Load Rating = 1800 VA

C-13 Load Rating = 1440 VA

Problem #8) Specify if each statement is True or False based on NEC guidelines and/or standard design practice

FALSE Given a branch circuit that utilizes copper conductors, the **ampacity** of the conductors can be increased by switching from copper to aluminum without changing conductor size

FALSE Increasing the length of a conductor will cause its **ampacity** to decrease.

TRUE The **overcurrent protection device** protecting a branch circuit should always be placed at the “service-end” of the circuit conductors.

FALSE Both **THHN-type** and **TW-type** conductors can be used as the circuit conductors in circuits having a 60°C, 75°C or 90°C temperature rating.

TRUE An “**overload**” current refers to any larger than rated current that flows along the normally conductive paths of a circuit.

 A “**branch-circuit**” consists of a set of [?] conductors that carry all of the currents that flow into the individual load ~~branches~~ ^{branches} served by a specific panelboard.

FALSE The “**interrupting rating**” of an circuit breaker is the magnitude of the continuous circuit current above which will cause the circuit breaker to trip.