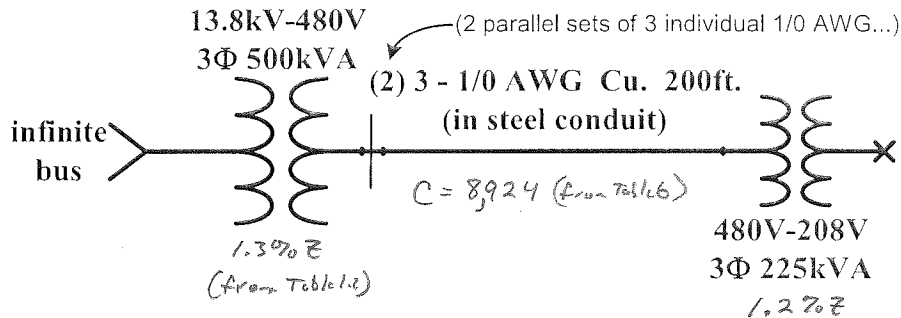


Industrial Distribution & NEC – Exam II pt. B Print Name (Last Name First):

Instructions: Part “B” of this exam is composed of a set of “take-home” problems that must be completed individually, under “closed-book” conditions, with absolutely no assistance from any other person or resource except for the PowerPoint slides provided on the course website.

Problem #9) Given the 3Φ distribution system shown in the following figure:

Note - Assume a 75°C terminal temperature rating and a 30°C ambient temperature.



a) Determine the 3Φ, L-L-L short circuit current available at the secondary terminals of the 500kVA transformer using the point-to-point method of calculation.

$$I_{FLA} = \frac{500,000}{\sqrt{3}(480)} = 601.4 \text{ A}$$

$$M = \frac{100\%}{1.3\%} = 76.9$$

$$I_{SCA} = I_{FLA} \cdot M = 46,262 \text{ A}$$

$$I_{SCA(SecT1)} = \underline{46,262} \text{ amps}$$

b) Determine the 3Φ, L-L-L short circuit current available at “load-end” of the 200’ feeder that connects the two transformers.

$$f = \frac{\sqrt{3}(200)(46,262)}{(8924)(2)(480)} = 1.87$$

$$M = \frac{1}{1+f} = \frac{1}{1+1.87} = 0.34836$$

$$I_{SCAF} = (46,262)(0.34836) = 16,116 \text{ A}$$

$$I_{SCA(Feeder)} = \underline{16,116} \text{ amps}$$

c) Determine the 3Φ, L-L-L short circuit current available at the secondary terminals of the 480-208V transformer using the point-to-point method of calculation.


$$f = \frac{\sqrt{3}(16,116)(480)(1.2)}{(500,000)(225)} = 0.7146$$

$$M = \frac{1}{1+0.7146} = 0.583$$

$$I_{SCA2} = (16,116)(0.583) \left(\frac{480}{208}\right) = 21,691 \text{ A}$$

$$I_{SCA(SecT2)} = \underline{21,691} \text{ amps}$$

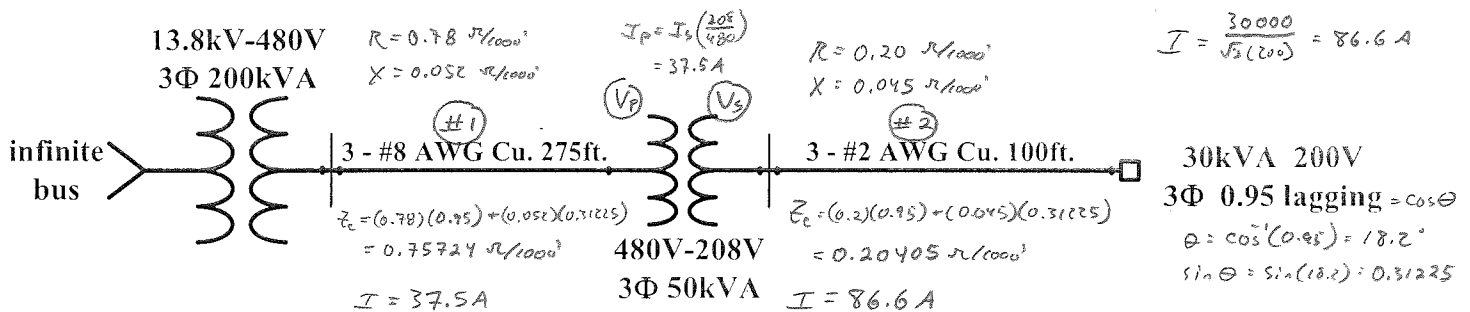Problem #10) Given the 3Φ distribution system shown in the following figure:



Neglecting any transformer losses, determine the operational line-voltage seen at the load outlet assuming that rated voltage is present at the secondary terminals of the 200kVA transformer and that the load is drawing rated power.

(Note – also assume that both circuits are fed through aluminum conduit and that the operational temperature of the circuit conductors is 60°C.)

Note: V_{drop} is 4% of “rated” line voltage @ load

$$V_{drop \#1} = \sqrt{3} I Z_c \frac{L}{1000} = \sqrt{3} (37.5)(0.75724) \frac{275}{1000} = 13.535 \text{ V}$$

$$V_P = 480 - 13.535 = 466.465 \text{ V} \quad V_S = V_P \left(\frac{208}{480}\right) = 202.135 \text{ V}$$

$$V_{Line(Load)} = \underline{199.1} \text{ volts}$$

$$V_{drop \#2} = \sqrt{3} (86.6)(0.20405) \left(\frac{100}{1000}\right) = 3.06 \text{ V} \quad V_{Load} = 202.135 - 3.06 = 199.07 \text{ V}$$