



# *ECET 4530*

## *Industrial Motor Control*

### *Introduction to Ladder Logic Programming I (in the RSLogix environment)*

1




## Ladder Logic Programming

Ladder Logic is one of many different languages\* that can be utilized when programming a PLC.

Ladder Logic programs take the form of a Ladder Diagram, the contents and structure of which defines the PLC's operation.

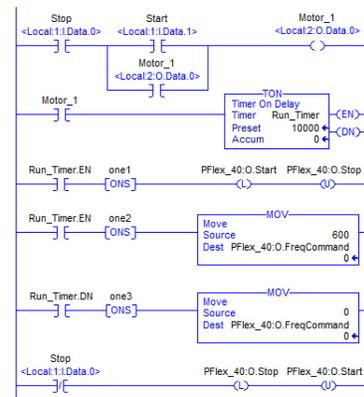A Graphical User Interface (GUI) is typically utilized in order to provide a simple drag-and-drop method for creation of the ladder diagram.



\* – other languages include Function Block Diagram (FBD), Instruction List (IL), Structured Text (ST), Sequential Function Chart (SFC), Continuous Function Chart (CFC), as well as high-level programming languages like Automation Basic and C++.

2




# Presentation Format – PPT I

This presentation on Ladder Logic Programming will begin by introducing the overall structure of a Ladder Diagram.

Included within the introduction is a brief discussion on the general types of Instructions that will appear within a Ladder Diagram, and the overall flow of the program as it is executed.

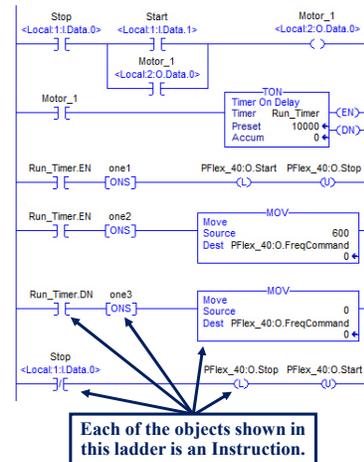Several commonly used Instructions will then be discussed in detail, including both the format of the instructions and their operation when utilized within a Ladder Logic Program.



3




# Presentation Format – PPT II

The second part of this presentation will focus on the practical implementation of Ladder Logic Programming in order to control the operation of a PLC.

The method for linking the operation of the PLC's Input and Output Ports to the operation of the Instructions within a Ladder Diagram will first be presented, after which several

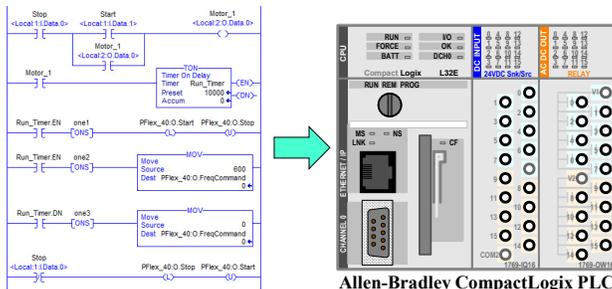basic control system tasks will be implemented with the use of Ladder Logic Programming.



4





# RSLogix/Studio 5000

**RSLogix 5000\*** is a platform developed by Rockwell Software for the programming of Allen-Bradley PLCs.

RSLogix 5000 (v.21) is shown in this presentation since we will utilize that software to program the PLCs in the lab.

Note that Ladder Logic is not exclusive to the RSLogix platform.

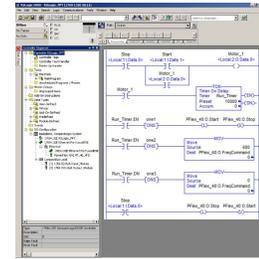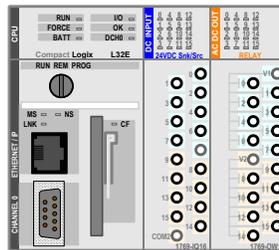It is a standardized programming language (IEC 61131-3) that has been adopted by all PLC manufacturers because of its structural similarity to relay-logic-based control circuits.



RSLogix 5000 Software Platform

\* – Studio 5000 is the new version of the RSLogix platform that was developed to support PLCs with multi-core processors. Although this presentation discusses RSLogix 5000, the contents also applies to the Studio 5000 platform.



(Part A)

## Ladder Diagrams




*Layout, Instruction Types,  
Evaluation, and Order of Execution*


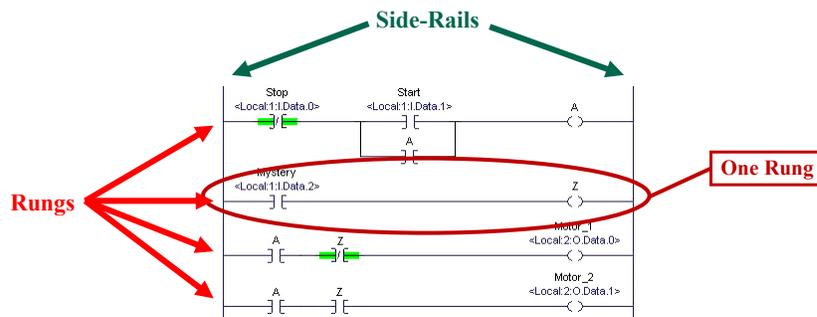
# Ladder Diagrams

Ladder Diagrams are graphical representations of a ladder logic program.

They are named such because of their ladder-like appearance, with two vertical Side-Rails and multiple horizontal Rungs.



7



## Ladder Diagrams – Rungs

The Rungs of the Ladder Diagram contain multiple Instructions that, when combined together, can provide the function of one or more lines of code in a text-based programming language.

For example, the function

let C=1 if (A=1 and B=0) else let C=0

can be implemented using either Ladder-Logic or C++ as:



Ladder Logic Rung

```

If ( A == 1 && B == 0 ) {
  C = 1
}
else {
  C = 0
}

```

C++ If-Else Statement


8


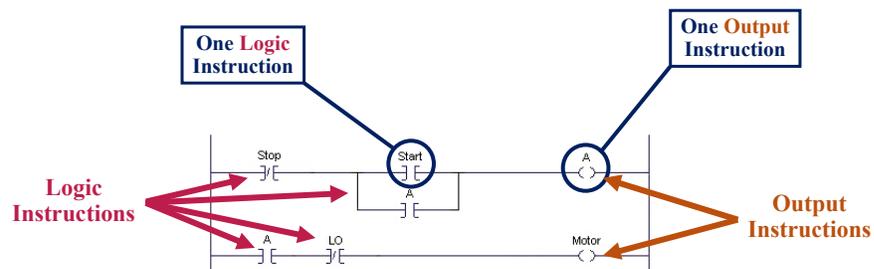
# Ladder Logic Instructions

Ladder Logic Instructions can be separated into two primary categories:

- **Output Instructions**
- **Logic (Input) Instructions**



9




# Output Instructions

Output Instructions perform a task.

The task performed may be simple or complex depending on the specific instruction, such as:

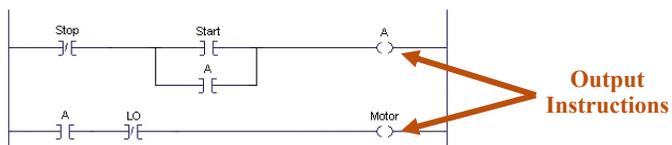- ✦ Changing the Value of a Number Stored in Memory
- ✦ Turning ON or OFF one of the PLC's Output Ports
- ✦ Operating as a Timer or a Counter
- ✦ Energizing or Changing the Output Frequency of a VFD



10



# Output Instructions

Output Instructions perform a task.

The task performed may be simple or complex depending on the specific instruction, such as:

- ✦ Changing the Value of a Number Stored in Memory
- ✦ Turning ON or OFF one of the PLC's Output Ports
- ✦ Operating as a Timer or a Counter
- ✦ Energizing or Changing the Output Frequency of a VFD

Note that all of these tasks involve manipulating the value of numbers that are stored in the memory of either the PLC or an external device.

11




# Logic Instructions

Logic Instructions provide the functional logic that controls the operation of the Output Instructions.

A **Logic Instruction** takes on either a **TRUE** or a **FALSE** state depending on the current state of its associated parameters.

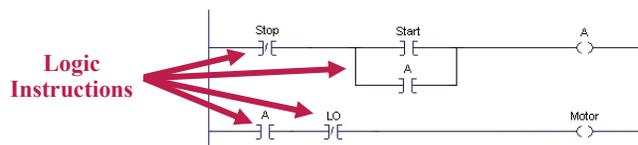In general, the “associated parameters” are one or more values stored in specific memory locations that are directly linked to a specific logic instruction.



12



## Rung Requirements

Each rung must have at least one **Output Instruction**.

An **Output Instruction** must occupy the right-most position\* on the rung.

Multiple **Output Instruction** may be placed in-series and/or in-parallel on the same rung.

Multiple **Logic Instructions** may be placed in-series and/or in-parallel on the same rung.

Each rung is not required to have any **Logic Instructions**.

\* – If multiple **Output Instructions** are placed on the same rung, **Logic Instructions** may be placed between those instructions provided that the right-most position on the rung is occupied by an **Output Instruction**. Note that rungs configured in this manner will not be covered in this presentation.

13



## Rung Condition

Rung Condition is a TRUE/FALSE logic state that is based on the state and placement of a rung's **Logic Instructions** and whether or not those instructions provide at least one path through **Logic Instructions** that are all **TRUE**, beginning from the left side-rail and progressing to the right.

It is actually the **Rung Condition** that governs the operation of any **Output Instructions** located on a specific rung.




14


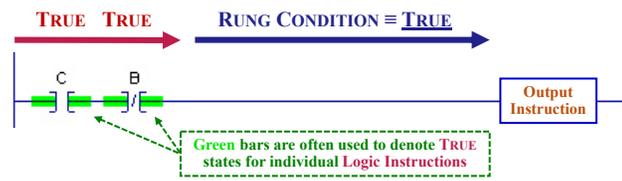
## TRUE Rung Condition

An **Output Instruction** experiences a **TRUE Rung Condition** when the rung's **Logic Instructions** provide a “**TRUE path**” from the left-hand side-rail of the ladder to the left side of the **Output Instruction**.




15


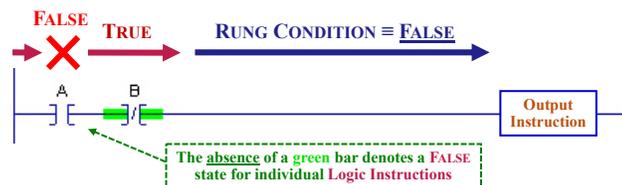
## FALSE Rung Condition

An **Output Instruction** experiences a **FALSE Rung Condition** when the rung's **Logic Instructions** prevent a “**TRUE path**” from the left-hand side-rail of the ladder to the left side of the **Output Instruction**.




16


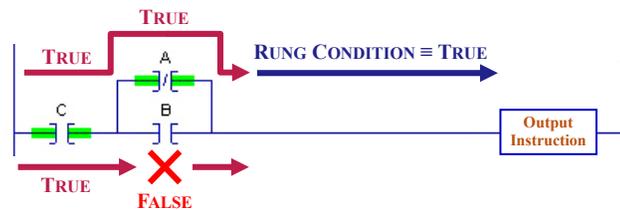
## Rung Condition

Note that the **Logic Instructions** placed on a rung may offer more than one potential path from the left-hand rail to an **Output Instruction**.

As long as at least one “**TRUE path**” exists, the **Rung Condition** for an **Output Instruction** is considered to be **TRUE**.




17


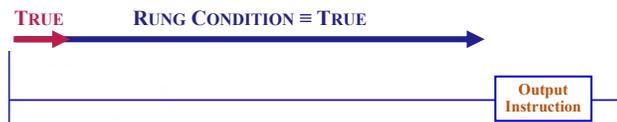
## Empty Rung Condition

When determining the **Rung Condition**, a rung is assumed to begin with a **TRUE** logic state at the left side-rail.

Because of this, a rung with no **Logic Instructions** will always return a **TRUE Rung Condition**.



18



## Rung Condition Evaluation Order

**Rung Condition** is not affected by an **Output Instruction** when progressing from left-to-right across a specific rung.

Thus, if a rung contains multiple **Output Instructions**, then:

- the **Rung Condition** for the left-most **Output Instruction** is determined first and the operation that instruction is completed, after which
- the process repeats for each additional **Output Instruction** on the rung until the right side-rail is reached.

19



## Rung Condition Evaluation Order

Even if the operation of an **Output Instruction** would change the state of the previously-evaluated **Logic Instructions**, those **Logic Instructions** will not be re-evaluated and the previously-determined **Rung Condition** (to the left) will remain unchanged until the next time the rung is executed.

On the other hand, an **Output Instruction** may affect the state of any **Logic Instructions** that are placed to its right on a rung, in-turn possibly affecting the **Rung Condition** that is experienced by any additional **Output Instructions** that are also placed to its right\*.

\* – This is a complex situation that will not be covered in this presentation.


20


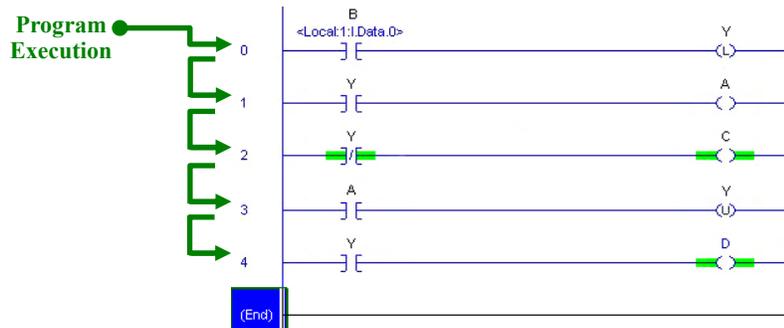
# Ladder Logic Program Execution

When a PLC is switched to **RUN** mode\*, the controller executes its ladder sequentially from top (Rung 0) to bottom (End), in the order that the rungs appear within the diagram.

\* – The PLC has two primary modes of operation, PROGRAM and **RUN**. When switched to PROGRAM mode, the controller stops executing its Ladder Logic program.




21


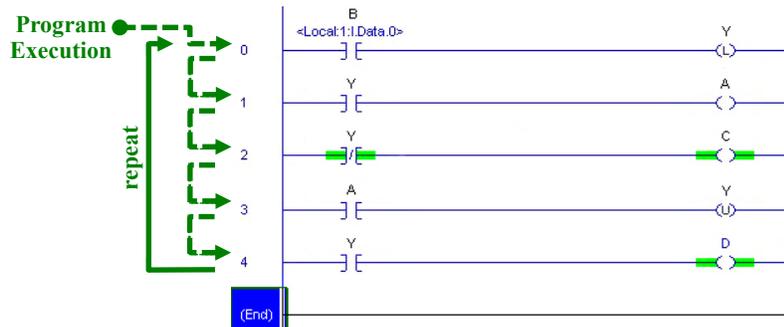
# Ladder Logic Program Execution

When the controller reaches the End rung, it jumps back to the top of the ladder (Rung 0) and the process begins again.

The controller will repetitively keep stepping through the ladder as long as the PLC remains in **RUN** mode.




22


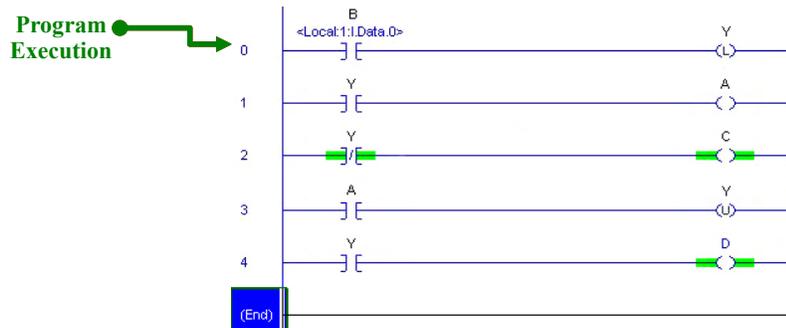
## Individual Rung Execution

Thus, beginning with Rung 0, the controller:

- Determines the **Rung-Condition** based on the state of the rung's **Logic Instructions**, and
- Completes any required tasks based on the **Rung-Condition** and the **Output Instruction(s)** on that rung.




23


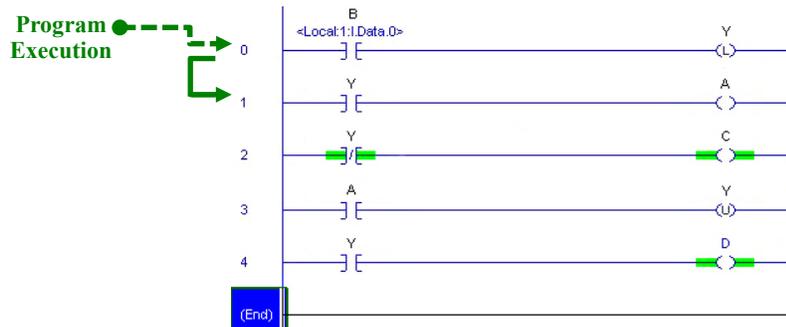
## Ladder Diagram Order of Execution

Once the controller completes the execution of a rung, it then moves to and executes the next rung by determining the **Rung Condition** on that rung and then applying the results to that rung's **Output Instruction(s)**.




24


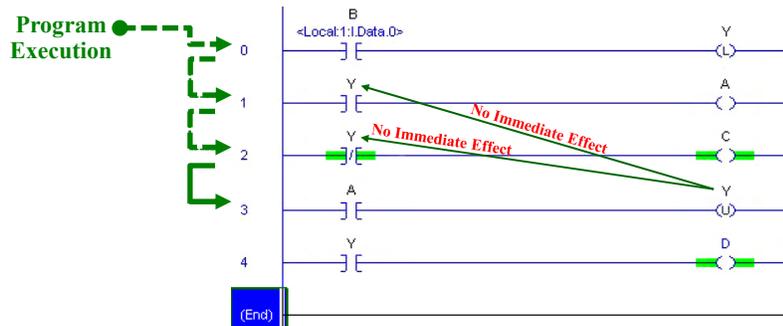
## Ladder Diagram Order of Execution

Although the execution of a rung may affect the state of the **Logic Instructions** on any previously-executed rungs, those changes are not acted upon until those rungs are re-executed.

I.e. – Once executed, a rung will not be re-evaluated until after the entire ladder has been executed and the controller sequentially steps through to that rung again.




25


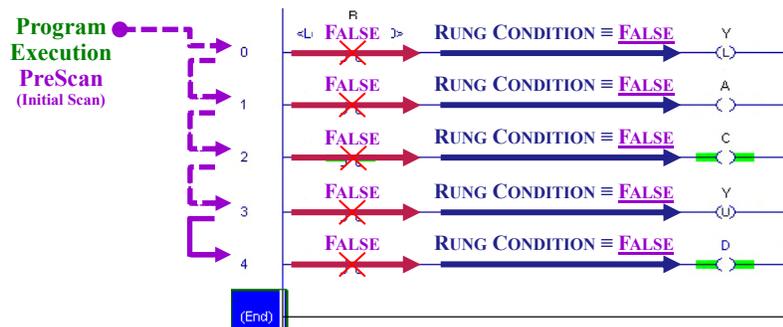
## PRESCAN Mode

Note that, if the PLC transitions from PROGRAM → RUN mode or if the PLC powers up in RUN mode, the **first (initial) scan** of the ladder diagram is executed in **PRESCAN** mode, during which all **Logic Instructions** return a **FALSE** state, in-turn resulting in all **FALSE Rung Conditions**.




26


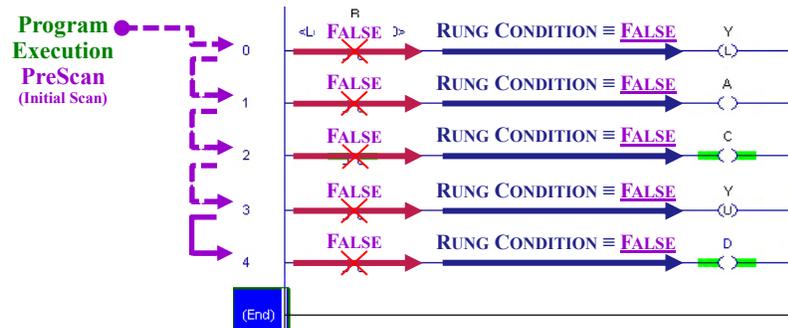
## PRESCAN Mode

Thus, for the first scan of the ladder, the operation of every **Output Instruction** is based upon a **FALSE Rung Condition**.

The significance of **PRESCAN** mode will not be apparent until the detailed operation of several Instructions is understood.



27



(Part B)

## *Ladder-Logic Instructions*

◆  
*Detailed Operation  
and Examples*

28



## Ladder Logic Instructions

The detailed operation of three, commonly used, Ladder Logic Instructions will now be presented:

- $\neg \text{[ ]}$  the **Examine if Closed (XIC)** instruction,
- $\neg \text{[ ]/}$  the **Examine if Open (XIO)** instruction, and
- $\text{-( )}$  the **Output Energize (OTE)** instruction.

Note – an analogy is often made between the look/operation of these instructions and that of a relay's Normally-Open (NO) contact, Normally-Closed (NC) contact, and Field Coil.

Although this analogy may be utilized during the associated lecture for this material, the analogy will NOT be discussed within this presentation because it can lead to several common misconceptions regarding their operation within a Ladder Diagram; instead, they will always be presented and discussed as “Instructions within a Ladder Logic Program”.

29



## Icons Used for Ladder Instructions


Note that the icon shown in this presentation for a various instruction will be the version displayed within the RSLogix (Allen-Bradley / Rockwell Software) environment.

Although other manufacturers (Siemens, Automation Direct, etc.) may use different icons, the overall operation of the various instructions should be consistent across the various platforms.


Shown below are some of the various Icons utilized for an “On-Delay Timer” in a Ladder Diagram:



RSLogix (Allen-Bradley)

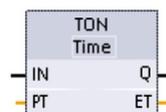

Siemens

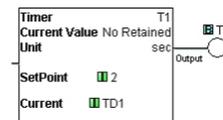

Automation Direct

30



## Logic Instructions – XIC

The **XIC (Examine If Closed)** instruction:



is a **Logic Instruction** that takes on either a **TRUE** or **FALSE** state depending on the value stored in a bit of memory.

But, in order to define the specific bit of memory upon which the **XIC**'s state is based, the **XIC** must be assigned a Tag.

An **XIC** is a Boolean instruction because it can only take on one of two states, **TRUE** or **FALSE**.


31


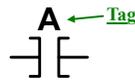
## Tags

Tags contain information that identifies and characterizes data stored in memory, allowing that data to be linked to the operation of one or more specific instructions.

For example, if the following **XIC** is assigned tag “A”:



The tag is displayed immediately above the icon for the instruction.

then Tag “A” identifies a specific bit in memory upon which this **XIC**'s state is based.

Tag “A” is a Boolean tag because it addresses a single bit that can only take on one of two values, **0** or **1**.

32



## Logic Instructions – XIC

If tag “A” is assigned to the **XIC (Examine If Closed)** instruction:



then the logic state (**TRUE** or **FALSE**) of that instruction is defined as follows:

When evaluated:  
(by the controller)

If bit A=1, then **XIC-A** → TRUE  
If bit A=0, then **XIC-A** → FALSE

The XIC is TRUE when A=1.

33



## Logic Instructions – XIO

The **XIO (Examine If Open)** Logic Instruction:



An **XIO** is also a Boolean instruction.

takes on the opposite state compared to that of an XIC.

If tag “B” is assigned to the **XIO**, then the logic state of this instruction (**TRUE** or **FALSE**) is defined as follows:

When evaluated:  
(by the controller)

If bit B=0, then **XIO-B** → TRUE  
If bit B=1, then **XIO-B** → FALSE

The XIO is TRUE when B≠1.

34





## Instructions – Icons vs. Current State

When a PLC is in **RUN** mode and its ladder diagram is being displayed (in real time) within the RSLogix environment:

- Instructions are always displayed by their standard icon
- The icons of **Logic Instructions** that return a **TRUE** state are highlighted with a **green-bar** behind their icons.

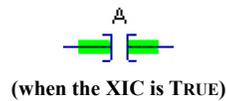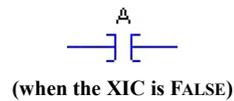Thus, given an XIC ( $\text{---} \overline{\text{---}} \text{---}$ ), it will be displayed as follows by the RSLogix software depending on its current logic state:



35



## Instructions – Icons vs. Current State


For example, given the bit values: **A = 0 B = 0 C = 1**  
and the following rungs:



If displayed while the PLC is in **RUN** mode, then:

**Rung-0:**     **XIC-A → FALSE,     XIO-B → TRUE**

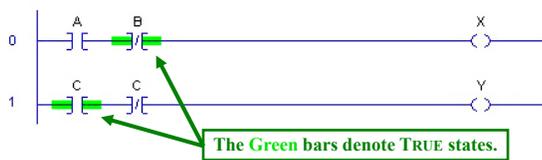**Rung-1:**     **XIC-C → TRUE,     XIO-C → FALSE**



36



## Output Instructions – OTE

The following **Output Instruction** is an **OTE (Output Energize)** instruction that has been assigned tag “C”:



An **OTE** will either set or reset (store a 1 or 0 in) the bit identified by its assigned tag based on the **Rung Condition** as follows:

If the **Rung Condition** is **TRUE**, then **OTE-C** sets bit C → 1  
(when evaluated by the controller)

If the **Rung Condition** is **FALSE**, then **OTE-C** resets bit C → 0

If a bit is “set”, it is changed to a one (1).  
If a bit is “reset”, it is changed to a zero (0).


37


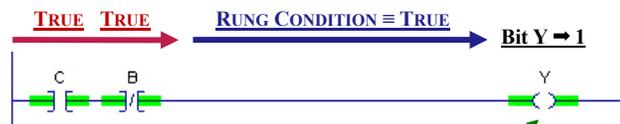
## OTE – TRUE Rung Condition

If the **Rung-Condition** for an **OTE** is **TRUE**, then the OTE will set its assigned bit to 1.

Thus, given the bit values: A = 0 B = 0 C = 1  
when the following rung is executed, both **XIC-C** and **XIO-B** will be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, in-turn causing the OTE to set bit Y → 1.



While displayed in real-time, a green bar behind a Boolean output instruction denotes that its assigned bit is a 1.

38



## OPE – FALSE Rung Condition

If the **Rung-Condition** for an **OPE** is **FALSE**, then the OPE will reset its assigned bit to 0.

Thus, given the bit values:  $A = 0$   $B = 0$   $C = 1$   
when the following rung is executed, both **XIC-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**, in-turn causing the OPE to reset bit  $X \rightarrow 0$ .



39



## OPE with Hold-In Example (Part 1)

Look closely at the following rung from a ladder diagram:



If bits A, B, and C are all zero ( $A=B=C=0$ ) when the rung is executed, **XIC-B** and **XIC-C** will both be evaluated **FALSE**, resulting in a **FALSE Rung Condition**.

Since the **Rung Condition** is **FALSE**, **OPE-C** resets bit  $C \rightarrow 0$ , and since bit  $C=0$ , the results will be the same the next time the rung is executed provided bit B remains zero ( $B=0$ ).

Since bit C was already a 0, it isn't changed.

Part 1 of Hold-In Example

40



Part 2 of Hold-In Example

## OPE with Hold-In Example (Part 2)

Given the same rung, what if bit B changes to a one ( $B \rightarrow 1$ ) and then the rung is executed again (assuming  $A=C=0$ )?

Then, the next time the rung is executed, **XIO-A** and **XIC-B** will both be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, and...




since the **Rung Condition** is now **TRUE**, **OPE-C** sets bit  $C \rightarrow 1$ .



(continued on the next slide)

41

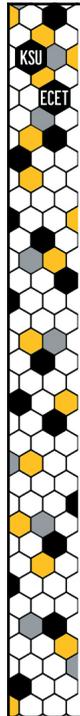

Part 2 of Hold-In Example (continued)

## OPE with Hold-In Example (Part 2)

Note that, although bit C is now one ( $C=1$ ), **XIC-C** is still shown to be **FALSE** (no green bar).



This is to highlight the fact that, once the state of a specific **Logic Instruction** is evaluated, it will not be re-evaluated until the rung is executed again.

But, once the rung is executed again, assuming that A and B remain unchanged, the rung will appear as:



42



Part 3 of Hold-In Example

## OTE with Hold-In Example (Part 3)

Now, given the current state of the rung ( $A=0, B=C=1$ ), what if bit B resets ( $B \rightarrow 0$ ) and then the rung is executed again?

Although **XIC-B** now evaluates **FALSE**, **XIO-A** and **XIC-C** still provide a **TRUE** path, maintaining the **TRUE Rung Condition**, and...



since the **Rung Condition** stays **TRUE**, **OTE-C** keeps bit C set.



43



Part 4 of Hold-In Example

## OTE with Hold-In Example (Part 4)

But, given the current state of the rung ( $A=B=0, C=1$ ), what if bit A changes to a one ( $A \rightarrow 1$ ) and the rung is executed again?

The next time the rung executes, **XIO-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**, and



since the **Rung Condition** is **FALSE**, **OTE-C** resets bit  $C \rightarrow 0$ .



(continued on the next slide)

44



## OTE with Hold-In Example (Part 4)

Note that, although C is now a zero ( $C=0$ ), **XIC-C** was still shown to be **TRUE** (with a **green bar**).




This is also to highlight that the state of the **Logic Instruction** is not re-evaluated until the rung is executed again.

But, if the rung is executed again and **XIC-C** is re-evaluated, the rung will appear as (assuming A and B remain unchanged):



Part 4 of Hold-In Example (continued)

45

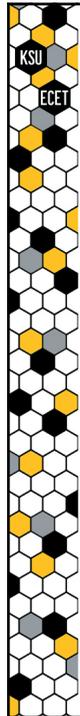

## OTE with Hold-In Example (Part 5)

And finally, what if bit A resets ( $A \rightarrow 0$ ) before the rung executes again?

The next time the rung executes, **XIO-A** will be evaluated **TRUE**, but the **Rung Condition** will remain **FALSE**.



Thus, the rung is back to the same overall state at that existed at the beginning of this example.



Part 5 of Hold-In Example

46


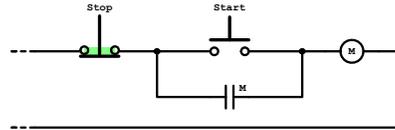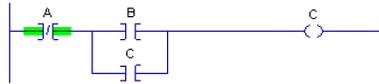
## OTE with Hold-In Example (Analysis)

Does the operation of the rung in this example remind you of the operation of a basic stop-start motor controller?




Analysis of Hold-In Example

This rung-structure is often used in a PLC-based control system for which a “hold-in” function is required.

The trick is to somehow associate the value of bit A with the state of a “Stop” button, the value of bit B with the state of a “Start” button, and the value of bit C with the state of a contactor’s field coil. How this is done will be discussed in Part B of this presentation.

47

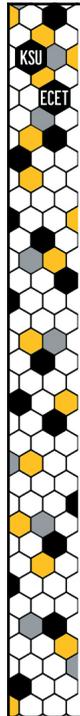

## Ladder Logic Instructions

Although many programming tasks can be completed using just the following three instructions:

- $\rightarrow$  [ ] the **Examine if Closed (XIC)** instruction,
- $\rightarrow$  [ / ] the **Examine if Open (XIO)** instruction, and
- $\rightarrow$  ( ) the **Output Energize (OTE)** instruction.

a handful of other instructions will also be presented in order to provide a solid foundation of Ladder Logic knowledge upon which the required programming tasks for a wide variety of PLC-based motor control systems can be implemented.

48



# Output Latch (OTL)

## OTL – Output Latch



An **Output Latch (OTL)** is an **Output Instruction** that can set a bit (B → 1) but cannot reset a bit back to zero.

If the **Rung-Condition** is **TRUE**, then **OTL-B** sets\* bit B → 1 (when evaluated by the controller)

If the **Rung-Condition** is **FALSE**, then **OTL-B** does nothing.

\* – It is often stated that an **OTL** “latches” a bit. The problem with this statement is that, in electronic circuits, a latch is a device that “sets and holds” a voltage at a specific level. It is true that the **OTL** can “set” a bit, but it doesn’t “hold” the bit at a value of one. Instead, it doesn’t have the ability to “reset” a bit, so even if the **Rung Condition** returns **FALSE**, the bit will remain set until it is actively reset by another instruction.



# OTL Example


Given the following rung that contains one **OTL (Output Latch)**:




If bit A changes to a one (A = 1), then the next time that the rung is executed, **XIC-A** will be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, and



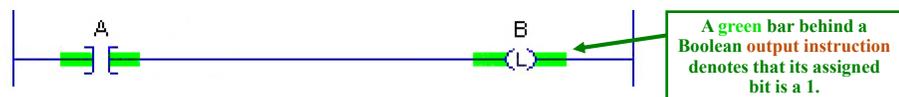since the **Rung Condition** is **TRUE**, **OTL-B** sets bit B → 1.



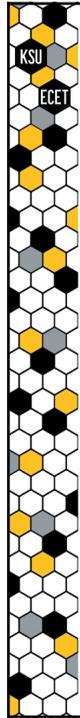

## OTL Example

On the other hand, given the following rung:




If bit A resets ( $A=0$ ), then the next time that the rung is executed, **XIC-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**.



But, **OTL-B** does nothing when the **Rung Condition** is **FALSE**, so bit **B** remains set ( $B=1$ ).

51

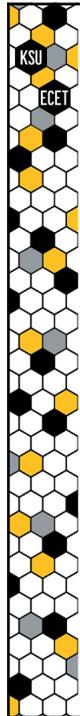

## Output Unlatch (OTU)

**OTU – Output Unlatch**



An **Output Unlatch (OTU)** is an **Output Instruction** that can reset a bit ( $B \rightarrow 0$ ) but cannot set a bit to a one.

If the **Rung-Condition** is **TRUE**, then **OTU-B** resets\* bit  $B \rightarrow 0$   
(when evaluated by the controller)

If the **Rung-Condition** is **FALSE**, then **OTU-B** does nothing.

\* – Note that the **OTU** resets a bit when the **Rung Condition** becomes **TRUE**. On the other hand, an **OTE** resets a bit when the **Rung Condition** becomes **FALSE**. This is a critical distinction between the abilities of **OTUs** and **OTEs** to reset a bit, and often provides a challenge for beginning Ladder Logic programmers.

52



## OTU Example

Given a rung that contains on **OTU (Output Unlatch)** ( $A=0, B=1$ ):



If bit A changes to a one ( $A=1$ ), then the next time that the rung is executed, **XIC-A** will be evaluated **TRUE**, resulting in a **TRUE Rung Condition**, and



since the **Rung Condition** is **TRUE**, **OTU-B** resets bit  $B \rightarrow 0$ .



53



## OTU Example

Given the same rung when  $A=1$  and  $B=0$ :



If bit A resets ( $A=0$ ), then the next time that the rung is executed, **XIC-A** will be evaluated **FALSE**, resulting in a **FALSE Rung Condition**.




But, **OTU-B** does nothing when the **Rung Condition** is **FALSE**, so bit B remains reset ( $B=0$ ).

54



# On-Delay Timer (TON)

## TON – On-Delay Timer

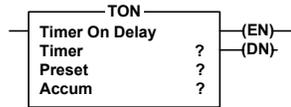

The On-Delay Timer (TON) is an **Output Instruction** that functions as a “non-retentive” timer.


A non-retentive timer is a timer that does not retain its count (accumulator value) if the timer is disabled.

(I.e. – the timer resets to its initial conditions when it is disabled)



# TON – Base Tag & Sub-Tags

## TON – On-Delay Timer

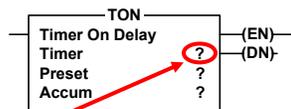

When a **Base Tag** is created for the **TON**, the name of which appears in the *Timer* field, several sub-Tags are automatically created by the RSLogix software:


The sub-Tags include:

- |                     |                    |                    |
|---------------------|--------------------|--------------------|
| <i>Base_Tag.PRE</i> | <i>Base_Tag.EN</i> | <i>Base_Tag.TT</i> |
| <i>Base_Tag.ACC</i> | <i>Base_Tag.DN</i> |                    |



# TON – Preset & Accumulator

## TON – On-Delay Timer

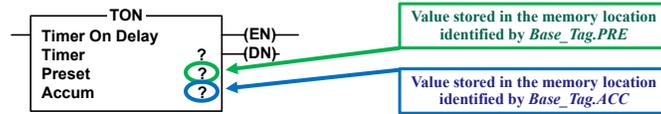

In addition to the *Timer* field that contains the Base Tag name, there are two user-defined fields shown in the icon:

- *Preset* – Contains the time-delay value (specified in msec) up to which the **TON** will count.  
(.PRE)
- *Accum* – Contains the initial time value (also in msec).  
(.ACC)

Note that the *Accum* field displays the current value stored in the accumulator when viewed “online” (in real time).



# TON – Operational State Bits

## TON – On-Delay Timer




Three sub-Tags characterize the **TON**'s operational state:

- *Base\_Tag.EN* – The *.EN* (Enable) bit is set to 1 when the **TON** is enabled and reset to 0 when it's disabled.
- *Base\_Tag.DN* – The *.DN* (Done) bit is set to 1 when the *Accum* equals the *Preset*, otherwise it's reset to 0.
- *Base\_Tag.TT* – The *.TT* (Time Transitioning) bit is set to 1 when the **TON** is actively counting, otherwise it's reset to 0.



# TON – Documentation

## TON – On-Delay Timer

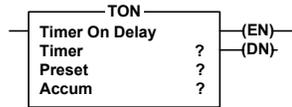


The following information can be found by using the Help tab within the RSLogix 5000 software:

Instruction:	Relay Ladder:	Function Block:	Structured Text:	Description:
TON Timer On Delay		see TONR	see TONR	The TON instruction is a non-retentive timer that accumulates time when the instruction is enabled (rung-condition-in is true).
Operand:	Type:	Format:	Description:	
Timer	TIMER	tag	timer structure	
Preset	DINT	immediate	how long to delay (accumulate time)	
Accum	DINT	immediate	number of msec the timer has counted; initial value is typically 0	
Arithmetic Status Flags:		Major Faults:		
not affected		Type 4	Code 34	<ul style="list-style-type: none"> <li>• PRE &lt; 0</li> <li>• ACC &lt; 0</li> </ul>



# TON – Detailed Operation

## TON – On-Delay Timer

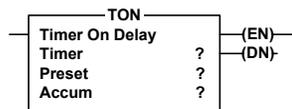

The **TON** is “enabled” when its **Rung Condition** is **TRUE**.


Once enabled, its *Enable* bit is set ( $.EN \rightarrow 1$ ) and the **TON** begins “actively” incrementing (accumulating time).

Note that, if the **Rung Condition** goes **FALSE**, the **TON** is disabled, causing its accumulator to return to its initial value (the default is 0) and the *Enable* bit to reset ( $.EN \rightarrow 0$ ).



# TON – Detailed Operation

## TON – On-Delay Timer

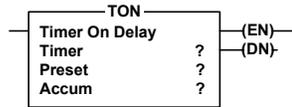

As long as the **TON** remains enabled, its accumulator will continue incrementing until it reaches the *Preset* value.


Note that, while the **TON** is “actively” accumulating time, the *Time Transitioning* bit will be set ( $.TT \rightarrow 1$ ).

But, if the **TON** is not accumulating time, either because it’s disabled or its accumulator has reached the *Preset* value, then the *.TT* bit will be reset ( $.TT \rightarrow 0$ ).



# TON – Detailed Operation

## TON – On-Delay Timer

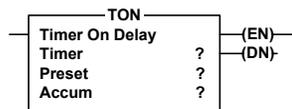

Once the **TON’s** accumulator reaches the *Preset* value, it will stop incrementing and the *Accum* value will remain equal to the *Preset* value as long as the timer is enabled.


Additionally, as long as  $.ACC = .PRE$ , the timer’s *Done* bit will be set ( $.DN \rightarrow 1$ ).

But, if for any reason  $.ACC \neq .PRE$ , such as the timer being disabled or reset, the *Done* bit will be reset ( $.DN \rightarrow 0$ ).


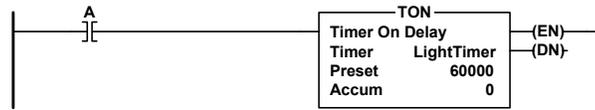
## TON Example

Given the **TON** that has been placed on a rung with **XIC-A**:



If the timer is configured as follows:

- the name of the Base Tag is “LightTimer”,
- the *Preset* value is 60,000 (60,000 msec = 60 sec), and
- the initial *Accum* value is 0.

describe, in detail:


- 1) the timer’s initial conditions while bit A = 0,
- 2) the operation of the timer when bit A is set (A → 1), and
- 3) the operation of the timer if bit A is reset (A → 0).

63


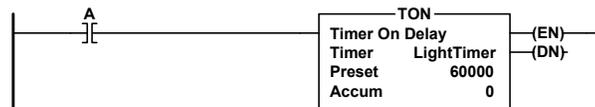
## TON Example – Initial Conditions

Given the **TON** that has been placed on a rung with **XIC-A**:



<i>LightTimer.EN</i> = 0 <i>LightTimer.TT</i> = 0 <i>LightTimer.DN</i> = 0
--

If bit A is initially zero (A=0), then:

- **XIC-A** ≡ **FALSE** and the **Rung Condition** is **FALSE**, and
- the **TON** is disabled.

Since the timer is disabled:


- the status bits *Enable*, *Time Transitioning*, and *Done* will all be zero (*.EN*=0, *.TT*=0, *.DN*=0), and
- the accumulator value will remain at zero (*.ACC*=0).

64


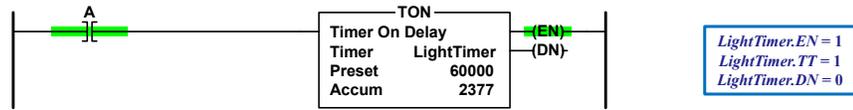
## TON Example – Timer Enabled

Given the **TON** that has been placed on a rung with **XIC-A**:



If bit **A**  $\rightarrow$  1, then the next time the rung is executed, **XIC-A** will be evaluated **TRUE**, making the **Rung Condition TRUE**, and the **TON** will be enabled.

When the timer is enabled:


- the *Enable* bit will be set ( $.EN \rightarrow 1$ ),
- the accumulator will begin incrementing, and
- the *Time Transitioning* bit will be set ( $.TT \rightarrow 1$ ).

65


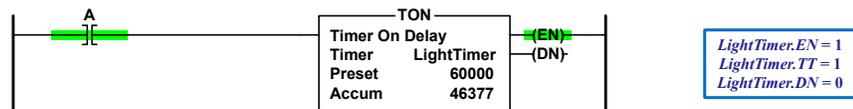
## TON Example – Time Transitioning

Given the **TON** that has been placed on a rung with **XIC-A**:



As long as the **TON** remains enabled and the *Accum* value is less than the *Preset* value ( $.ACC < 60,000$ ), then accumulator will keep incrementing until it reaches the *Preset* value.

Thus, while the accumulator is incrementing:


- the *Enable* bit will remain set ( $.EN = 1$ ), and
- the *Time Transitioning* bit will remain set ( $.TT = 1$ ).

66


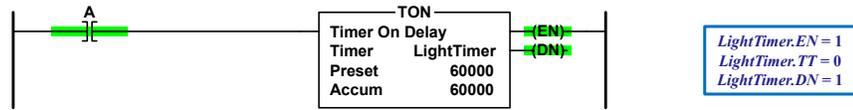
## TON Example – Timer Done

Given the **TON** that has been placed on a rung with **XIC-A**:



When the *Accum* value reaches the *Preset* value ( $.ACC=60,000$ ), which will occur 60 seconds after the timer is enabled:

- the accumulator stops incrementing and remains at 60,000,
- the *Enable* bit will remain set ( $.EN=1$ ),
- the *Time Transitioning* bit will reset ( $.TT \rightarrow 0$ ), and
- the *Done* bit will be set ( $.DN \rightarrow 1$ ).


The timer will remain in this “done” state until it is either disabled (i.e. – the Rung Condition goes FALSE) or reset by a RES instruction.

67


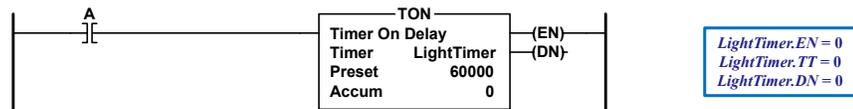
## TON Example – Timer Done

Given the **TON** that has been placed on a rung with **XIC-A**:



At any point in time, if bit  $A \rightarrow 0$ , then the next time the rung is executed, **XIC-A** will be evaluated **FALSE**, making the **Rung Condition FALSE**, and the **TON** will be disabled.

If the timer is disabled:

- the *Enable* bit will be reset ( $.EN \rightarrow 0$ ),
- the accumulator will reset back to its initial value,
- the *Done* bit will be reset ( $.DN \rightarrow 0$ ), and
- the *Time Transitioning* bit will be reset ( $.TT \rightarrow 0$ ) if it was set.

68



# Reset (RES)

## RES – Reset



The **Reset** instruction is an **Output Instruction** that can be used to reset the accumulator (.ACC) and the status bits (.EN, .DN, .TT) of a timer or a counter.

The Base Tag (name) associated with either the timer or counter that the **RES** instruction is being used to reset must be placed in the **Reset's tag field**.

For example, a **RES** instruction could be used to reset **LightTimer's** accumulator if assigned the tag **LightTimer**.

69



# RES – Operation

## RES – Reset



The operation of the **Reset** instruction is based upon the **Rung Condition** on the rung.

When the rung is executed:

if the **Rung Condition** is **TRUE**, the **RES** will reset the status bits of its assigned timer, and it will reset the timer's accumulator back to its initial value, or


if the **Rung Condition** is **FALSE**, the **RES** does nothing.

70


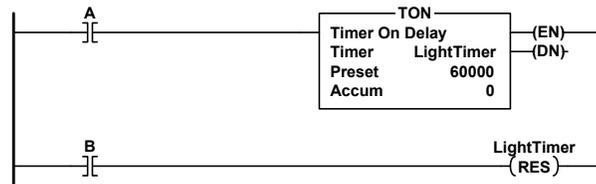
## RES Example (with TON)

Given the following rungs that contain a **TON** and a **RES**:



If bits A and B are initially both zero ( $A=B=0$ ):


- ⇒ the **Rung Conditions** for both rungs are **FALSE**
- ⇒ the **TON** is disabled
- ⇒ the **RES** instruction does nothing

71


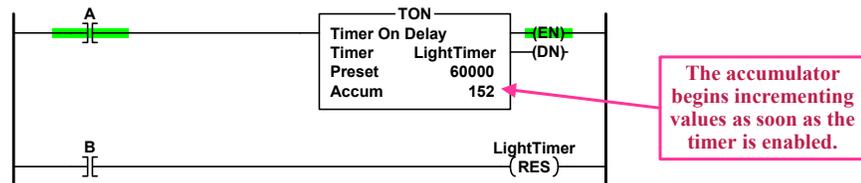
## RES Example – TON Enabled

Given the following rungs that contain a **TON** and a **RES**:




- If bit A → 1
- ⇒ **XIC-A** ≡ **TRUE**
  - ⇒ the **Rung Condition** for the **TON** is **TRUE**
  - ⇒ **TON-LightTimer** is enabled
  - ⇒ the timer's *Enable* bit is set ( $.EN \rightarrow 1$ )
  - ⇒ the timer's accumulator begins incrementing
  - ⇒ the timer's *Time Transitioning* bit is set ( $.TT \rightarrow 1$ )

72


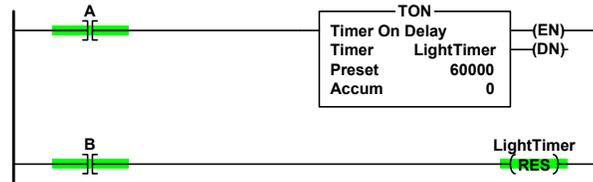
## RES Example – TON Reset

Given the following rungs that contain a **TON** and a **RES**:




- If bit B → 1
- ⇒ **XIC-B** ≡ **TRUE**
  - ⇒ the **Rung Condition** for the **RES** is **TRUE**
  - ⇒ the **RES** resets **LightTimer's** status bits and it resets **LightTimer's** accumulator back to its initial value

73


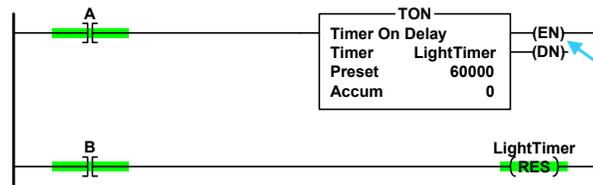
## RES Example – TON Reset

Given the following rungs that contain a **TON** and a **RES**:



Note that, since the software used to display the state of the ladder in “real-time” only has a limited refresh rate, the **.EN** bit may be highlighted green as if set, unhighlighted as if reset, or intermittently change back and forth depending on the actual layout of the ladder diagram.

- If bits A and B both remain set (A=B=1):
- ⇒ when the **TON's** rung is executed, the timer's **.EN** bit will be set, and the timer will begin accumulating, but
  - ⇒ when the **RES's** rung is executed, the **RES** timer will be reset again, and the process will repeat.


This can be confusing if the two rungs are not located next to each other in the ladder diagram because it might appear as if the **TON** is disabled despite its **TRUE Rung Condition**.

74


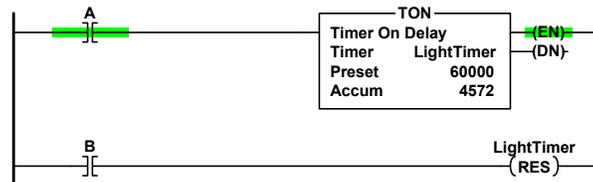
## RES Example – TON re-Enabled

Given the following rungs that contain a **TON** and a **RES**:



- If bit B → 0
- ⇒ **XIC-B** ≡ **FALSE**
  - ⇒ the **Rung Condition** for the **RES** is **FALSE**
  - ⇒ the **RES** does nothing
  - ⇒ since the **Rung Condition** for the timer is **TRUE**, the next time the **TON's** rung is executed, the timer will be re-enabled, and its accumulator will begin incrementing again.

75



## Numerical Comparison Instructions

There are many **Logic Instructions** available the return either **TRUE** or **FALSE** states based on a comparison of two values.

These instructions include:

- **GRT** – Greater Than
- **GEQ** – Greater Than or Equal To
- **LES** – Less Than
- **LEQ** – Less Than or Equal To
- **EQU** – Equal To
- **NEQ** – Not Equal To


Only the **Greater Than (GRT)** instruction is covered in this presentation since the other comparison-type instructions function similarly.

76



# Greater Than (GRT)

## GRT – Greater Than

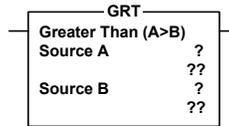

The **GRT (Greater Than)** instruction is used to compare the values of two numbers, A and B.


- If  $A > B$ , then the **GRT** returns a **TRUE** state.
- If  $A \leq B$ , then the **GRT** returns a **FALSE** state.

77



# GRT – Configuration

## GRT – Greater Than

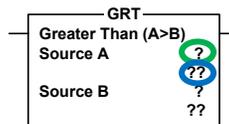

The **GRT (Greater Than)** instruction is used to compare the values of two numbers, A and B.


- Source A – This field contains either a numerical value for A or a tag name relating to the data that contains the value for A.
- If the Source A field contains a tag name, the second field shows the value currently identified by that tag.

78



## GRT – Configuration

### GRT – Greater Than

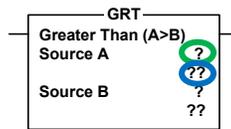

The **GRT (Greater Than)** instruction is used to compare the values of two numbers, A and B.


- Source A – This field contains either a numerical value for A or a tag name relating to the data that contains the value for A.
- If the Source A field contains a tag name, the field immediately below Source A displays the value currently stored in the tag assigned to Source A.

79



## GRT – Configuration

### GRT – Greater Than

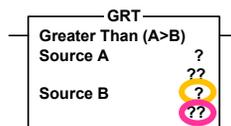

The **GRT (Greater Than)** instruction is used to compare the values of two numbers, A and B.


- Source B – This field contains either a numerical value for B or a tag name relating to the data that contains the value for B.
- If the Source B field contains a tag name, the field immediately below Source B displays the value currently stored in the tag assigned to Source B.

80


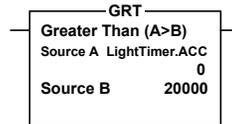
## GRT Example



The following **GRT** is configured to compare the value stored in **LightTimer's** accumulator to the number 20,000.



Note that the value stored in **LightTimer's** accumulator is displayed in the field immediately below Source A as shown in the following examples:

Thus, when the **GRT** is evaluated:

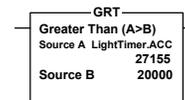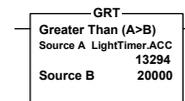- If *LightTimer.ACC* is  $\leq 20000$ , the **GRT** will return a **FALSE** state.
- While *LightTimer.ACC* is  $> 20000$ , the **GRT** will return a **TRUE** state.




81


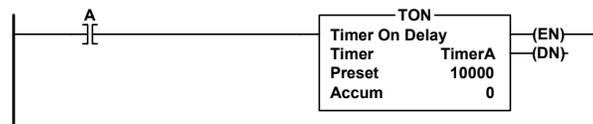
## Self-Repeating Timer Example

What if you have a 10-second timer that, after it is “enabled”, needs to count to 10 seconds and then automatically reset back to zero and begin counting again, and will continue to do so until it is “disabled”?




To perform this task, the timer's *.DN* bit can be utilized to trigger a reset of the timer whenever the timer's Accumulator reaches the Preset value (i.e. – it is “done” counting).

82


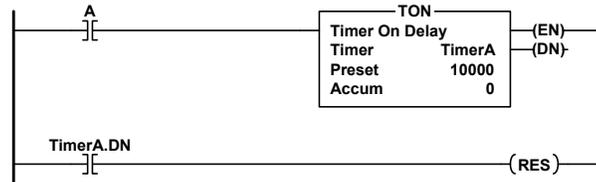
## Self-Repeating Timer Example

Given the following rungs that contain a **TON** and a **RES**:



If bit **A** is initially zero ( $A=0$ ):


- ⇒ **XIC-A** ≡ **FALSE**
- ⇒ the **Rung Condition** for the **TON** is **FALSE**
- ⇒ the **TON** is disabled (and thus  $TimerA.EN=0$ )
- ⇒ **XIC-TimerA** ≡ **FALSE**
- ⇒ the **Rung Condition** for the **RES** is **FALSE**

83



## Self-Repeating Timer Example

Timer initially Enabled

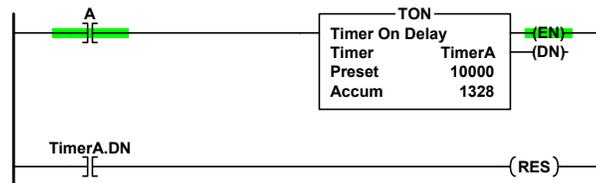


- If bit **A** → 1
- ⇒ **XIC-A** ≡ **TRUE**
  - ⇒ the **Rung Condition** for the **TON** is **TRUE**
  - ⇒ **TON-TimerA** is enabled
  - ⇒ the timer's *Enable* bit is set ( $.EN \rightarrow 1$ )
  - ⇒ the timer's accumulator begins incrementing
  - ⇒ the timer's *Time Transitioning* bit is set ( $.TT \rightarrow 1$ )

84



## Self-Repeating Timer Example

Timer reaches its Preset Value

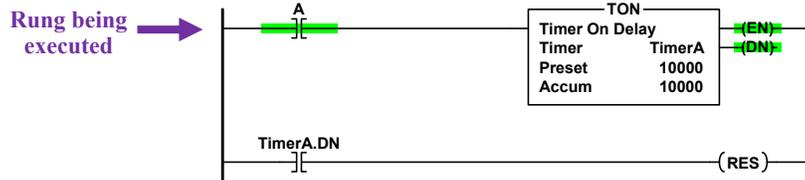


When *TimerA.ACC* increments to 10000:

⇒ the timer's *Done* bit is set (*.DN* → 1)


Note that, even though the *.DN* bit has been set, the state of the **XIC** on the second rung will not change to **TRUE** until the **RES's** rung is executed again (after the *.DN* bit was set).

85

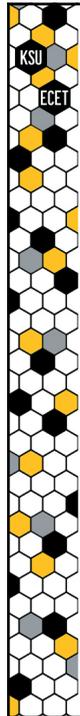

## Self-Repeating Timer Example

Timer is Reset

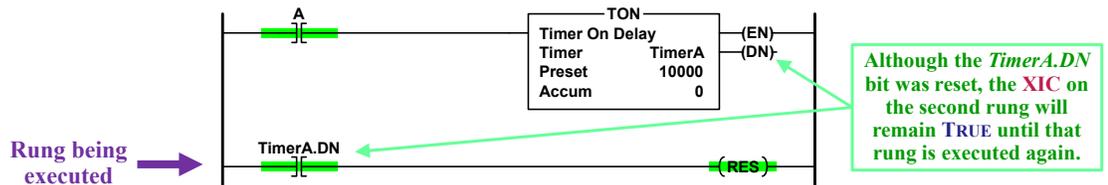

The next time the **RES's** rung is executed (after the *.DN* bit was set):

⇒ **XIC-*TimerA.DN*** ≡ **TRUE**

⇒ the **Rung Condition** for the **RES** is **TRUE**

⇒ the **RES** resets **TimerA's** status bits and it resets **TimerA's** accumulator back to its **initial value**

86



## Self-Repeating Timer Example

Timer is re-Enabled



The next time the **TON's** rung is executed (after the **TON** was reset):


- ⇒ **XIC-A**  $\equiv$  **TRUE** (it never changed to **FALSE**)
- ⇒ the **Rung Condition** for the **TON** is still **TRUE**
- ⇒ **TON-TimerA** is re-enabled, its **.EN** bit is set, its accumulator begins incrementing again, and its **.TT** bit is set

87



## Self-Repeating Timer Example

After the Timer is re-Enabled

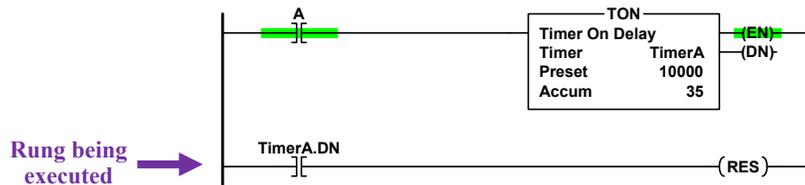

The next time the **RES's** rung is executed (after the **TON** was reset):

- ⇒ **XIC-TimerA**  $\equiv$  **TRUE**
- ⇒ the **Rung Condition** for the **RES** is **FALSE**
- ⇒ the **RES** does nothing


As long as bit A remains set ( $A = 1$ ), the **TON** will remain enabled and it will continue incrementing until it's "Done" again, at which time the **RES** will reset the timer again. This process will repeat indefinitely.

88



# Other Instructions – Counter Up (CTU)

The **CTU (Counter Up)** is an **Output Instruction** whose function is similar to that of the On-Delay Timer:

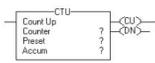
Instruction:	Relay Ladder:	Function Block:	Structured Text:	Description:
CTU Counter Up		see CTUD	see CTUD	The CTU instruction counts upward.
Operand:	Type:	Format:	Description:	
Counter	COUNTER	tag	counter structure	
Preset	DINT	immediate	how high to count	
Accum	DINT	immediate	number of times the counter has counted; initial value is typically 0	
Arithmetic Status Flags:		Major Faults:		
not affected		none		

The Counter Up (CTU) is useful for keeping track of the number of specific events that occur, such as the number of items passing by an optical detector. When the CTU's rung-condition becomes TRUE, the CTU's accumulator is incremented by one (1). Note that, for the CTU to count up again, the CTU's rung-condition must first become FALSE and then TRUE again.



# Off-Delay Timer (TOF)

**TOF – OFF Delay Timer**

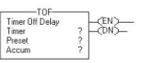Instruction:	Relay Ladder:	Function Block:	Structured Text:	Description:
TOF Timer Off Delay		see TOFR	see TOFR	The TOF instruction is a non-retentive timer that accumulates time when the instruction is enabled (rung-condition-in is false).
Operand:	Type:	Format:	Description:	
Timer	TIMER	tag	timer structure	
Preset	DINT	immediate	how long to delay (accumulate time)	
Accum	DINT	immediate	number of msec the timer has counted; initial value is typically 0	
Arithmetic Status Flags:		Major Faults:		
not affected		Type 4	Code 34	<ul style="list-style-type: none"> <li>• PRE &lt; 0</li> <li>• ACC &lt; 0</li> </ul>

The Off-Delay timer (TOF) works similar to the On-Delay timer (TON) except that the TOF is enabled when its rung-condition becomes FALSE.